 


Electronics for Particle Physics


Christophe de LA TAILLE

OMEGA microelectronics group
Ecole Polytechnique & CNRS IN2P3
<http://omega.in2p3.fr>

- A lot of electronics in the experiments...
 - The performance of electronics often impacts on the detectors
 - Analog electronics (V,A,A...) / Digital electronics (bits)




ATLAS detector in 2008

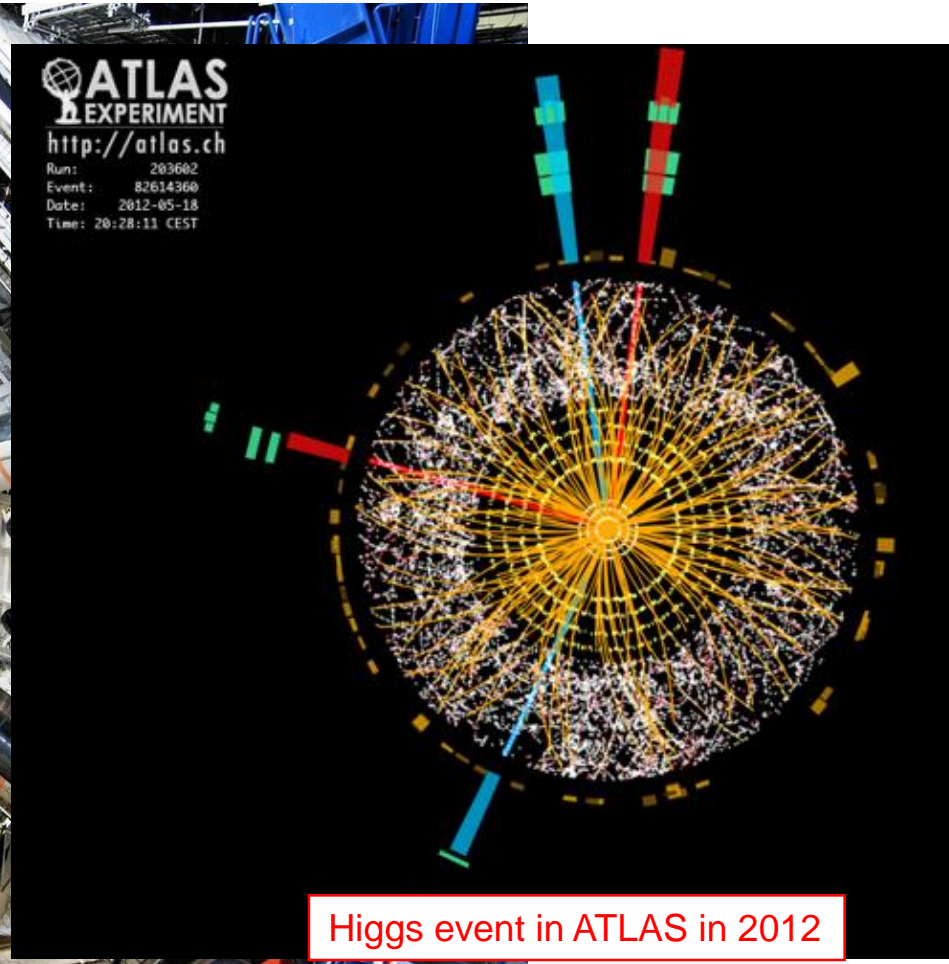


Higgs event in ATLAS in 2012

 
- Measurement of (charged) particle tracks
 - millions of pixels (~100 μm)
 - binary readout at 40 MHz
 - High radiation levels
 - Made possible by ASICs



Tracks in an e+e- collision at ILC

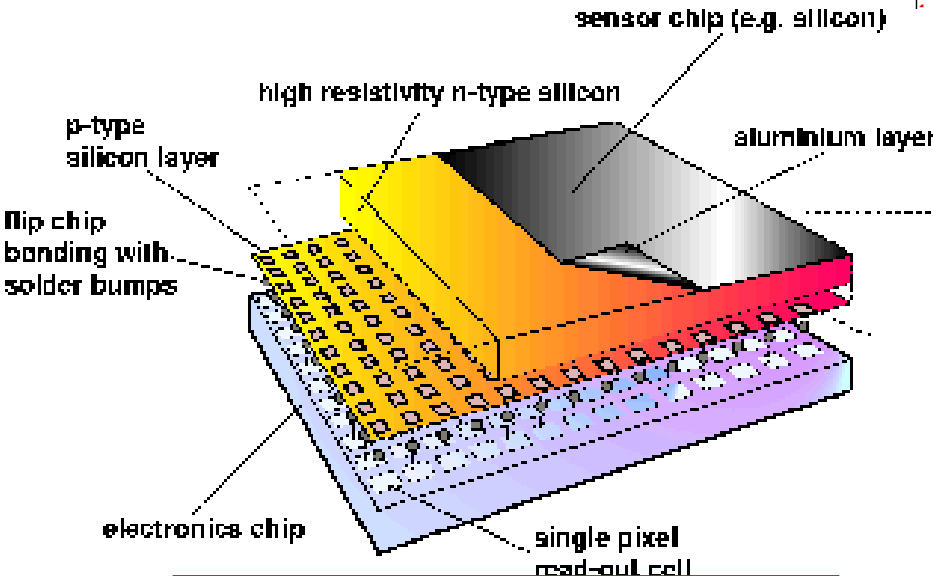



Pixel detector and readout electronics

 


Pixel detector in CMS


- Large dynamic range (10^4 - 10^5)
- High Precision $\sim 1\%$
 - Importance of low noise, uniformity, lli
 - Importance of calibration

H -> $\gamma\gamma$ in CMS calorimeter

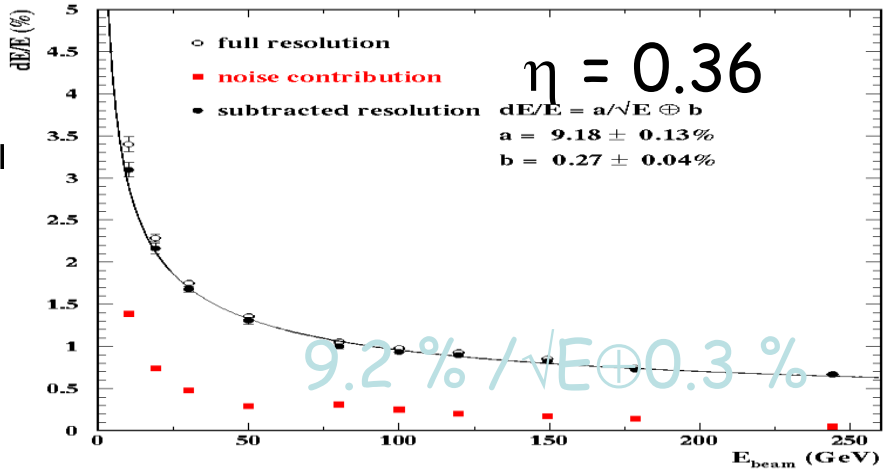 

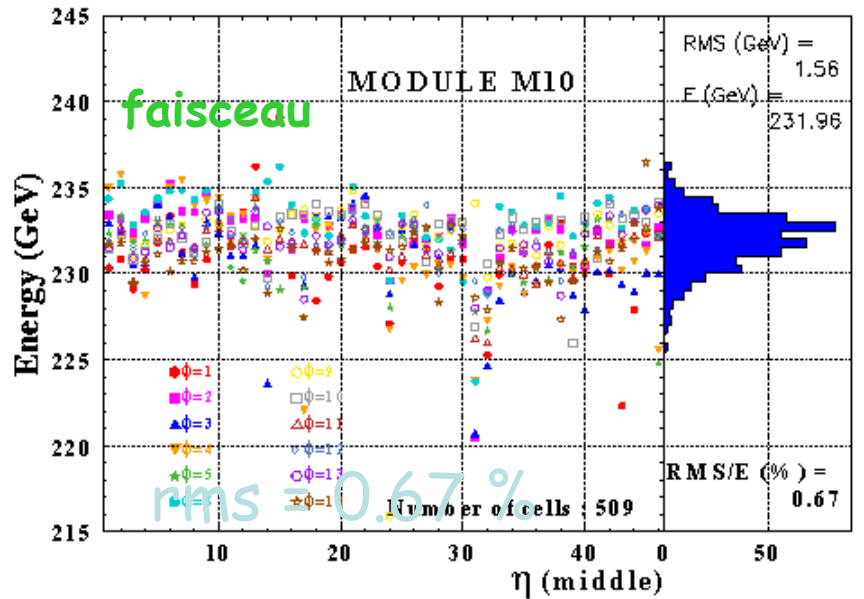Energy resolution and uniformity in ATLAS




 

- For humans
 - large diameter FOV (>60 cm)
 - spatial resolution: **few mm**
 - time resolution **CRT < 400 ps** for ToF
 - high sensitivity (low dose) → large area
 - high total data rate
- For mice, rats, rabbits (& human brain)
 - Small diameter FOV (4-15 cm)
 - spatial resolution: **< 1 mm**
 - time resolution only for coinc. (few ns)
 - medium sensitivity
 - Depth - of - Interaction desirable to fight parallax effect


■ Voltage generators or source

 - Ideal source : constant voltage, independent of current (or load)
- In reality : non-zero source impedance R_S




• Current generators

 - Ideal source : constant current, independent of voltage (or load)
- In reality : finite output source impedance R_S



■ Ohms' law

 
- $Z = R, 1/j\omega C, j\omega L$
- Note the **sign** convention





Frequency domain & time domain

- **Frequency domain :**

 - $V(\omega, t) = A \sin(\omega t + \varphi)$
 - Described by **amplitude** and **phase** (A, φ)
- **Transfer function : $H(\omega)$ [or $H(s)$]**
- = The ratio of output signal to input signal in the frequency domain assuming **linear** electronics
- $V_{out}(\omega) = H(\omega) V_{in}(\omega)$



\mathcal{F}^{-1}

  

- **Time domain**

- **Impulse response : $h(t)$**
- = the output signal for an **impulse** (delta) input in the time domain
- The output signal for **any** input signal $v_{in}(t)$ is obtained by **convolution** : «*» :
- $V_{out}(t) = v_{in}(t) * h(t) = \int v_{in}(u) * h(t-u) du$

- $H(\omega) = 1 \rightarrow h(t) = \delta(t)$ (impulse)
- $H(\omega) = 1/j\omega \rightarrow h(t) = S(t)$ (step)
- $H(\omega) = 1/j\omega (1+j\omega T) \rightarrow h(t) = 1 - \exp(-t/T)$
- $H(\omega) = 1/(1+j\omega T) \rightarrow h(t) = \exp(-t/T)$
- $H(\omega) = 1/(1+j\omega T)^n \rightarrow h(t) = 1/n! (t/T)^{n-1} \exp(-t/T)$
- ...




- **Correspondance through Fourier transforms**


- $X(\omega) = \mathcal{F}\{x(t)\} = \int x(t) \exp(j\omega t) dt$
- a few useful Fourier transforms in appendix

Frequency response

- **Bode plot**

- Magnitude (dB) = $20 \log |H(j\omega)|$
- -3dB bandwidth : $f_{-3dB} = 1/2\pi RC$
 - $R=10^5\Omega$, $C=10\text{pF} \Rightarrow f_{-3dB}=160 \text{ kHz}$
 - At f_{-3dB} the signal is attenuated by 3dB $\sqrt{2}$, the phase is -45°
- Above f_{-3dB} , gain **rolls-off** at **20dB/decade** (or -6dB/octave)

  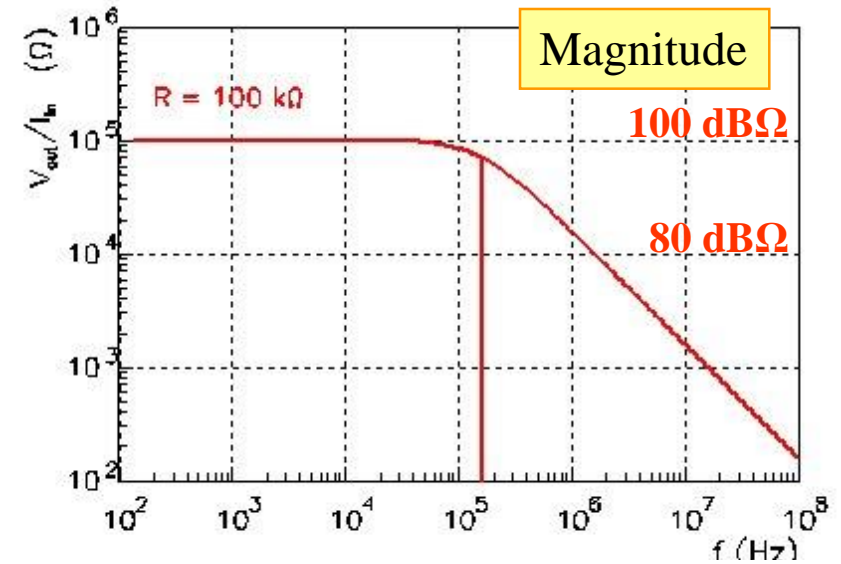


 

ATLAS : Higgs boson




Planck : CMB

 

CDF : top quark



Edelweiss : dark matter




 


SuperK : neutrino oscillations




AUGER : cosmic rays 10^{20} eV

   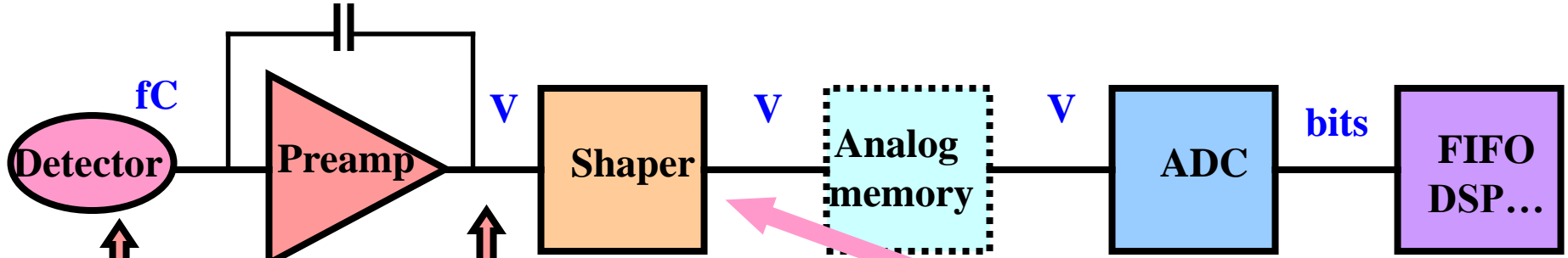- Most front-ends follow a similar architecture




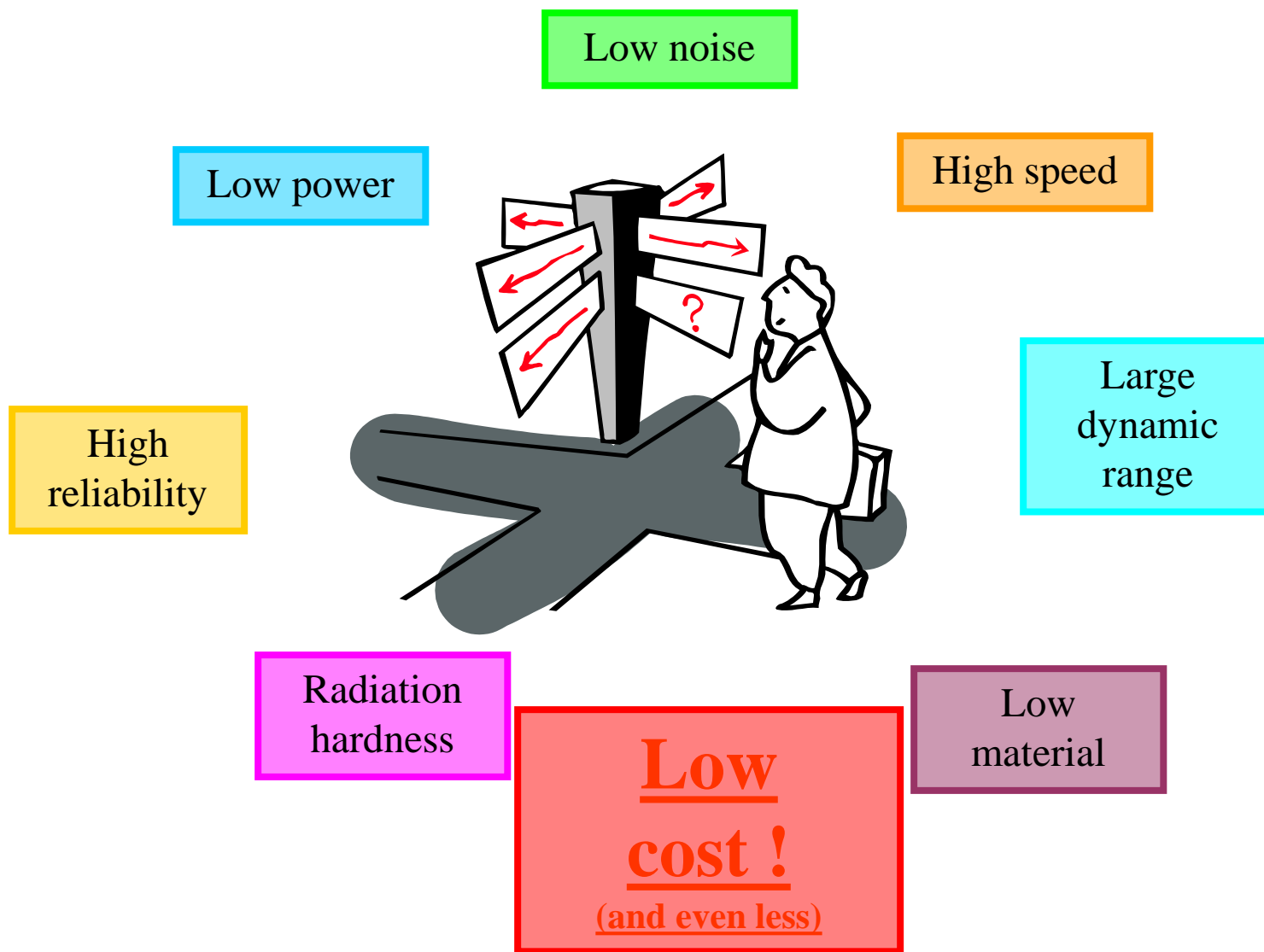- n Very small signals (fC) -> need **amplification**
- n Measurement of **amplitude** and/or **time** (**ADCs**, **discris**, **TDCs**)
- n Several thousands to millions of channels
- n **Trends** : high speed, low power



Detector modelization


- Detector = capacitance C_d
 - Pixels/strips : 0.1-10 pF
 - PMs/SiPMs : 3-300 pF
 - Ionization chambers 10-1000 pF
 - Sometimes effect of transmission line
- Signal : current source
 - Pixels : $\sim 100e^-/\mu\text{m}$
 - PMs : 1 photoelectron $\rightarrow 10^5\text{-}10^7 e^-$
 - Modelized as an impulse (Dirac) :
 $i(t) = Q_0 \delta(t)$
- Missing :
 - High Voltage bias
 - Connections, grounding
 - Neighbours
 - Calibration...

 

Detector modelization



CMS pixel module

 


ATLAS LAr calorimeter

Vacuum Photomultipliers

$$G = 10^5 - 10^7$$

$$C_d \sim 10 \text{ pF}$$

$$L \sim 10 \text{ nH}$$



 


Silicon Photomultipliers

$$G = 10^5 - 10^7$$

$$C = 10 - 400 \text{ pF}$$

$$L = 1 - 10 \text{ nH}$$

   

Optimizing signal shape for timing


Collazuol 2012

Single cell model $\rightarrow (R_d || C_d) + (R_q || C_q)$

SiPM + load $\rightarrow (||Z_{cell}) || C_{grid} + Z_{load}$


Signal = **slow** pulse ($\tau_{d (rise)}, \tau_{q-slow (fall)}$) + **fast** pulse ($\tau_{d (rise)}, \tau_{q-fast (fall)}$)

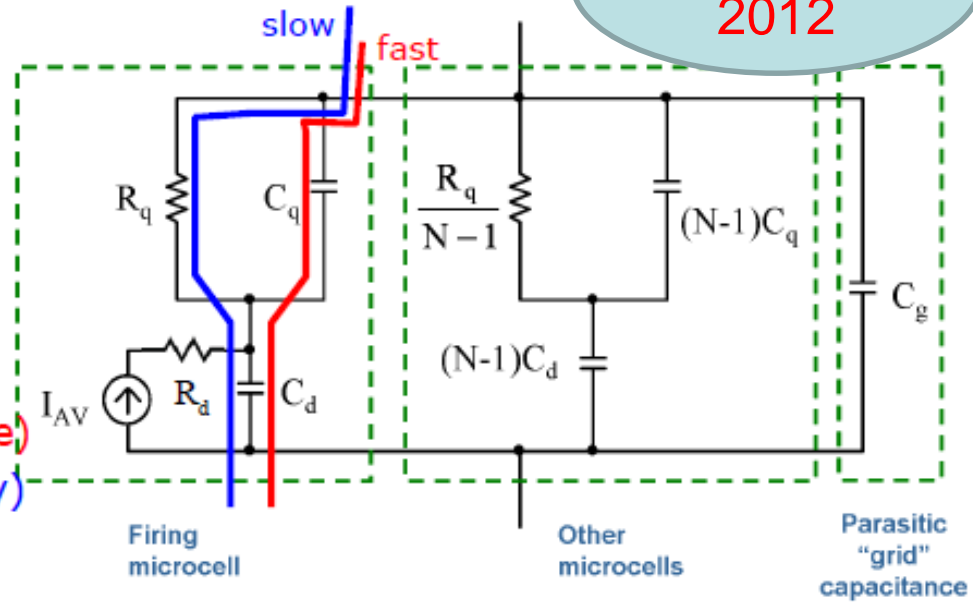- $\tau_{d (rise)} \sim R_d (C_q + C_d)$
- $\tau_{q-fast (fall)} = R_{load} C_{tot}$ (fast; parasitic spike)
- $\tau_{q-slow (fall)} = R_q (C_q + C_d)$ (slow; cell recovery)



Pulse shape
 
$$V(t) \approx \frac{Q}{C_q + C_d} \left(\frac{C_q}{C_{tot}} e^{-\frac{t}{\tau_{FAST}}} + \frac{R_{load}}{R_q} \frac{C_d}{C_q + C_d} e^{-\frac{t}{\tau_{SLOW}}} \right)$$



→ charge ratio $\frac{Q_{fast}}{Q_{slow}} \sim \frac{C_q}{C_d}$



→ peak height ratio $\frac{V_{fast}^{max}}{V_{slow}^{max}} \sim \frac{C_q^2 R_q}{C_d C_{tot} R_{load}}$ increasing with R_q and $1/R_{load}$ (and C_q of course)

Increasing C_q/C_d or/and R_q/R_{load}
 → spike enhancement
 → better timing

  G. Collazuol - PhotoDet 2012

SiPM impedance and model


- RLC too simple, inaccurate at high frequency
- CdRqCqLR OK
 - May better explain HF noise behaviour



Measured impedance
MPPC HPK 3x3 mm
Line : $C = 320 \text{ pF}$

- Signal

 
- Signal = current source
- Detector = capacitance C_d
- Quantity to measure
 - Charge => integrator needed
 - Time => discriminator + TDC



Voltage readout

- Integrating on C_d


 
- Simple : $V = Q/C_d$
- « Gain » : $1/C_d$: 1 pF -> 1 mV/fC
- Need a follower to buffer the voltage...
- Gain loss, possible non-linearities
- crosstalk
- Need to empty C_d ...



Impulse response

 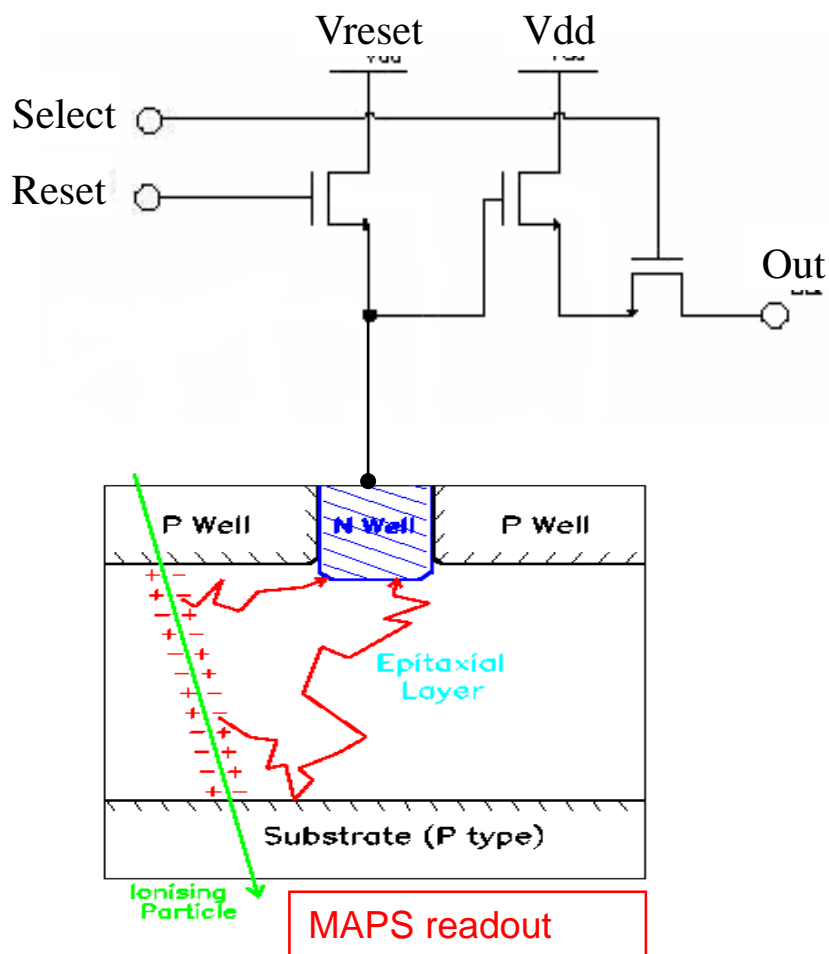
Example : Monolithic active pixels

- Epitaxial layer forms sensitive volume (2-20 μm)
- Charge collection by diffusion
- Read $\sim 100\text{ e}^-$ on Cd $\sim 10\text{fF}$ = few mV




Ideal charge preamplifier


 
- ideal opamp in transimpedance
 - Shunt-shunt feedback
 - transimpedance : v_{out}/i_{in}
 - $V_{in}=0 \Rightarrow V_{out}(\omega)/i_{in}(\omega) = -Z_f = -1/j\omega C_f$
 - **Integrator** : $v_{out}(t) = -1/C_f \int i_{in}(t)dt$
- $$v_{out}(t) = -Q/C_f$$
- « Gain » : $1/C_f$: 0.1 pF \rightarrow 10 mV/fC
 - C_f determined by maximum signal



 - Integration on C_f
 - Simple : $V = -Q/C_f$
 - Unsensitive to preamp capacitance C_{PA}
 - Turns a short signal into a long one
 - **The front-end of 90% of particle physics**
 - **But always built with custom circuits...**





- Finite opamp gain
 - $V_{out}(\omega)/i_{in}(\omega) = -Z_f / (1 + C_d / G_0 C_f)$
 - Small signal loss in $C_d/G_0 C_f \ll 1$ (ballistic deficit)
- Finite opamp bandwidth
 - First order open-loop gain
 - $G(\omega) = G_0 / (1 + j \omega / \omega_0)$
 - G_0 : low frequency gain
 - $G_0 \omega_0$: gain bandwidth product
- Preamp risetime
 - Due to gain variation with ω
 - Time constant : τ (*tau*)
 - $\tau = C_d / G_0 \omega_0 C_f$
 - Rise-time : $t_{10-90\%} = 2.2 \tau$
 - Rise-time optimised with w_C or C_f

  

Impulse response with non-ideal preamp

Charge preamp seen from the input

- Input impedance with ideal opamp
 - $Z_{in} = Z_f / G+1$
 - $Z_{in} \rightarrow 0$ for ideal opamp
 - « Virtual ground » : $V_{in} = 0$
 - Minimizes sensitivity to detector impedance
 - Minimizes crosstalk
- Input impedance with real opamp
 - $Z_{in} = 1/j\omega G_0 C_f + 1/ G_0 \omega_0 C_f$
 - Resistive term : $R_{in} = 1/ G_0 \omega_0 C_f$
 - Exemple : $\omega_C = 10^{10}$ rad/s $C_f = 1$ pF $\Rightarrow R_{in} \approx 100 \Omega$
 - Determines the input time constant :
 - $t = R_{eq} C_d$
 - Good stability= (...!)
 - Equivalent circuit :

  


SIGNAL, NOISE AND RESOLUTION IN POSITION-SENSITIVE DETECTORS*

 
V. Radeka
 Brookhaven National Laboratory
 Upton, N. Y. 11973

ABSTRACT


An analysis is presented of signal, noise and position resolution relations for some of the most interesting position-sensing methods. "Electronic cooling" of delay line terminations is introduced in order to reduce noise in the position-sensing with delay lines. A new method for terminating transmission lines and for "noiseless" damping which employs a capacitance in feedback is presented. It is shown that the position resolution for the charge division method with resistive electrodes is determined only by the electrode capacitance and not by the electrode resistance, if optimum filtering is used.



 
$$Z_{in} = 1/j\omega G_0 C_F + 1/ G_0 \omega_0 C_F$$



 
- Capacitive coupling between neighbours
 - Crosstalk signal is **differentiated and with same polarity**
 - Small contribution at signal peak
 - Proportionnal to C_x/C_d and preamp input impedance
 - Slowed derivative if $R_{in}C_d \sim t_p \Rightarrow$ non-zero at peak
- Long distance crosstalk
 - Inductive/resistive common ground return
 - References impedance
 - Connectors : mutual inductance



Crosstalk electrical modelization



 


 - Definition of Noise
 - Random fluctuation superposed to interesting signal
 - Statistical treatment
- Three types of noise
 - Fundamental noise (Thermal noise, shot noise)
 - Excess noise ($1/f$...)
 - Parasitics -> EMC/EMI (pickup noise, ground loops...)




- Modelization
 - Noise generators : $e_n, i_n,$
 - Noise spectral density of e_n & i_n : $S_v(f)$
 - $S_v(f) = | \mathcal{F}(e_n) |^2$ (V²/Hz)

   - Rms noise V_n
 - $V_n^2 = \int e_n^2(t) dt = \int S_v(f) df$
 - White noise (e_n) : $v_n = e_n \sqrt{\frac{1}{2} \pi f_{-3dB}}$





Calculating electronics noise

 - Fundamental noise
 - Thermal noise (**resistors**) : $S_v(f) = 4kTR$
 - Shot noise (**junctions**) : $S_i(f) = 2qI$



  - Noise referred to the input
 - All noise generators can be referred to the input as **2** noise generators :
 - A voltage one e_n in series : **series noise**
 - A current one i_n in parallel : **parallel noise**
 - Two generators : no more, no less...



■ **To take into account the Source impedance**


■ **Golden rule :**

- **Always calculate the signal before the noise**
what counts is the signal to noise ratio


Noise generators
referred to the input

Noise in transimpedance amplifiers



- 2 noise generators at the input
 - Parallel noise : (i_n^2) (leakage)
 - Series noise : (e_n^2) (preamp)
- Output noise spectral density :
 - $S_v(\omega) = (i_n^2 + e_n^2/|Z_d|^2) * |Z_f|^2$
- For charge preamps
 - $S_v(\omega) = i_n^2 / \omega^2 C_f^2 + e_n^2 C_d^2 / C_f^2$
 - Parallel noise in $1/\omega^2$
 - Series noise is flat, with a « noise gain » of C_d/C_f
- rms noise V_n
 - $V_n^2 = \int S_v(\omega) d\omega / 2\pi \rightarrow \infty$
 - Benefit of shaping ...

 

Noise generators in charge preamp

 


- Noise reduction by optimising useful bandwidth
 - Low-pass filters (**RCⁿ**) to cut-off high frequency noise
 - High-pass filter (**CR**) to cut-off parallel noise
 - -> pass-band filter CRRCⁿ
- Equivalent Noise Charge : **ENC**
 - Noise referred to the input in electrons
 - $ENC = I_a(n) e_n C_t / \sqrt{T} \oplus I_b(n) i_n^* \sqrt{T}$
 - Series noise in $1/\sqrt{T}$
 - Parallel noise in \sqrt{T}
 - 1/f noise independant of T
 - Optimum shaping time $\tau_{opt} = \tau_c / \sqrt{2n-1}$

  

Step response of CR RCⁿ shapers

t/τ_c

 - Peaking time t_p (5-100%)
 - ENC(t_p) independent of n
 - Also includes preamp risetime
- Complex shapers are **obsolete** :
 - Power of **digital filtering**
 - Analog filter = CRRC ou CRRC²
 - antialiasing



ENC vs tau for CR RCⁿ shapers


- A useful formula : **ENC (e⁻ rms) after a CRRC² shaper :**

$$\text{ENC} = 174 e_n C_{\text{tot}} / \sqrt{t_p} (\delta) \oplus 166 i_n \sqrt{t_p} (\delta)$$

- e_n in nV/ $\sqrt{\text{Hz}}$, i_n in pA/ $\sqrt{\text{Hz}}$ are the **preamp** noise spectral densities
- C_{tot} (in pF) is dominated by the detector (C_d) + input preamp capacitance (C_{PA})
- t_p (in ns) is the shaper peaking time (5-100%)


■ Noise minimization

 - Minimize source capacitance
- Operate at optimum shaping time
- Preamp series noise (e_n) best with high transconductance (g_m) in input transistor
=> large current, optimal size




 Example of ENC measurement

- 2000/0.35 PMOS 0.35 μ m SiGe $I_d=500 \mu$ A
 - Series : $e_n = 1.4 \text{ nV}/\sqrt{\text{Hz}}$, $C_{PA} = 7 \text{ pF}$
 - 1/f noise : 12 e-/pF
 - Parallel : $i_n = 40 \text{ fA}/\sqrt{\text{Hz}}$





ENC vs peaking time



 


ENC vs Capacitance $t_p=100\text{ns}$

ENC for various technologies

  

 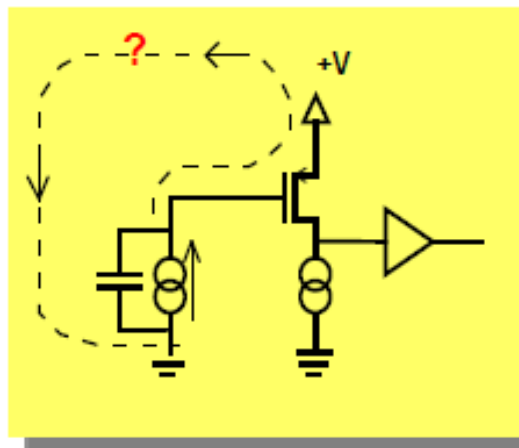 
- PMOS lower $1/f$ noise
- NMOS white series noise advantage over PMOS diminishes each generation
- PMOS can be operated at reverse V_{BS} to reduce bulk resistance noise
- PMOS lower tunneling current at ultra-thin t_{ox}
- Single-supply operation of PMOS-input preamp awkward:




Ultra-Low Noise ASIC High Resolution X-Ray Spectroscopy

Collaboration with NASA at Moon Elemental Mapping

 16 mm² Semiconductor Drift Pixels, 500 cm²



 - 14 channels, 1.2 mW/channel
- **sub-10 electrons resolution**
- **peak detection and sparse readout**
- 30,000 transistors, dev. time: 15 months



G. De Geronimo et al., NSS (2007)
Instrumentation Div. Review


11/12/2008

Electronics and Signal Processing

26

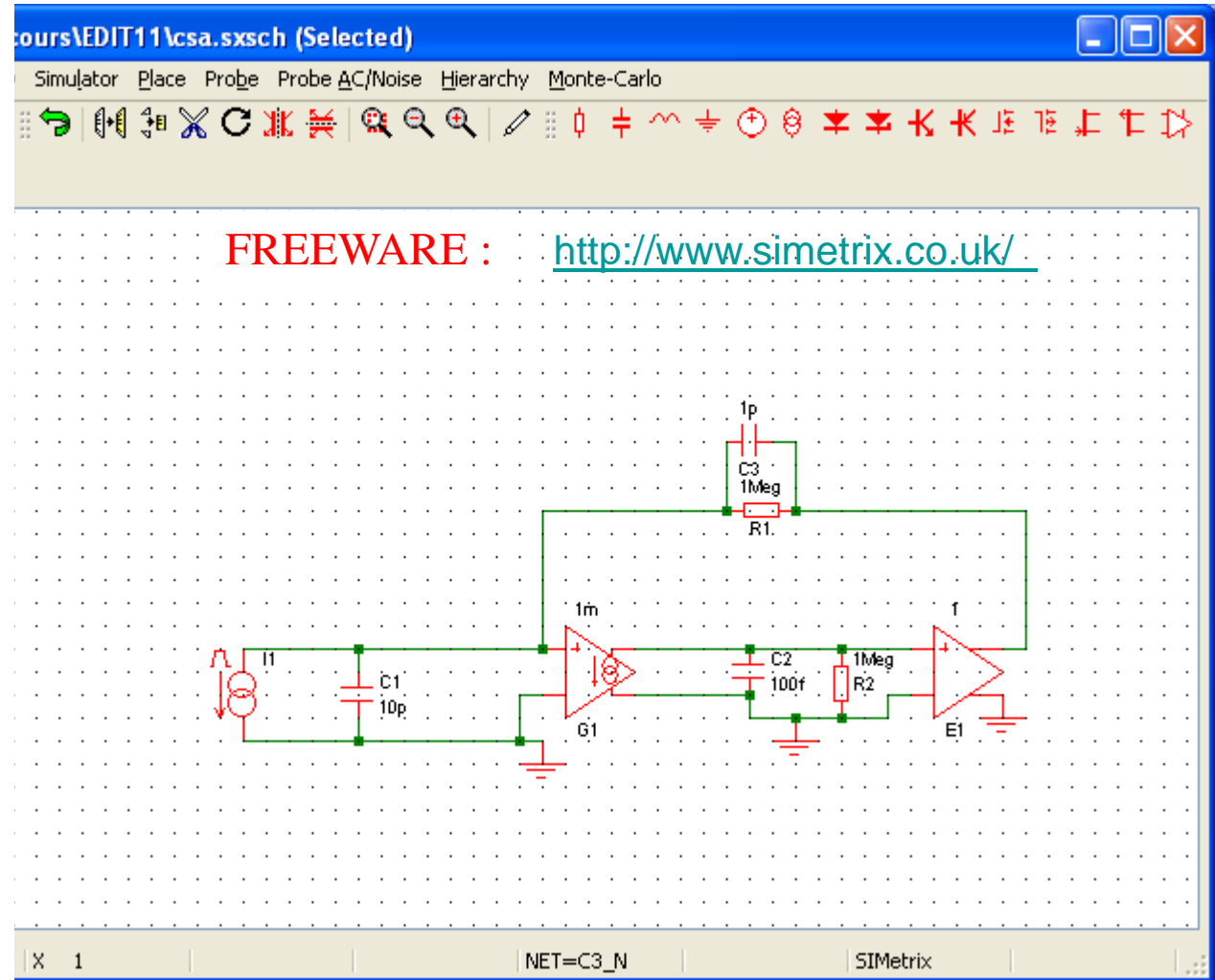
Example : bandwidth and EMC of simple charge preamp

- Simulate impulse response
- Frequency response
- Input impedance
- Ballistic deficit
- Effect of amplifier gain
- Effect of resistive feedback
- Test pulse injection
- Effect of input capacitance
- **Parasitic inductance**
- Capacitive crosstalk
- Resistive/Inductive ground return



FREEWARE : <http://www.simetrix.co.uk/>

- Importance of front-end on electronics on physics performance
- Benefits of charge preamplifiers :
low noise, low crosstalk
 - The front-end of 90% of particle physics detectors...
 - But always built with custom circuits...

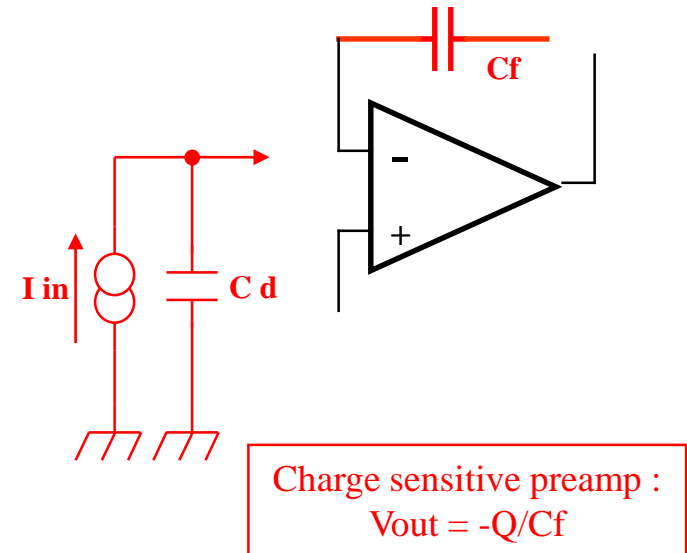



 
 



Figure 3

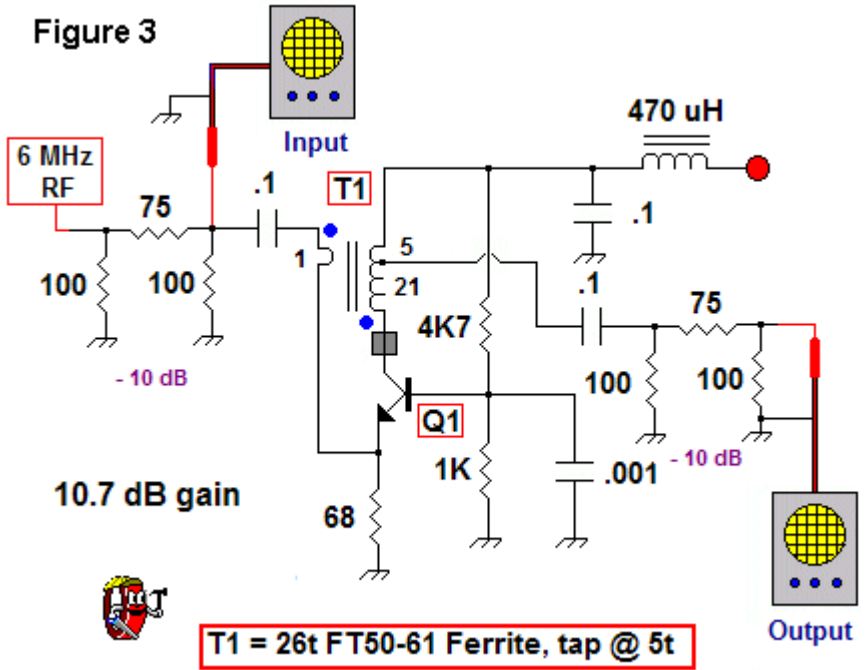

 - Charge preamp
- Capacitive feedback C_f
- $V_{out}/I_{in} = -1/j\omega C_f$
- Perfect integrator : $v_{out} = -Q/C_f$
- Difficult to accommodate large SiPM signals (200 pC)
- Lowest noise configuration
- Need R_f to empty C_f




 - Current preamp
- Resistive feedback R_f
- $V_{out}/I_{in} = -R_f$
- Keeps signal shape
- Need C_f for stability




Transimpedance configuration

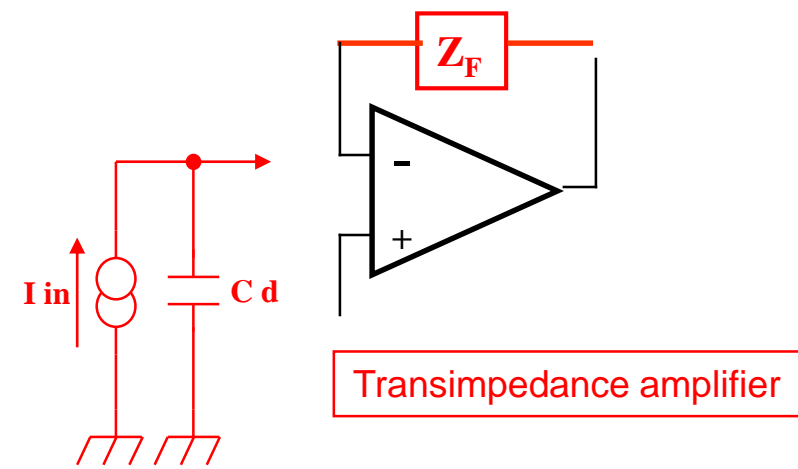- Transfer function
 - Using a VFOA with gain G
 - $V_{out} - v_{in} = -Z_f i_f$
 - $V_{in} = Z_d (i_{in} - i_f) = -v_{out}/G$
 - $V_{out}(\omega)/i_{in}(\omega) = -Z_f / (1 + Z_f / GZ_d)$



 
- $Z_f = R_f / (1 + j\omega R_f C_f)$
 - At $f \ll 1/2\pi R_f C_f$:
 - $V_{out}(\omega)/i_{in}(\omega) = -R_f$
 - current preamp**
 - At $f \gg 1/2\pi R_f C_f$:
 - $V_{out}(\omega)/i_{in}(\omega) = -1/j\omega C_f$
 - charge preamp**



- Ballistic deficit with charge preamp
 - Effect of finite gain : G_0
 - Output voltage «only» $Q C_d / G_0 C_f$


Transfer function

 - Charge preamps
 - Best noise performance
 - Best with short signals
 - Best with small capacitance
- Current preamps
 - Best for long signals
 - Best for high counting rate
 - Significant parallel noise
- Charge preamps are not slow, they are long
- Current preamps are not faster, they are shorter (but easily unstable)




Input impedance

- Input impedance
 - $Z_{in} = Z_f / G + 1$
 - $Z_{in} \rightarrow 0$ **virtual ground**
 - Minimizes sensitivity to detector impedance
 - Minimizes crosstalk
- Equivalent model
 - $G(\omega) = G_0 / (1 + j \omega / \omega_0)$
- Terms due to C_f
 - $Z_{in} = 1 / j\omega G_0 C_f + 1 / G_0 \omega_0 C_f$
 - **Virtual resistance** : $R_{eq} = 1 / G_0 \omega_0 C_f$
- Terms due to R_f
 - $Z_{in} = R_f / G_0 + j \omega R_f / G_0 \omega_0$
 - **Virtual inductance** : $L_{eq} = R_f / G_0 \omega_0$
- Possible oscillatory behaviour with capacitive source

 

Input impedance or TZA

 

Equivalent circuit at the input

Current preamplifiers :

- Easily oscillatory
 - Unstable with capacitive detector
 - Inductive input impedance :


$$L_{eq} = R_f / \omega_C$$
 - Resonance at : $f_{res} = 1/2\pi \sqrt{L_{eq} C_d}$
 - Quality factor : $Q = R / \sqrt{L_{eq}/C_d}$
 - $Q > 1/2 \rightarrow$ ringing
 - Damping with capacitance C_f
 - $C_f = 2 \sqrt{(C_d/R_f G_0 \omega_0)}$
 - Easier with fast amplifiers

- In frequency domain


- $H(j\omega) = -R_f / (1 + j\omega R_f C_d)$

- $G(\omega) = G_0 / (1 + j\omega/\omega_0)$
 
$$H = -R_f / (1 + j\omega R_f C_d / G_0 - \omega^2 R_f C_d / G_0 \omega_0)$$





 Step response of current sensitive preamp



42


- Voltage feedback operational amplifier (VFOA)
 - Voltage amplifiers, RF amplifiers (VA,LNA)
 - Current feedback operational amplifiers (CFOA)
 - Current conveyors (CCI, CCII +/-)
 - Current (pre)amplifiers (ISA,PAI)
 - Charge (pre)amplifiers (CPA,CSA,PAC)
 - Transconductance amplifiers (OTA)
 - Transimpedance amplifiers (TZA,OTZ)
-
- **Mixing up open loop (OL) and closed loop (CL) configurations !**

  

Only 4 open-loop configurations


- Voltage operational amplifiers (OA, VFOA)

 - $V_{out} = G(\omega) V_{in\ diff}$
- $Z_{in+} = Z_{in-} = \infty$ $Z_{out} = 0$




- Transimpedance operational amplifier (CFOA !)

 - $V_{out} = Z(\omega) i_{in}$
- $Z_{in-} = 0$ $Z_{out} = 0$




- Current conveyor (CCI,CCII)

 - $i_{out} = G(\omega) i_{in}$
- $Z_{in} = 0$ $Z_{out} = \infty$



- Transconductance amplifier (OTA)

 
- $i_{out} = G_m(\omega) V_{in\ diff}$
- $Z_{in+} = Z_{in-} = \infty$ $Z_{out} = \infty$



Open loop gain variation with frequency




 - Define exactly what is « gain » v_{out}/v_{in} , v_{out}/i_{in} ...
- « Gain » varies with frequency : $G(j\omega) = G_0/(1 + j \omega/\omega_0)$
 - G_0 low frequency gain
 - ω_0 dominant pole
 - $\omega_c = G_0 \omega_0$ Gain-Bandwidth product (sometimes referred to as unity gain frequency)



Feedback : an essential tool

 - Improves gain performance
 - Less sensitivity to open loop gain (a)
 - Better linearity



- Essential in low power design

- Potentially unstable


$$\frac{X_{out}}{X_{in}} = \frac{a}{1 + a\beta} = \frac{1/\beta}{1 + 1/a\beta}$$

- Feedback constant : $\beta = E/X_{out}$

- Open loop gain : $a = X_{out}/E$


- Closed loop gain : $X_{out}/X_{in} \rightarrow 1/\beta$

- Loop gain : $T = 1/a\beta$

 


Only 4 feedback configurations

- Shunt-shunt = transimpedance
 - Small Z_{in} ($= Z_{in}(OL)/T$) -> current input
 - small Z_{out} ($= Z_{out}(OL)/T$) -> voltage output
 - De-sensitizes transimpedance $= 1/\beta = Z_f$
- Series-shunt
 - Large Z_{in} ($= Z_{in}(OL)*T$) -> voltage input
 - Small Z_{out} ($= Z_{out}(OL)/T$) -> voltage output
 - Optimizes voltage gain ($= 1/\beta$)
- Shunt series
 - Small Z_{in} ($= Z_{in}(OL)/T$) -> current input
 - Large Z_{out} ($= Z_{out}(OL)*T$) -> current output
 - Current conveyor
- Series-series
 - Large Z_{in} ($= Z_{in}(OL)*T$) -> voltage input
 - Large Z_{out} ($= Z_{out}(OL)*T$) -> current output
 - Transconductance
 - Ex : common emitter with emitter degeneration

 

 
- Calculating $\beta = E/X_{out} = Z_d/(Z_d+Z_f)$



- Electronics noise dominated by series noise e_n
 - Large detector capacitance
 - For voltage preamp and load resistor R_L ,
 - Output rms noise $V_n^2 = (e_n^2 + 4kTR_s) G^2 \pi/2 * BW_{-3dB}$
 - Typical values : $R_s = 50 \Omega$, $e_n = 1 \text{ nV}/\sqrt{\text{Hz}}$ $V_n = 1 \text{ mV}$ for $G = 10$, $BW = 1 \text{ GHz}$
 - For current sensitive preamps, possible noise peaking due to C_d

- Jitter

 - Part due to electronics noise :
- $\sigma_t = \sigma_v / (dV/dt)$
- Minimized by increasing BW




$$\sigma_j = \frac{\sigma_e}{\left(\frac{dV}{dt}\right)_{\text{threshold}}}$$

- Open loop configurations : current conveyors, RF amplifiers
- Usually designed at transistor level MOS or SiGe


- **Current conveyors**

 - **Small Z_{in}** : current sensitive input
- **Large Z_{out}** : current driven output
- Unity gain current conveyor
- E.g. : (super) common-base configuration
- Low input impedance : $R_{in} = 1/g_m$
- Transimpedance : R_c
- Bandwidth : $1/2\pi R_c C_d > 1 \text{ GHz}$





- **RF amplifiers**

 - **Large Z_{in}** : voltage sensitive input
- **Large Z_{out}** : current driven output
- Current conversion with resistor R_S
- E.g. common-emitter configuration
- Transimpedance : $-g_m R_c R_S$
- Bandwidth : $1/2\pi R_S C_t$



  Examples of pulse shapes

- Short pulse : $Q=16$ fC, $C_d=100$ pF, $L=0-10$ nH, $R_L=5-50$ Ω
- Smaller signals with SiPM (large Cd) \sim mV/p.e.
- Sensitivity to parasitic inductance
- Choice of R_L : decay time, stability
- Convolve with current shape... (here delta impulse)



- Experimental measurements on SiGe test structures

Testboard #3	RF (Common Emitter)	Common Base	Super Common Base
<i>With 100pf/50 Ohm injector (SiPM emulation)</i>		Vb_cb : 400 #DAC	Vb_scb : 1023 #DAC
Noise floor (pedestal)	185-187 #DAC / 1.196V	216-224 #DAC / 1.259V	340-342 #DAC / 1.514V
Signal value @ 10pe	235 #DAC / 1.300V	137 #DAC / 1.085V	115 #DAC / 1.038V
Signal amplitude @ 10pe (signal minus pedestal)	50 #DAC / 110mV	83 #DAC / 174mV	226 #DAC / 476mV
Gain (mV/pe)	10.4mV/pe (5 #DAC/pe)	17.4mV (8.3 #DAC)	47.6mV/pe (22.6 #DAC/pe)
Jitter - threshold 1 pe @10pe	13ps RMS	6ps RMS	8ps RMS
Jitter - threshold 3 pe @10pe	8ps RMS	6ps RMS	8ps RMS
<i>With 100nF DC block (for voltage gain & BW meas.)</i>	18mV injection	18mV injection	7mV injection
Signal Value	267 #DAC / 1.371V	41 #DAC / 0.884V	192 #DAC / 1.2V
Signal amplitude (signal minus pedestal)	81 #DAC / 175mV	179 #DAC / 375mV	150 #DAC / 320mV
Voltage gain (before 50 ohm bridge => factor of 0.5)	4.86 V/V	10.4 V/V	22.5 V/V
Bandwidth, after discriminator (Δt 10% T50% meas.)	Δt : 150ps / 660MHz	Δt : 360ps / 280MHz	Δt : 400ps / 250MHz

With 1pe-=160 fC



- 16 channels, prototyping ASIC
- 16 discriminator output, 16 charge output, MUX charge output, Trigger OR
- Power consumption **3.5mW/ch**
- RF, common emitter SiGe fast amplifier, DC coupled to detector, **GBWP 10GHz@1mW**
- Fast SiGe discriminator, **BW 1GHz @ 1.5mW**
- Low noise amp+shaper for charge measurement
 - Adjustable peaking time (25ns, 50ns, 75ns, 100ns)
 - Low gain for high swing (up to 3000pe) : 360uV/pe

PETIROC2



- **32 channels**
- **Internal ADC/TDC**



weeroc

 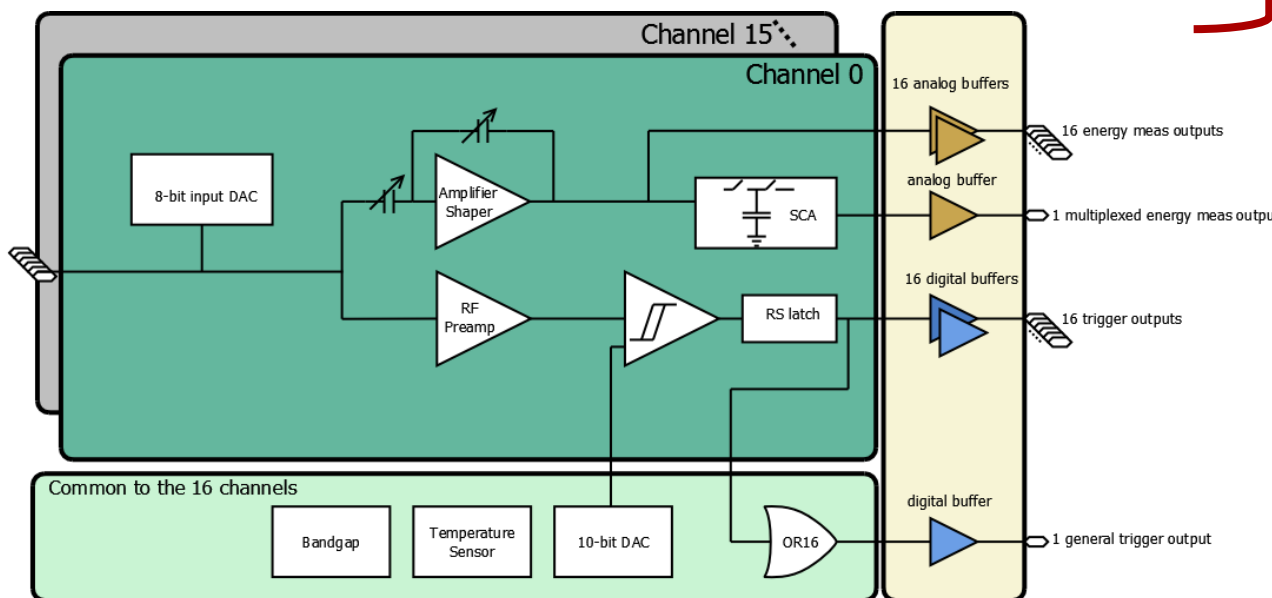

 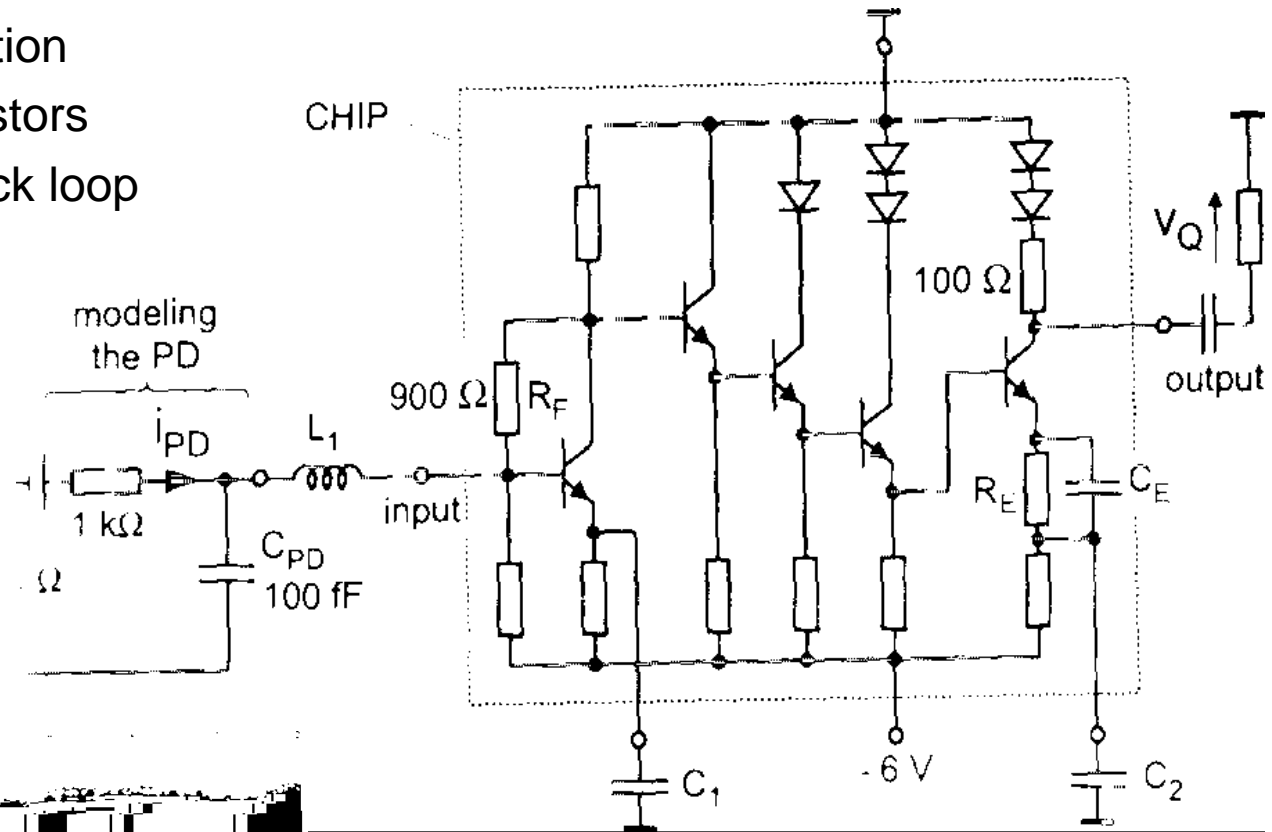
- « Simple architecture »
 - CE + CC configuration
 - SiGe bipolar transistors
 - CC outside feedback loop
 - « pole splitting »



- Strong push for high speed front-end > GHz
 - Essential for timing measurements
 - Several configurations to get GBW > 10 GHz
 - Optimum use of SiGe bipolar transistors
- Voltage sensitive front-end
 - Easiest : 50Ω termination, many commercial amplifiers (mini circuit...)
 - Beware of power dissipation
 - Easy multi-gain (time and charge)
- Current sensitive front-end
 - Potentially lower noise, lower input impedance
 - Largest GBW product
- In all cases, importance of reducing stray inductance

Summary of transistor level design

 
- Performant design is at transistor level
- Simple models
 - hybrid π model
 - Similar for bipolar and MOS
 - Essential for design



High frequency hybrid model of bipolar

Three basic configurations


 
- Common emitter (CE) = V to I (transconductance)
- Common collector (CC) = V to V (voltage buffer)
- Common base (BC) = I to I (current conveyor)




The *Art* of electronics design

- Numerous « composites »
 - Darlington, Paraphase, Cascode, Mirrors...

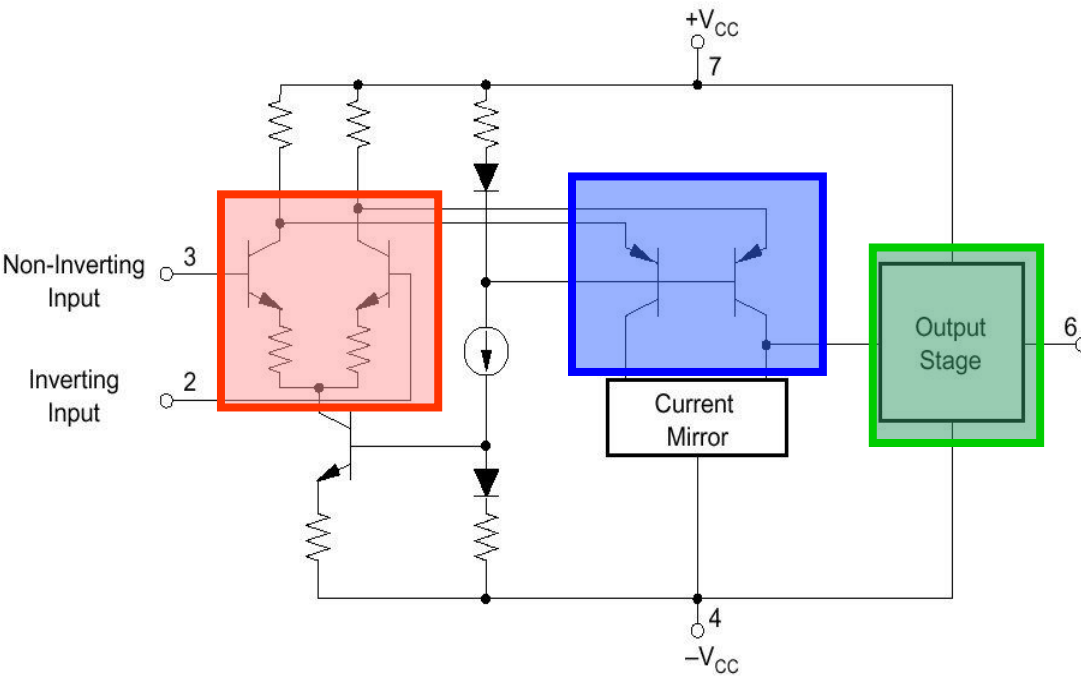 - From the schematic of principle
 - Using of a fast opamp (OP620)
 - Removing unnecessary components...
 - Similar to the traditional schematic «Radeka 68 »
 - Optimising transistors and currents




Schematic of a OP620 opamp ©BurrBrown

 

Charge preamp ©Radeka 68

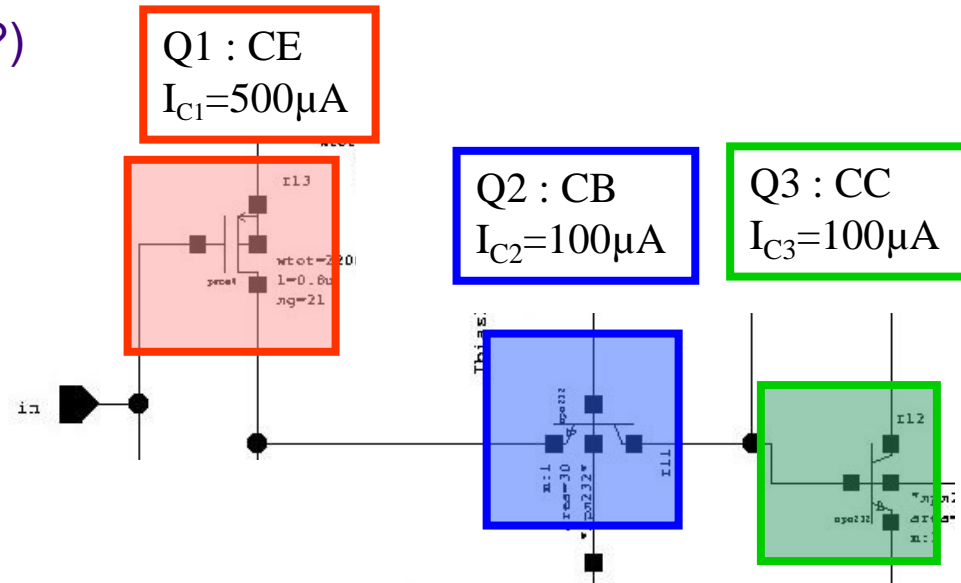Example : designing a charge preamp (2)


- Simplified schematic
- Optimising components
 - What transistors (PMOS, NPN ?)
 - What bias current ?
 - What transistor size ?
 - What is the noise contribution of each component ?
 - how to minimize it ?
 - What parameters determine the stability ?
 - What is the saturation behaviour
 - How vary signal and noise with input capacitance ?
 - How to maximise the output voltage swing ?
 - What is the sensitivity to power supplies, temperature...



Simplified schematic of Charge preamp

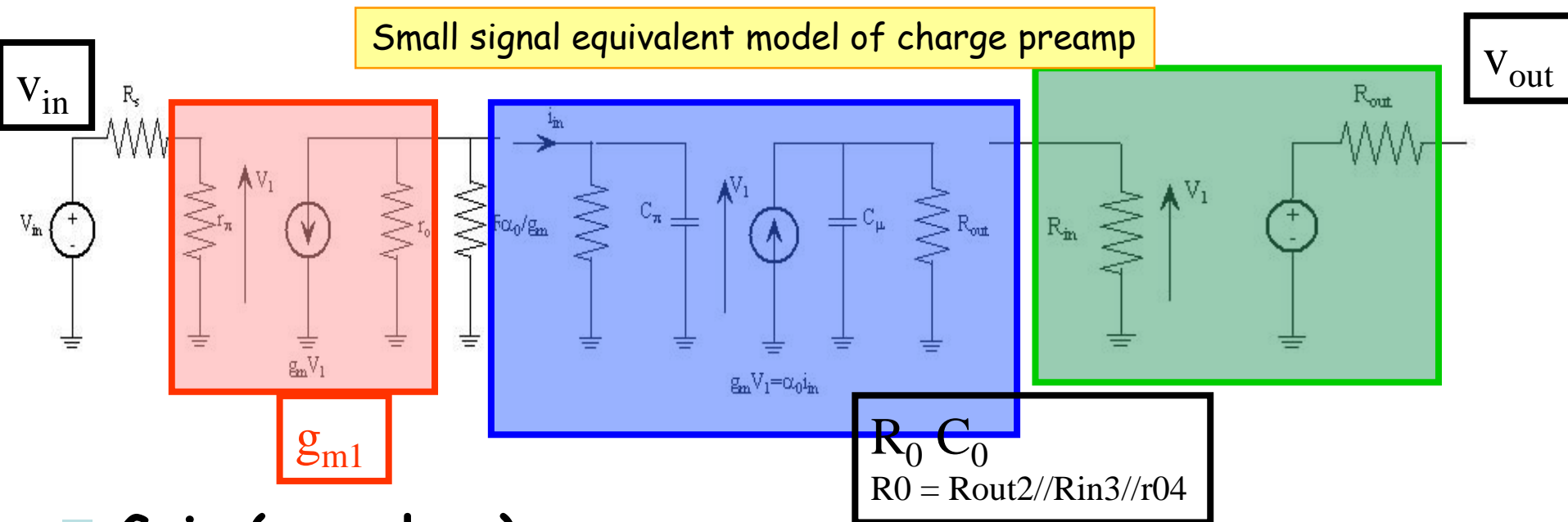Example : designing a charge preamp (3)

- Small signal equivalent model
 - Transistors are replaced by hybrid π model
 - Allows to calculate open loop gain




■ Gain (open loop) :


$$v_{out}/v_{in} = -g_{m1} R_0 / (1 + j\omega R_0 C_0)$$

- Ex : $g_{m1} = 20 \text{ mA/V}$, $R_0 = 500 \text{ k}\Omega$, $C_0 = 1 \text{ pF} \Rightarrow G_0 = 10^4$ $\omega_0 = 210^6$ $G_0 \omega_0 = 2 \cdot 10^{10} = 3 \text{ GHz}!$

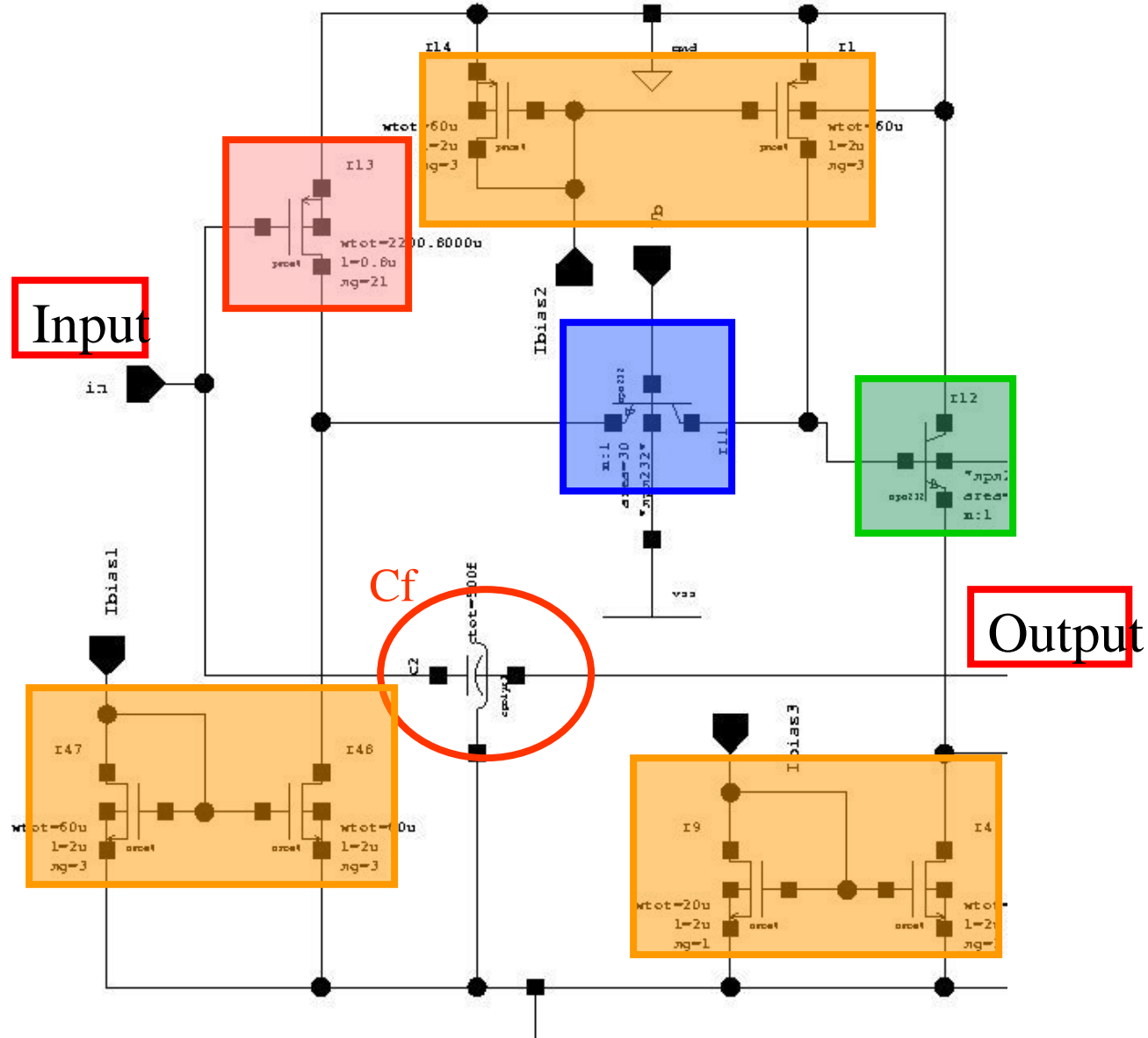
- Complete schematic
 - Adding bias elements



 - Complete simulation
 - Checking hand calculations against 2nd order effects
 - Testing extreme process parameters (« corner simulations »)
 - Testing robustness (to power supplies, temperature...)




Simulated open loop gain

 


Saturation behaviour


- Layout
 - Each component is drawn
 - They are interconnected by metal layers
- Checks
 - DRC : checking drawing rules (isolation, minimal dimensions...)
 - ERC : extracting the corresponding electrical schematic
 - LVS (layout vs schematic) : comparing extracted schematic and original design
 - Simulating extracted schematic with parasitic elements
- Generating GDS2 file
 - Fabrication masks : « reticule »

 


 Charge preamp in 65nm
Clicpix P. Valerio (CERN 2013)



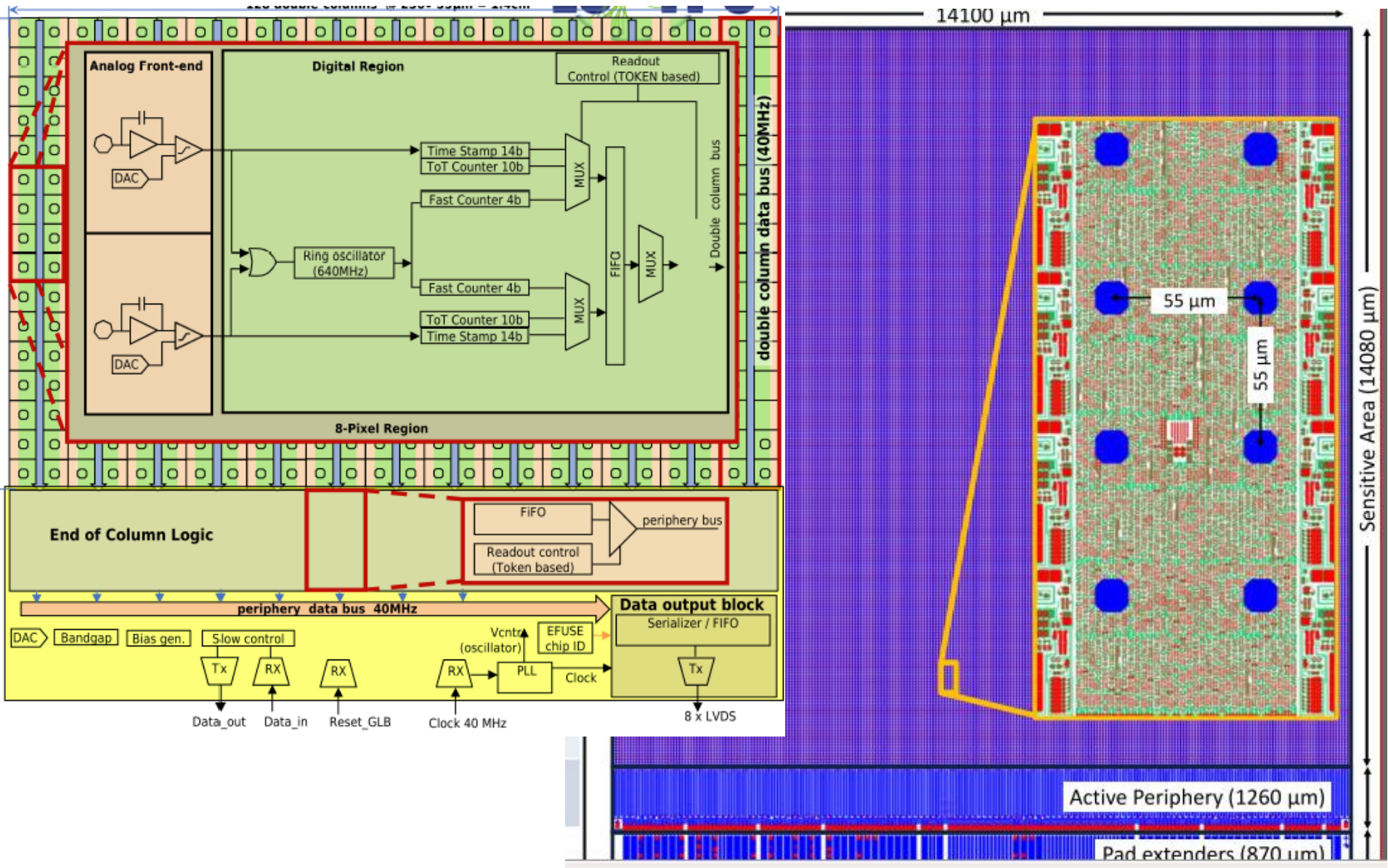From preamp to chip : Timepix 3 [CERN]...



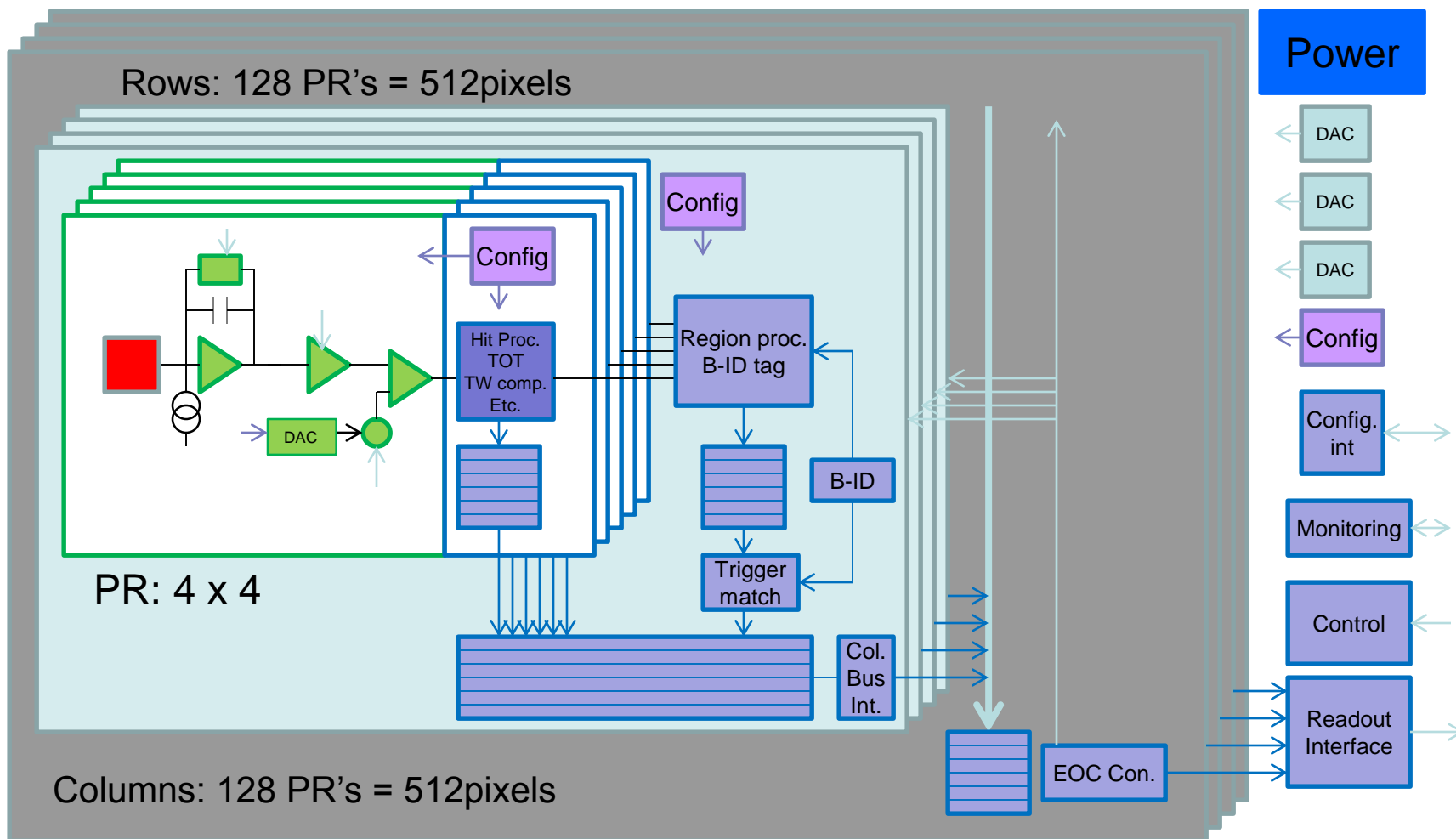

- Pixels: $4 \times 4 \times \sim 128 \times \sim 128 = \sim 256k$ (262144)
- Chip size = $\sim 50\mu m \times 4 \times 128 = \sim 2.6cm \times \sim 3cm$ (Yield maximization required)
- Obviously resembles LHCb/ALICE, FEI4, LHCb Velopix and other high rate pixels
 - And any other data driven (HEP) chip/system: System on a chip


```
process(Rstb, Clk)
begin
  if Rstb ='0' then
    Q <= '0';
  elsif rising_edge Clk then
    Q <= D;
  end if;
end process;
```

Architecture Design

High Level Synthesis

Synthesis

Verification



Placement

Extraction and Timing Verification

Routing


GDSII

Manufacturing

  


ASIC specific flow for digital routing

Skiroc2 power planning

 

Skiroc2 clock tree

 

IO Pad Placement

Power planning
(Stripes & rings)

Global Placement

DFT (scan chains)

Clock Tree Synthesis


Global Routing

LVS / DRC
Specific Analysis (IR, Antennas)


GDS2

(M1, M2, M3) =
(blue, red, green)

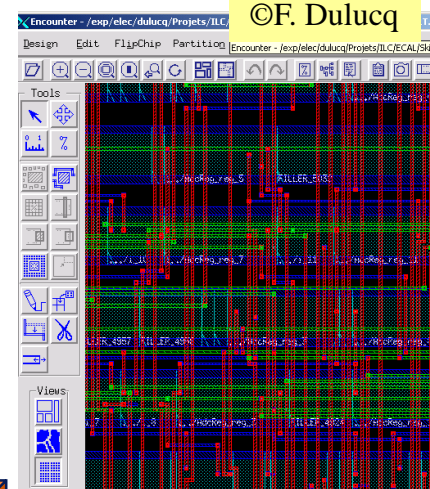Extraction and
Delay Calc. Timing
Verification




(a) After completion

 

Antennas fixing

(b) Under construction

 



Pentium4



Parisroc2 IR drop Analysis
(red = drop > 5mV)

MIN PVT (1.6 ; 3.6V ; -50°C)

MAX PVT (1.4 ; 3V ; 125°C)

 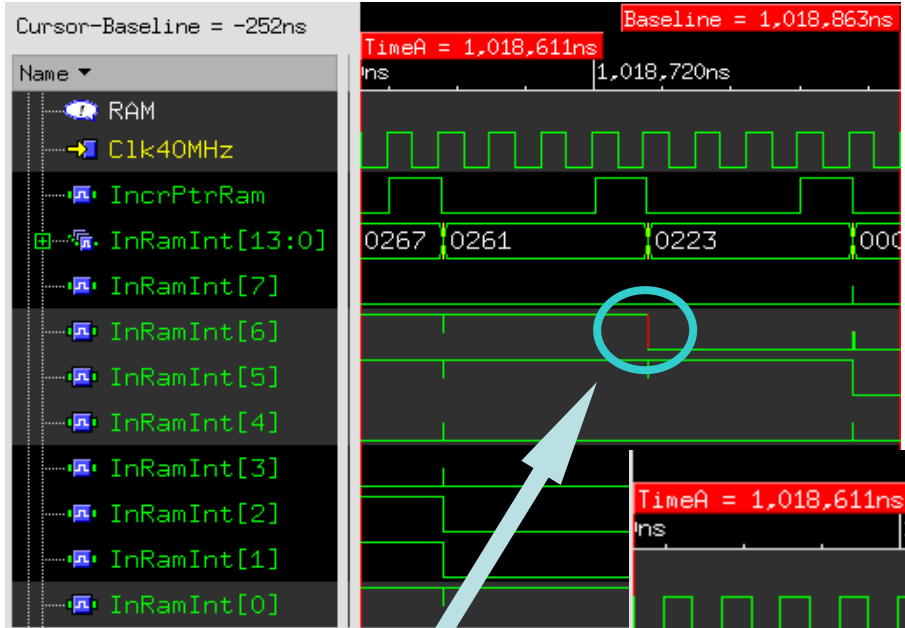


1 violations

4 violations

TYP PVT (1 ; 3.3V ; 25°C)


0 violations

 


- Coexistence analog-digital
 - Capacitive, inductive and common-impedance couplings
 - A full lecture !
 - A good summary : there is no such thing as « ground », pay attention to current return



- ASICs : Application Specific Integrated Circuits
 - Access to foundries through **multiproject runs** (MPW)
 - Reduced development costs : 600-1000 €/mm² compared to dedicated runs (50-200 k€)
 - **Full custom layout, at transistor level**
 - mostly **CMOS & BiCMOS**
- Very widespread in high Energy Physics
 - High level of integration, limited essentially by power dissipation and parasitic couplings (EMC)
 - Better **performance** : reduction of parasitics
 - Better **reliability** (less connections)
 - But **longer developpement time**
- **Trends** :
 - Evolution of technologies (see next slides)
 - Low power design

 

MAROC : 64ch
MaPMT readout chip

 

300 mm wafer

- From Sand to ICs...

RETICLE
(Pattern with 0.7 micron apertures ie 4 X 0.18)

Lithography.

UV Light


Silicon Wafer

Light Sensitive Coating.


Multiple Layers.
>350 process steps.

CREATING > 125 million TRANSISTORS ON EACH MICROPROCESSOR;
WITH FEATURES 1/2000th THE WIDTH OF A HUMAN HAIR.


The diagram illustrates the lithography process. It starts with a Silicon Wafer (black circle) which is coated with a Light Sensitive Coating (green oval). A Reticle (a pattern with 0.7 micron apertures) is used in the Lithography step, where UV Light is projected through it onto the coating. This process is repeated for multiple layers, involving more than 350 process steps. The final result is a microprocessor with over 125 million transistors and features that are 1/2000th the width of a human hair. A photograph on the right shows a technician in a cleanroom environment handling a large silicon wafer.

 

 
SiGe Bipolar in 0.35μm monolithic process




First planar IC (1961)

 



5 μm MOSFET (1985)

 



32 nm MOSFET (2010)

 

  - Reduction of dimensions
 - « Quasi-constant voltage scaling »
 - Decrease of W, L, t_{ox}
 - (partial) decrease of V_{DD} et V_{Th}
- Improvement of speed as $1/L^2$
 - Improvement of transconductance as W/L and reduction of capacitance as WL
- Power increases as k and power density even worse
 - V_{DD} does not scale as L




  
- Moore's law : number of transistors doubling every ~2 years
- Technology nodes (gate length) *0.7 every 2 years



Processor	4004	8086	i386	Pentium	Pentium 4	Core2	3G Core7
Year	1971	1978	1985	1993	2000	2007	2012
Clock	108 kHz	10 MHz	16 MHz	66 MHz	1.5 GHz	2.4 GHz	2.9 GHz
Technology	10 μm	3 μm	1.5 μm	0.8 μm	0.18 μm	65 nm	22 nm
Nb transistors	2300	29000	275000	3.1M	42M	291M	1.4G
 
<http://www.intel.com/content/www/us/en/history>



 

* Note: The wafer production capacity data are plotted from the SICAS* 4Q data for each year, except 1Q data for 2011. The width of each of the production capacity bars corresponds to the MOS IC production start silicon area for that range of the feature size (y-axis). Data are based upon capacity if fully utilized.

<http://www.itrs.net/Links/2011ITRS/2011Chapters/2011ExecSum.pdf>



Example of prices, prototyping



© K. Troki (CMP)




CMOS	.35 μ	AMS	650 €/mm ²
CMOS opto	.35 μ	AMS	810 €/mm ²
CMOS HV	.35 μ	AMS	1000 €/mm ²
CMOS	130nm	ST	2200 €/mm ²
CMOS	65 nm	ST	7500 €/mm ²
CMOS	40 nm	ST	15000 €/mm ²
SiGe BiCMOS	.35 μ	AMS	890 €/mm ²
SiGe:C BiCMOS	130nm	ST	3500 €/mm ²
SOI	130nm	ST	4000 €/mm ²
SOI	65nm	ST	9500 €/mm ²
Poly-SOI-Metal	MUMPS	MEMSCAP	3700 €/cm ²

CMP annual users meeting, January 20th 2011, PARIS




http://cmp.imag.fr/aboutus/slides/Slides2011/02_Runs_2011.pdf

© R. Hermel

   - Faster bipolar transistors for RF telecom
 - Better mobility and FT
 - Better current gain (beta)
 - Better Early voltage
 - Interesting improvement at low T
 - Compact CMOS (0.25 or 0.35µm) for mixed-s



   
- BJT : best g_m/I ratio ($1/U_T$)
 - Large transconductance with small devices
- Speed goes as $F_T = g_m/2\pi C$
 - $C \sim 10$ fF g_m typ mA/V
 - $F_T \sim 60$ GHz for SiGe $0.35\mu\text{m}$
 - Interesting for fast preamps
- Not forgetting 100V Early voltage and **matching** performance ($A \sim \text{mV} \cdot \mu\text{m}$)
- $V_{BE} = V_T \ln(I_C/I_S)$
- Large swing : $V_{CEsat} \sim 3 U_T$



Intel CMOS Transistor Architecture Evolution in the Last Decade


.13 μm and before

Traditional

 


90nm/65 nm

Strained Silicon

 


45 nm/32 nm

 High k/Metal Gate +
Strained Silicon

CMOS scaling has evolved from classical dimensional scaling to modern scaling with innovations in structures and materials




32 nm RF CMOS Technology

 






- **TM1 Inductor:** high Q and density
- **Passives:**
 - Precision Resistor
 - High Q Inductor
 - High Density Decap



   - **HV PA Transistor**
- **RF Transistor:** Templates/Modeling




     - **Transistor:**
 - Logic, low power, I/O
 - JFET, BJT
- **Well:** Triple Well/Deep Nwell
- **Substrate:** High Resistivity




Basic 32 nm CMOS technology is expanded with many more mixed signals/RF features to meet RF SoC requirements

RF CMOS Technology Performance Metrics

 

RF Devices	RF Circuits	Key Device Characteristics
Logic Transistor	MAC/BB, ADC, DAC	I_{dsat} , I_{dlin} , V_t , I_{off}
Analog Transistor	ADC, DAC, MAC/BB	G_m , R_{out} , Matching, Linearity, Noise, NF_{min}
RF Transistor	PA, Mixer, T/R Switch	f_T , f_{max} , $1/f$ Noise, NF_{min}
PA Transistors	PA	R_{on} , Linearity, f_T , f_{MAX} , Efficiency, Breakdown V ,
Precision Resistors	ADC, DAC, BB Filter, others	R , $\sigma R/R$, Matching
Linear Capacitors	PLL, VCO	C , Q , Matching
Varactors	PLL, VCO	Tuning Ratio, Q , KV_{CO} ,
Inductor/Transformer/Balun	PA, LNA, Mixer	L , Q

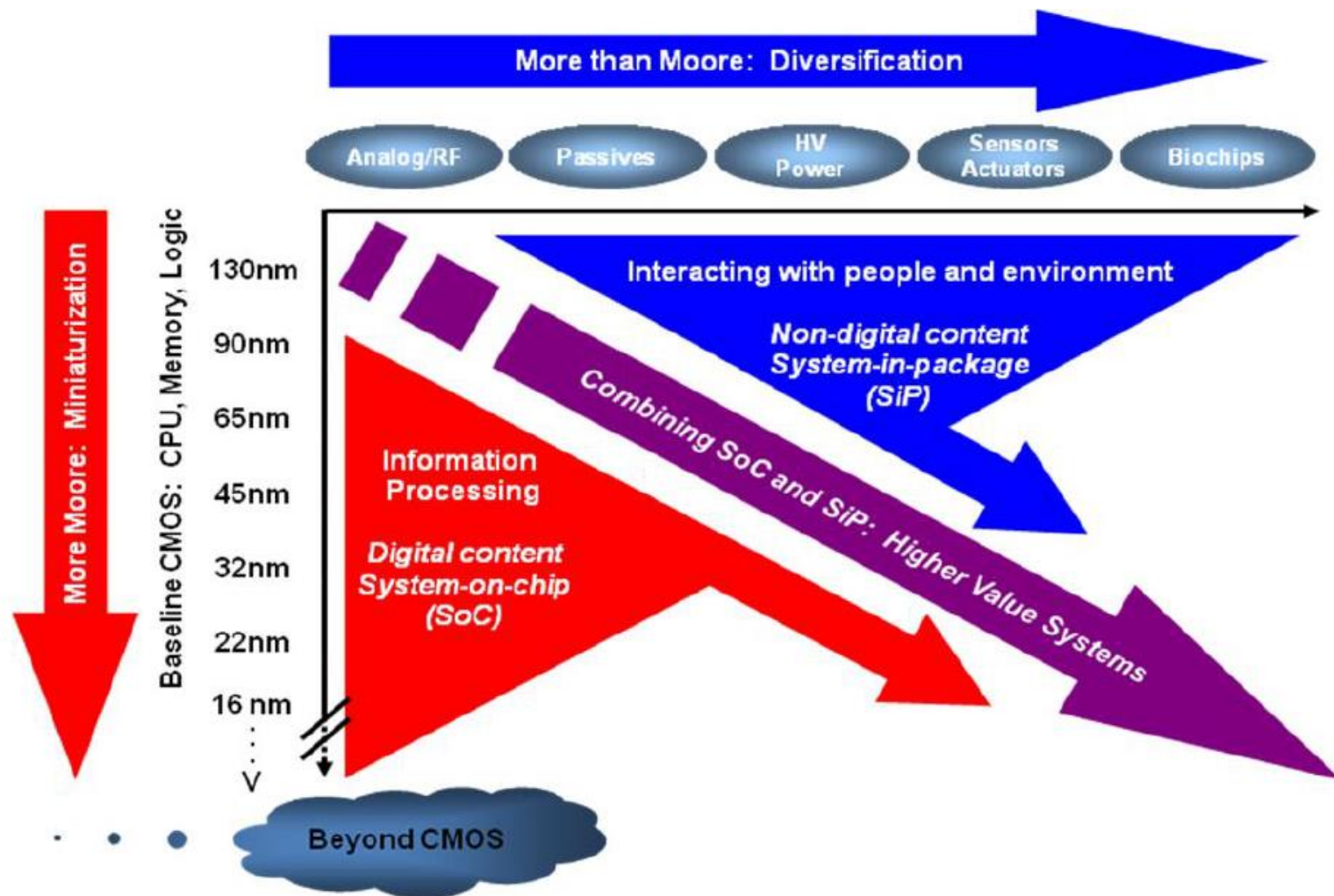What are the impacts of CMOS scaling on these metrics ?




Generic MOSFET scaling trends



Novel materials and architectures





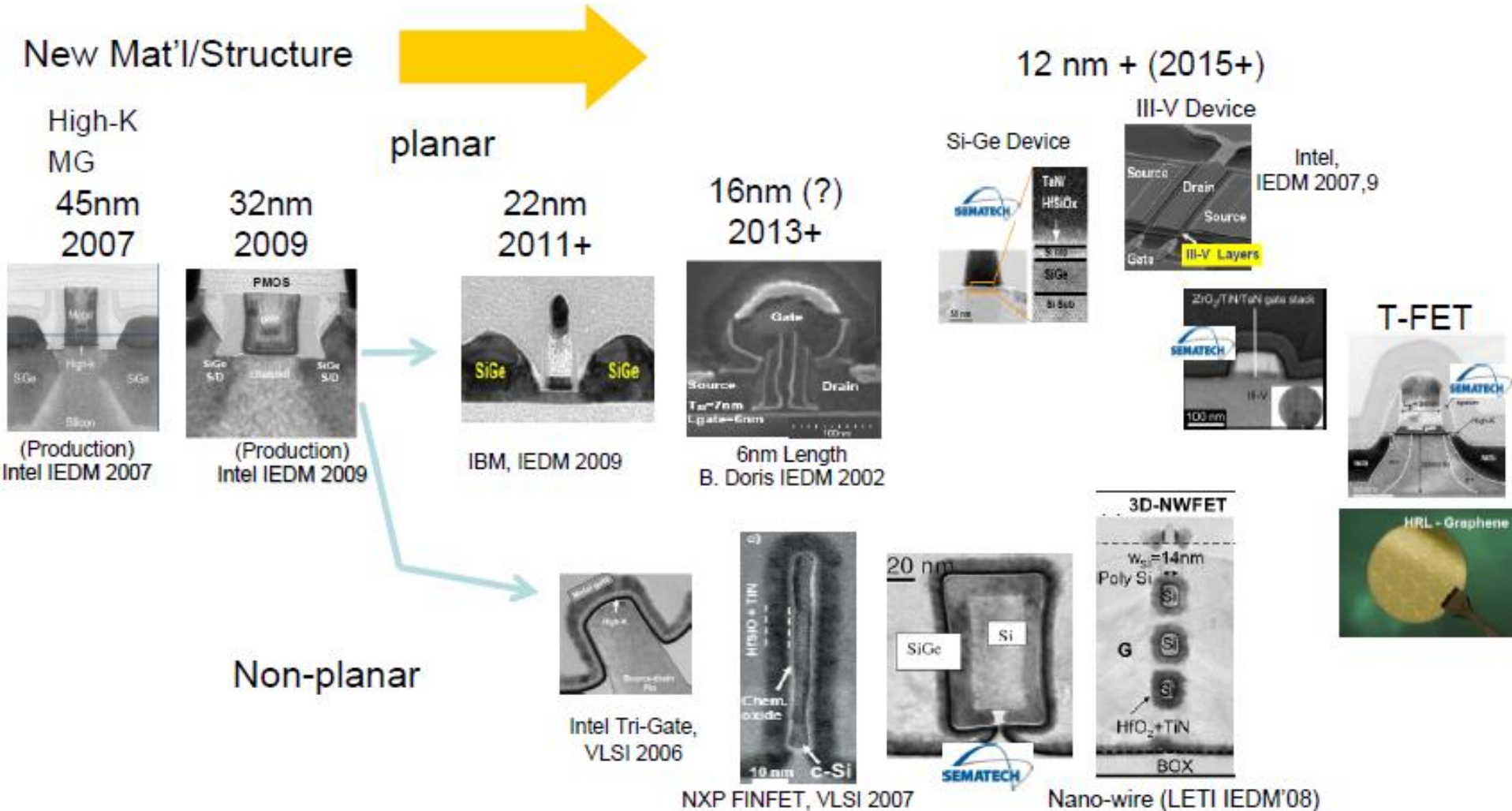
http://www.sematech.org/meetings/archives/symposia/9027/pres/Session%202/Jammy_Raj.pdf



 
 
- Increasing integration density, mixing technologies
- Wafer thinning to $<50\ \mu\text{m}$
- Minimization of interconnects
- Large industrial market
 - Processors, image sensors...



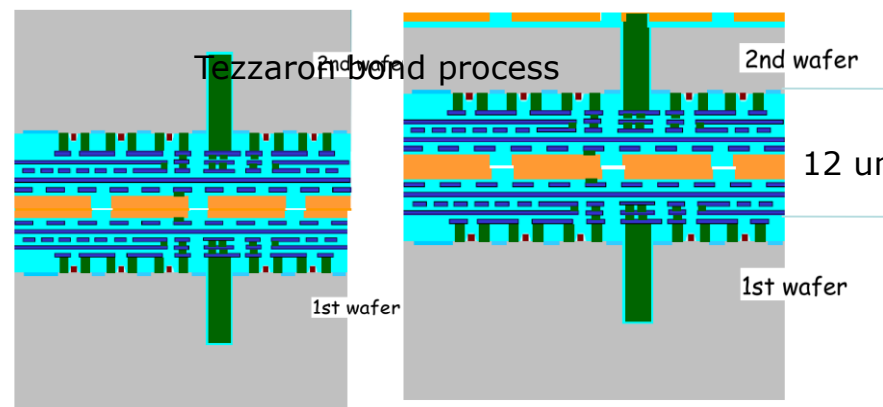 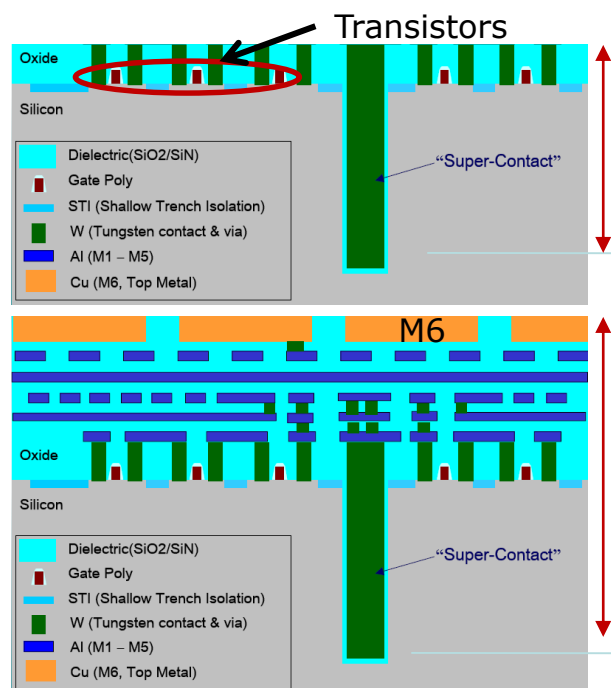
- Access to 3D via Tezzaron
 - 130 nm Global foundry wafers
 - 1 μm vias (Via middle process)
 - Cu-Cu bonding face to face



© R. Yarema (FNAL)

 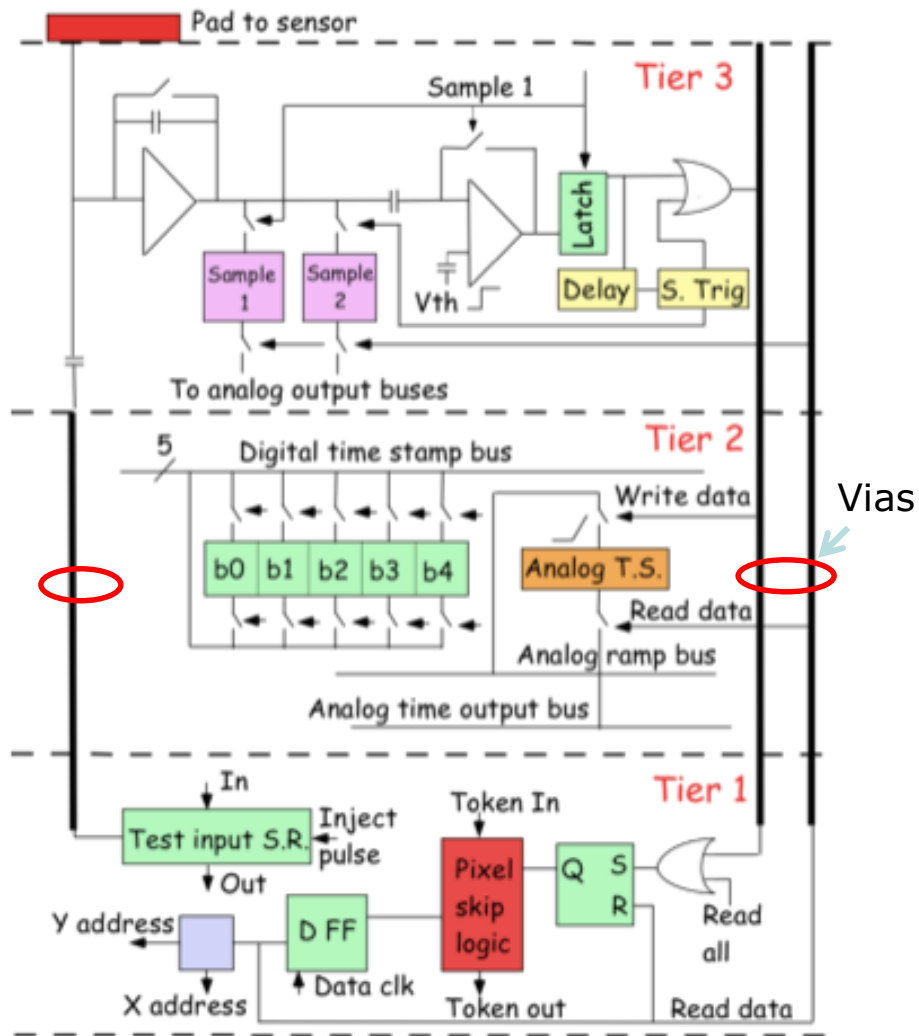

VIP1 3D chip by FNAL

 

Medipix1 (1998)

*1 μ m SACMOS, 64x64 pixels, 170x170 μ m²
PC / Frame based readout*

Medipix2 (2001)

*0.25 μ m CMOS, 256x256 pixels, 55x55 μ m²
PC / Frame based readout*

Timepix (2006)

*0.25 μ m CMOS, 256x256 pixels, 55x55 μ m²
PC, ToT, ToA / Frame based readout*

Medipix3 (2009)

*0.13 μ m CMOS, 256x256 pixels, 55x55 μ m²
PC / Frame based readout
Event by event charge reconstruction and allocation*

Dosepix (2011)

*0.13 μ m CMOS, 16x16 pixels, 220x220 μ m²
ToT, PC / Rolling shutter (programmable column readout)
Event by event binning of energy spectra (16 digital thrs)*

Timepix3 (2013)

*0.13 μ m CMOS, 256x256 pixels, 55x55 μ m²
PC; ToT, ToA (simultaneous)/ Data driven readout*

Velopix

*0.13 μ m CMOS, 256x256 pixels, 55x55 μ m²,
ToA, Binary/ToT (TBD), Data driven readout*

Smallpix

*0.13 μ m CMOS, 512x512 pixels, 40x40 μ m² (TBD), TSV compatible
PC, iTOT; ToA, ToT1 (simultaneous)/ Frame based (ZC)*

Clicpix prototype (2013)

*65nm CMOS, 64x64 pixels, 25x25 μ m²
ToA, ToT1 (simultaneous)/ Frame based (ZC)*

- More and more functions are integrated inside chips (ASICs)
- Evolution of technologies make them more and more performant but more and more complex




FADCs

- 8 bits – 3 GS/s – 1.9 W → 24 Gbits/s
- 10 bits – 3 GS/s – 3.6 W → 30 Gbits/s
- 12 bits – 3.6 GS/s – 3.9 W → 43.2 Gbits/s
- 14 bits – 0.4 GS/s – 2.5 W → 5.6 Gbits/s

1.8 GHz!

1/10 k€/ch


24x1.8 Gbits/s

 

PX1500-4:
2 Channel
3 GS/s
8 bits





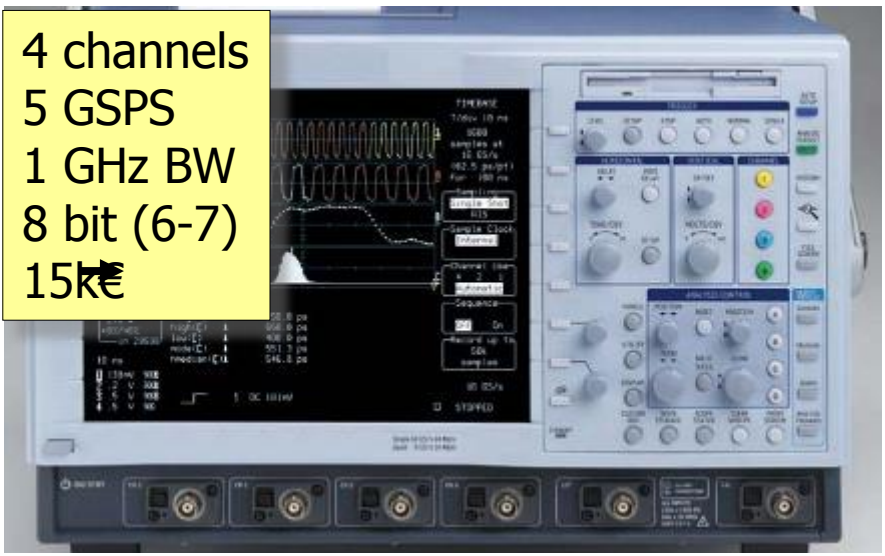4 channels
5 GSPS
1 GHz BW
8 bit (6-7)
15k€




  4 channels
5 GSPS
1 GHz BW
11.5 bits
900€
USB Power






"Time stretcher"
GHz \rightarrow MHz

 

How is timing resolution affected?

 

$$\Delta t = \frac{\Delta u}{U} \cdot \frac{1}{\sqrt{3f_s \cdot f_{3dB}}}$$


Assumes zero aperture jitter
↓


today:
optimized SNR:
next generation:

U	Δu	f_s	f_{3db}	Δt
100 mV	1 mV	2 GSPS	300 MHz	~10 ps
1 V	1 mV	2 GSPS	300 MHz	1 ps
1V	1 mV	10 GSPS	3 GHz	0.1 ps

Design Options

 - CMOS process (typically 0.35 ... 0.13 μm) \rightarrow sampling speed
- Number of channels, sampling depth, differential input
- PLL for frequency stabilization
- Input buffer or passive input
- Analog output or (Wilkinson) ADC
- Internal trigger
- Exact design of sampling cell



 


E. Delagnes
D. Breton
CEA Saclay



H. Frisch et al., Univ. Chicago

STRAW3 LABRADOR3 TARGET

 

- 0.25 μm TSMC
- Many chips for different projects (Belle, Anita, IceCube ...)


www.phys.hawaii.edu/~idlab/

AFTER SAM NECTAR0



- 0.35 μm AMS
- T2K TPC, Antares, Hess2, CTA

matacq.free.fr

 


PSEC1 - PSEC4

Poster 232

- 0.13 μm IBM
- Large Area Picosecond Photo-Detectors Project (LAPPD)


psec.uchicago.edu

DRS1

 

2002

DRS2

 


2004

DRS3



2007

DRS4

 

2008


- 0.25 μm UMC
- Universal chip for many applications
- MEG experiment, MAGIC, Veritas, TOF-PET

Poster 15, 106




Stefan Ritt
R. Dinapoli
PSI, Switzerland

drs.web.psi.ch

 


 C. Tintori (CAEN)
 V. Jordanov *et al.*, NIM **A353**, 261 (1994)


- Trends
 - Reduce dead time
 - increase analog bandwidth
 - Increase depth, give more latency
 - Include high speed low noise preamps (NECTAR...)
- Comments
 - Unbeatable for pulse shape analysis or discrimination
 - Ultra low timing measurements (ps)
 - More power hungry than dedicated front-end (many CdV/dt...), needs careful study for large systems (>> kch)




PET hyperimage project [P. Fisher]

 

SKIROC on ILC ECAL

 

MAROC on ATLAS ALFA luminometers

 


1m² RPC detector for ILC DHCAL [I. Laktineh]


- Move to Silicon Germanium 0.35 μm BiCMOS technology in 2004
- Readout for MaPMT and SiPM for ILC calorimeters and other applications <http://omega.in2p3.fr>
- Very high level of integration : System on Chip (SoC)

Chip	detector	ch	DR (C)
MAROC	PMT	64	2f-50p
SPIROC	SiPM	36	10f-200p
SKIROC	Si	64	0.3f-10p
HARDROC	RPC	64	2f-10p
PARISROC	PM	16	5f-50p
SPACIROC	PMT	64	5f-15p
MICROROC	μMegas	64	0.2f-0.5p
PETIROC	SiPM	32	10f-200p


MAROC3

 


HARDROC2

 


MICROROC1

 


SKIROC2

 


SPIROC2

 

SPACIROC


 


PARISROC2

 


  Example : SPIROC for SiPM

- SPIROC : Silicon Photomultiplier Integrated Readout Chip to read out the analog hadronic calorimeter for CALICE (ILC)
- **Ultra low-power 36-Channel ASIC**
- **Internal input 8-bit DAC** (0-5V) for individual SiPM gain adjustment
- **Energy measurement : 14 bits, 1 pe to 2000 pe**
 - pe/noise ratio : ~11
- **Auto-trigger on MIP or on single photo-electron**
 - Auto-Trigger on 1/3 pe (50fC)
- **Time measurement :**
 - 12-bit Bunch Crossing ID (coarse time)
 - 12-bit step~1 ns TDC->TAC (fine time)
 - Analog memory for time and charge measurement : depth = 16
 - **Low consumption** : ~25 μ W per channel (in power pulsing mode)
 - **4kbytes internal memory and daisy chain readout**




(0.36m)² Tiles + SiPM + SPIROC (144ch)

 


M. Bouchel, S. Callier, F. Dulucq, J. Fleury, J.-J. Jaeger, C. de La Taille, G. Martin-Chassard, and L. Raux, "SPIROC (SiPM integrated read-out chip): Dedicated very front-end electronics for an ILC prototype hadronic calorimeter with SiPM read-out," J. Instrum. 6(01), C01098 (2011).


SPIROC architecture

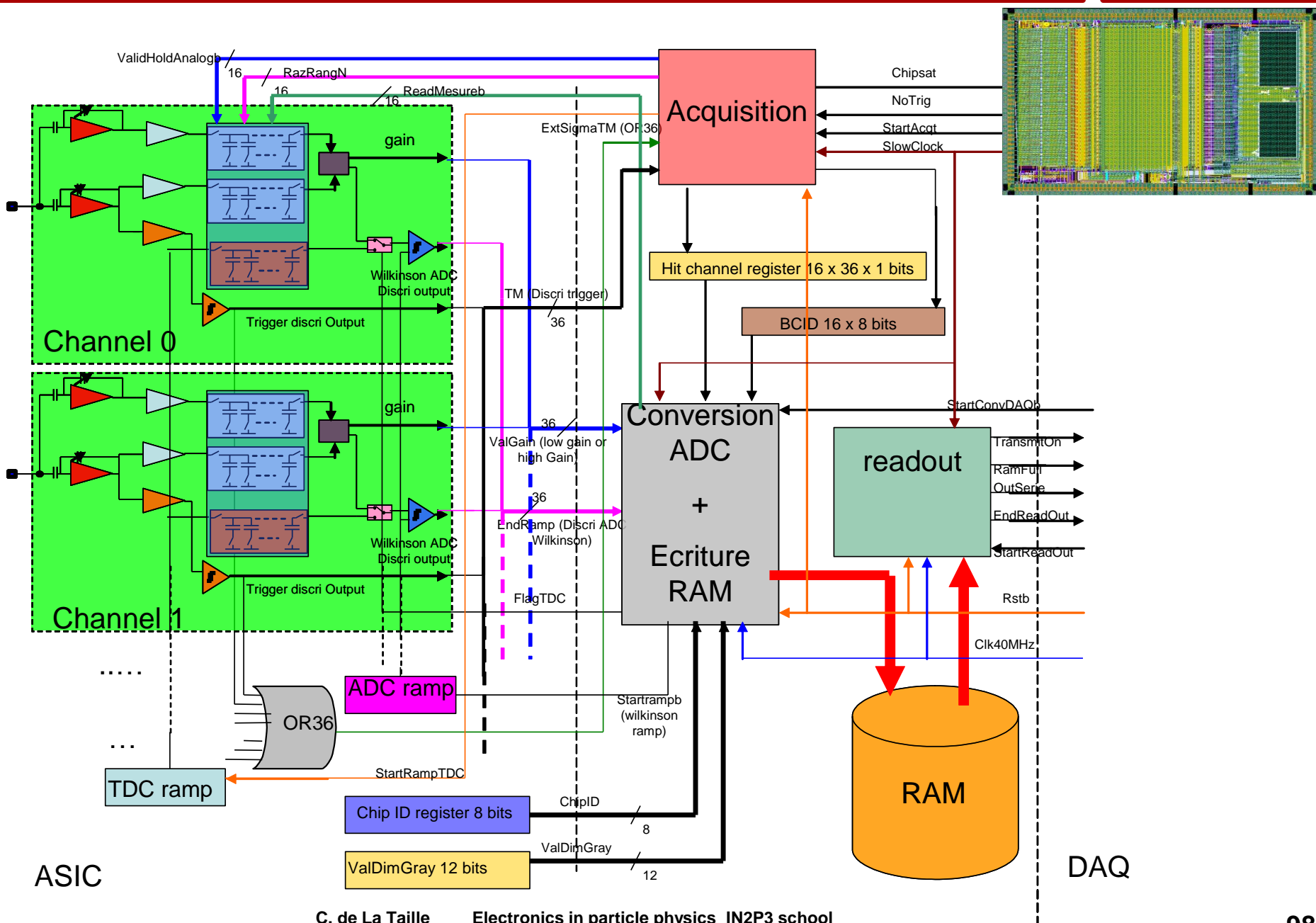

 
36-channel S-curves: trigger efficiency versus threshold (1 LSB = 2 mV)



 
linearity using the auto gain mode and internal ADC





SiPM SPECTRUM with Autotrigger

 

 MIP response in DESY 6 GeV electron testbeam



- PET/MRI projekt
 - P. Fischer et al. Heidelberg, Philips, Aachen, FBK Trento
- 40-channel system on chip for readout of the detectors that generate low voltage (several mV) signals
- Combined high precision time (~ 14 ps) and energy measurements (signal integral = energy)
- Time of flight measurements with energy discrimination
- Particle recognition, by mass measurement
- Medical imaging (SiPM based PET)
- [M. Ritzert...: “Compact SiPM based Detector Module for Time-of-Flight PET/MR” on IEE NPS Real Time Conference

  

- Have fun designing electronics for future detectors !

44

Large collaborations... [V. Radeka]

