

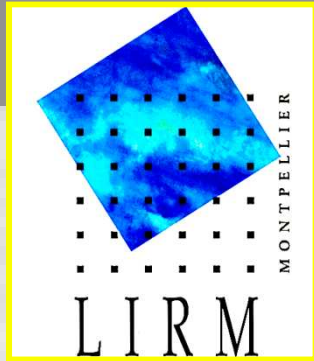

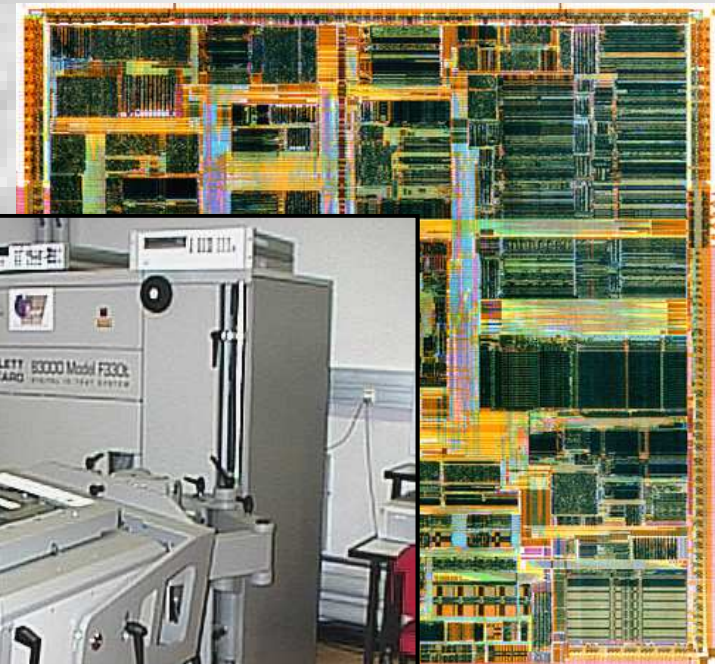
# Fundamentals of Digital & Analog System Testing



*Michel Renovell*

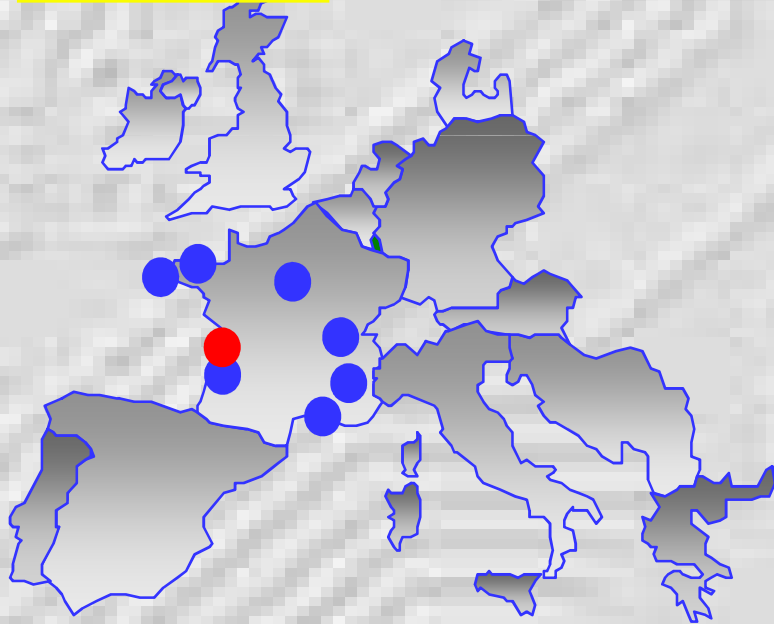

**Ecole Numérique IN2P3**


# Introduction

IN2P3

**Application**




**Test** (preparation)

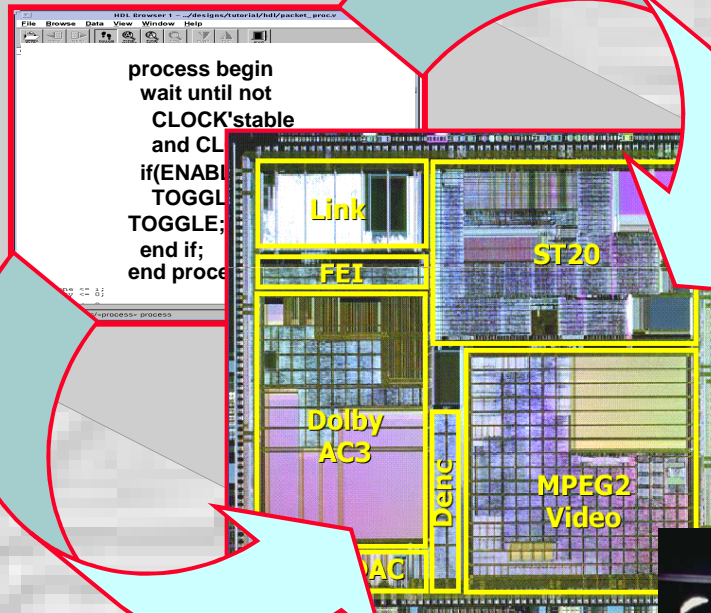

**Technology**

**Design**

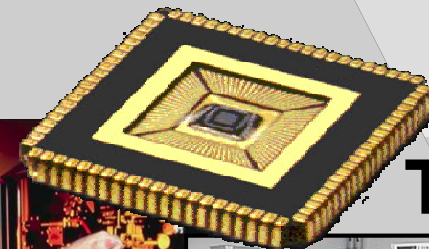

**Test**



# Introduction


```
process begin  
  wait until not  
    CLOCK'stable  
    and CLOCK=1;  
  if(ENABLE='1') then  
    TOGGLE<= not  
    TOGGLE;  
  end if;  
end process;
```

**Design Error**



**Design**

**Layout**

**Manufacturing**

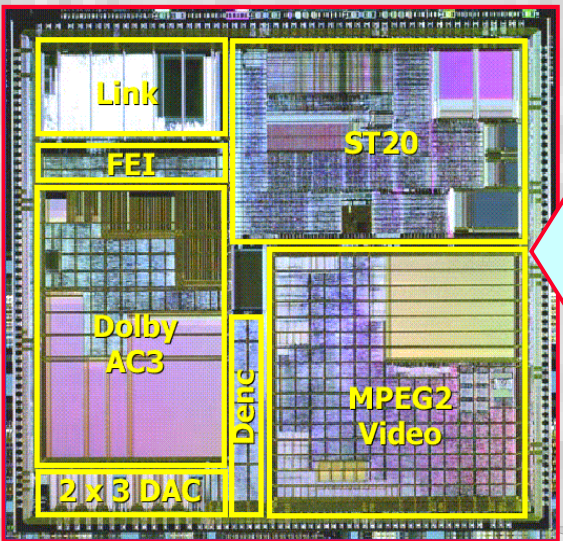



**Deviation & Spot**

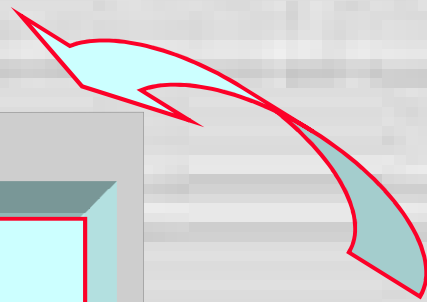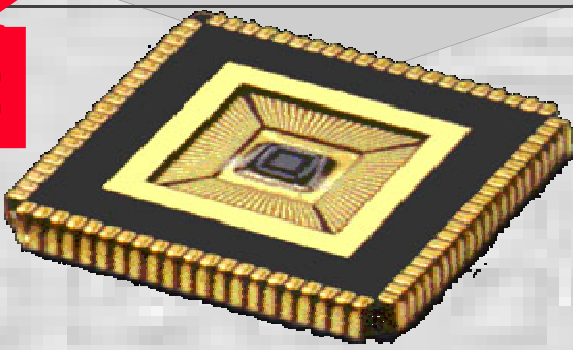

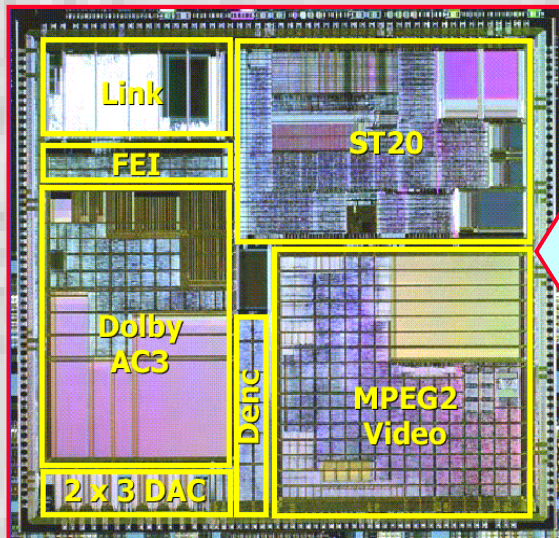
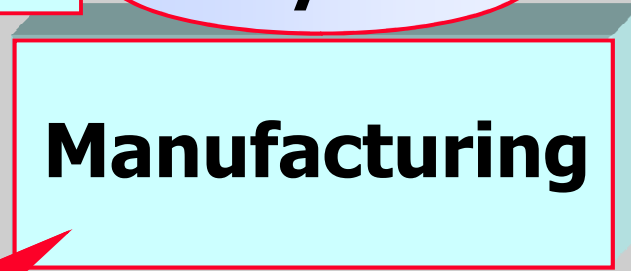
# Introduction

IN2P3

```
process begin
wait until not
CLOCK'stable
and CLOCK=1;
if(ENABLE='1') then
TOGGLE<= not
TOGGLE;
end if;
end process;
```




**Deviation & Spot**

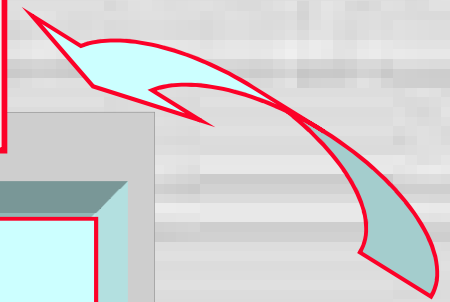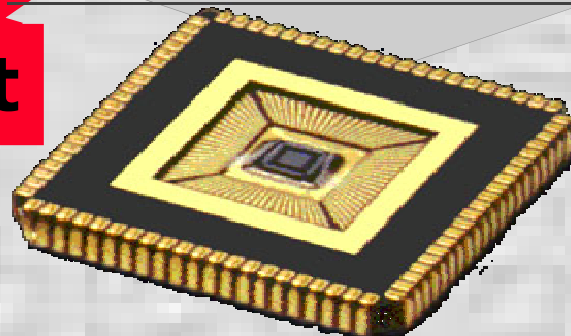

# Introduction

IN2P3

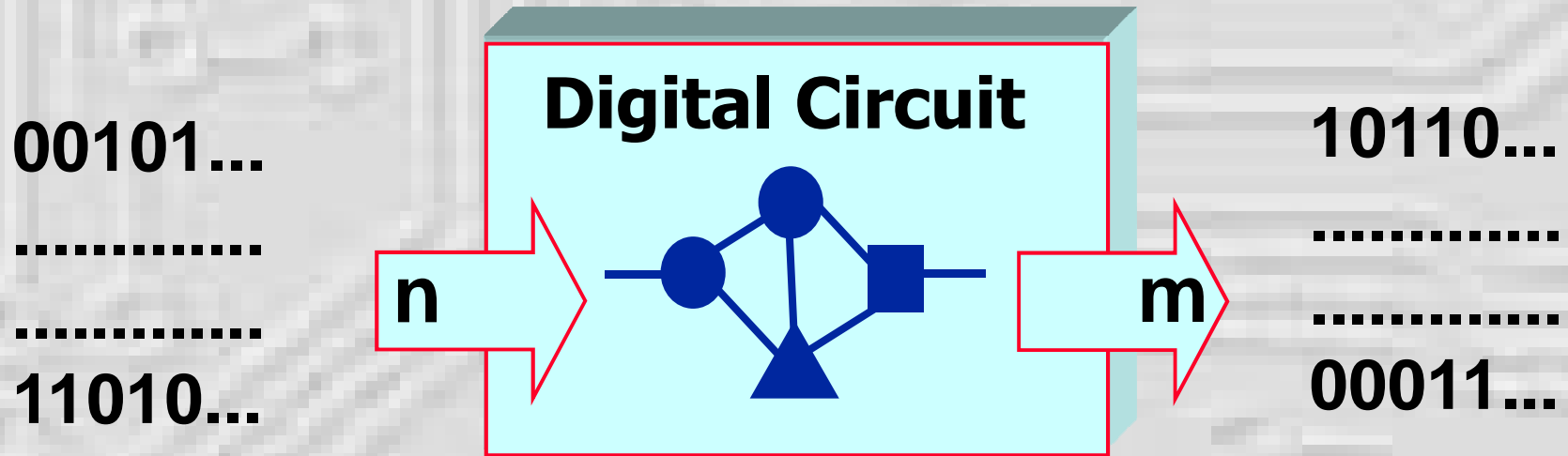


- Boolean Testing
- Test Patterns
- Go/NoGo



# Introduction


IN2P3

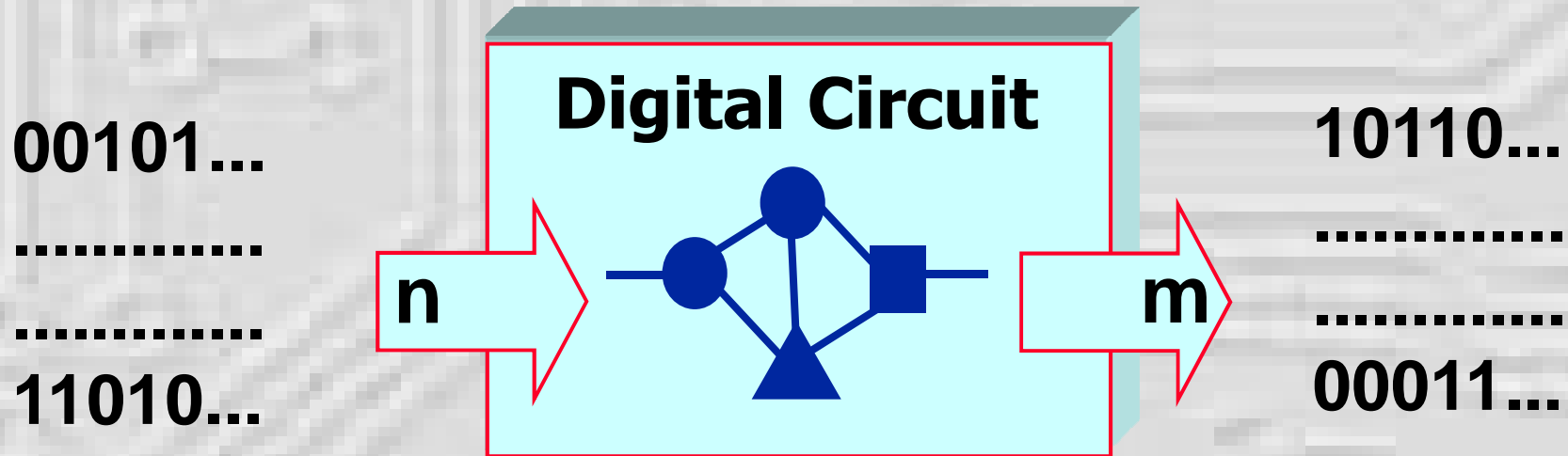

- Exhaustive Testing
- $2^{64}$  patterns
- $10^{20}/100\text{MHz} = 10^{12}\text{s}$
- **=> 5850 years**



- Realistic Test
- 10s / 100MHz
- $10^9$
- $1 / 10^{11}$

# Introduction

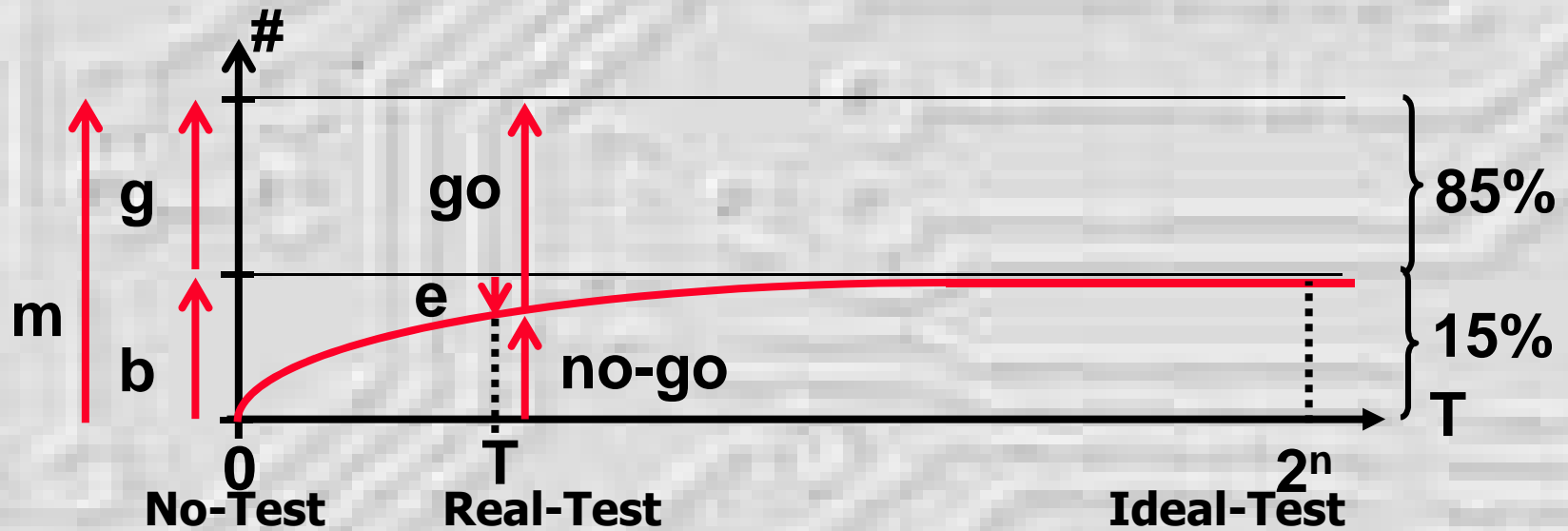


$go \cdot Pg - m \cdot Pm > \text{Margin}$

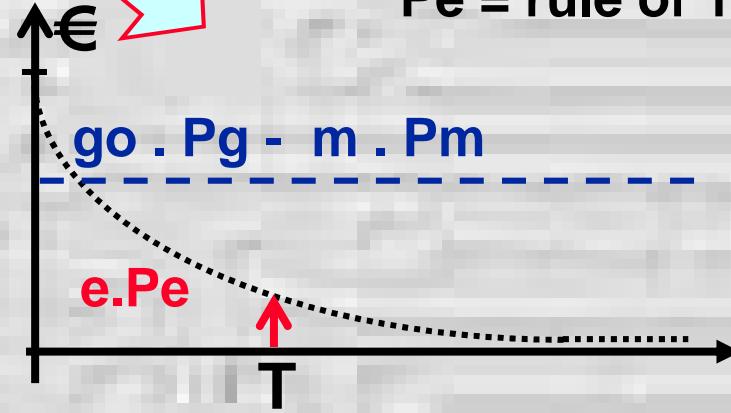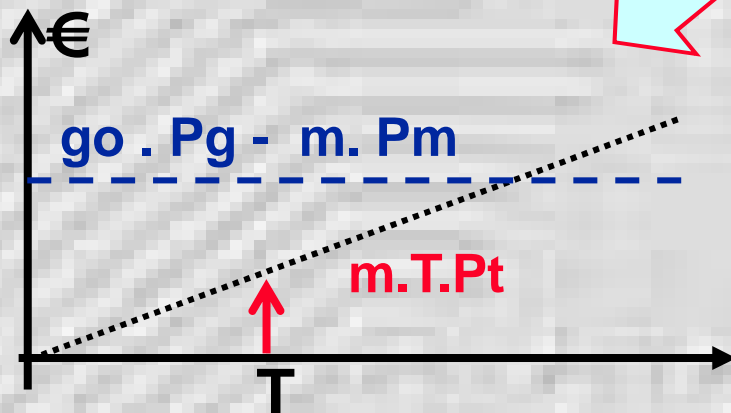Y = 75%  
 e = 500 ppm  
 Pe = rule of 10




# Introduction

IN2P3

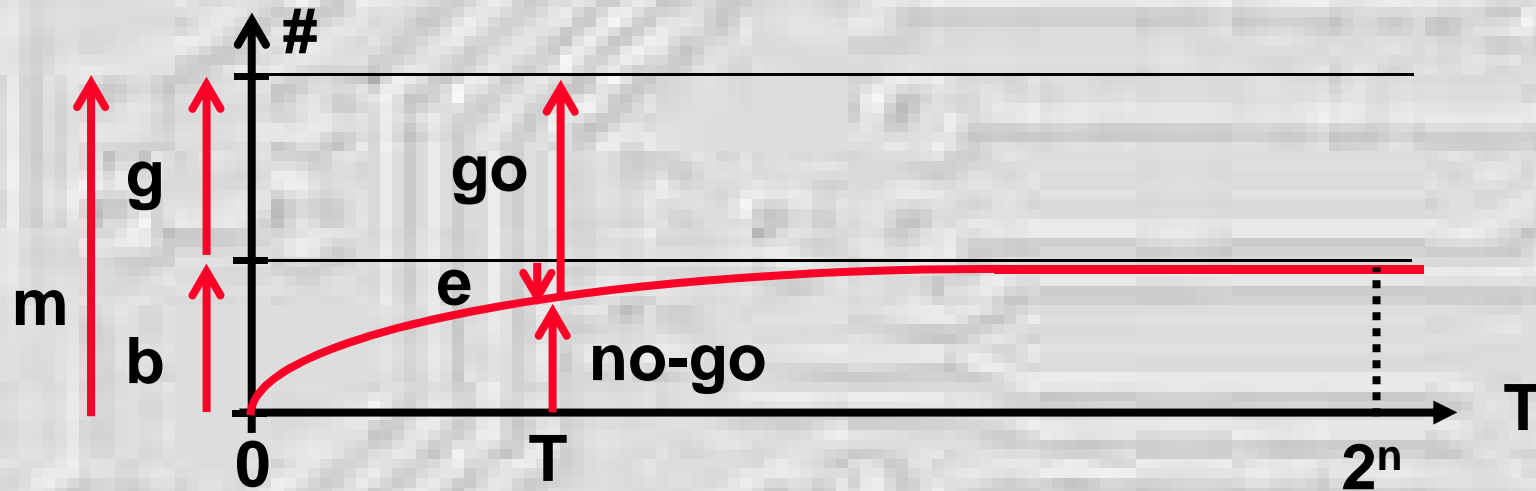

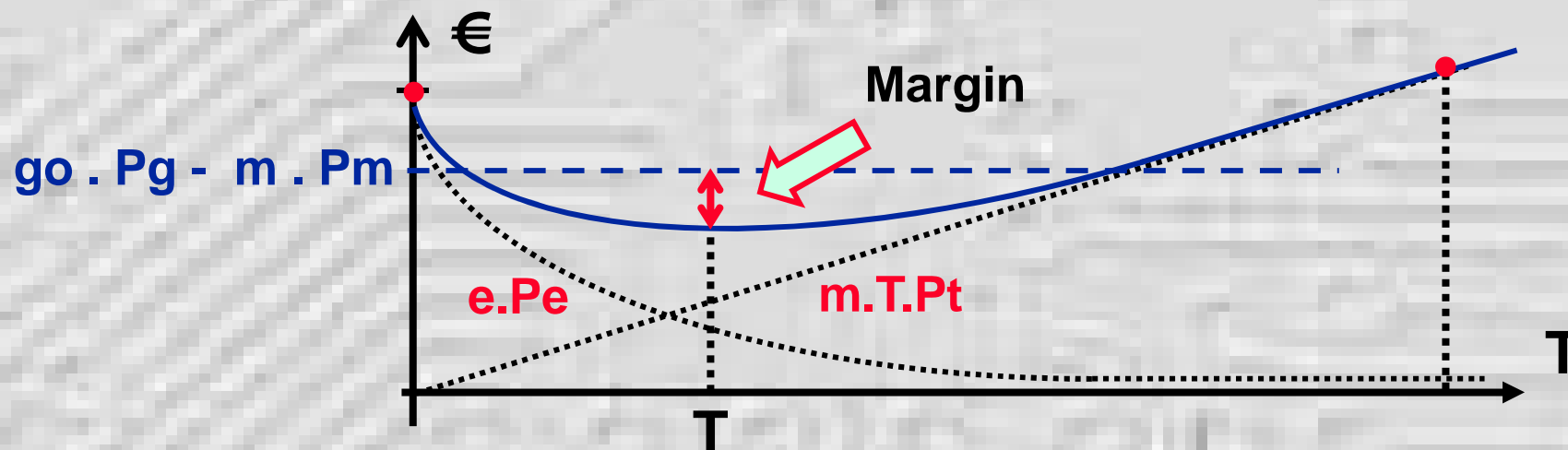
$$go \cdot Pg - m \cdot Pm \geq m \cdot T \cdot Pt + e \cdot Pe$$






# Introduction

IN2P3

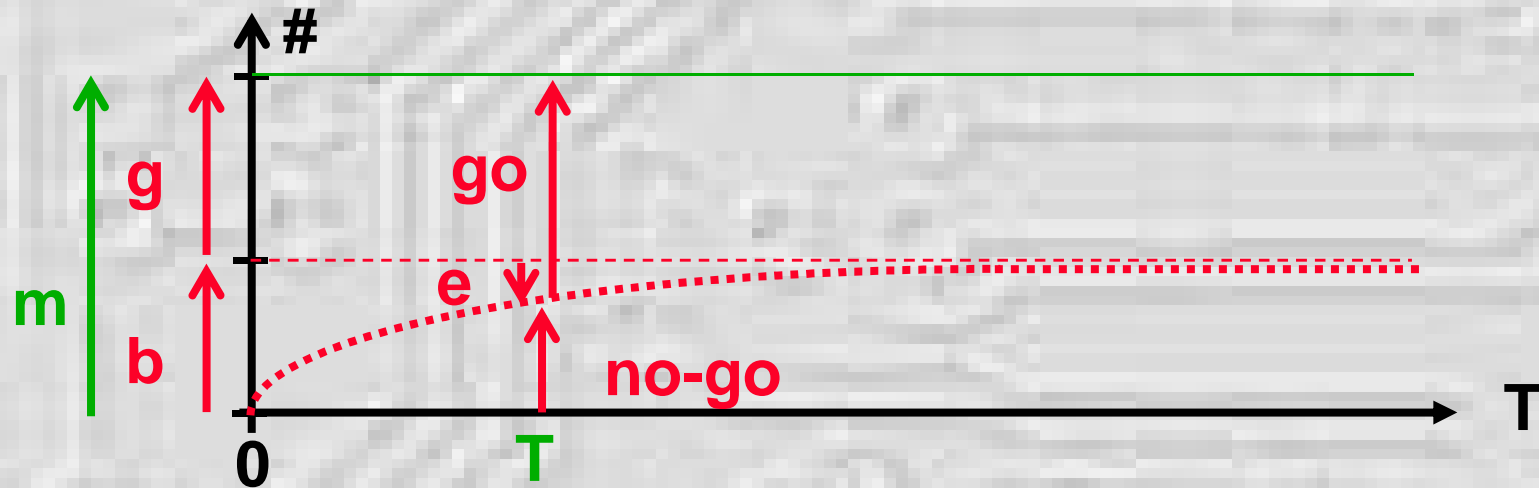

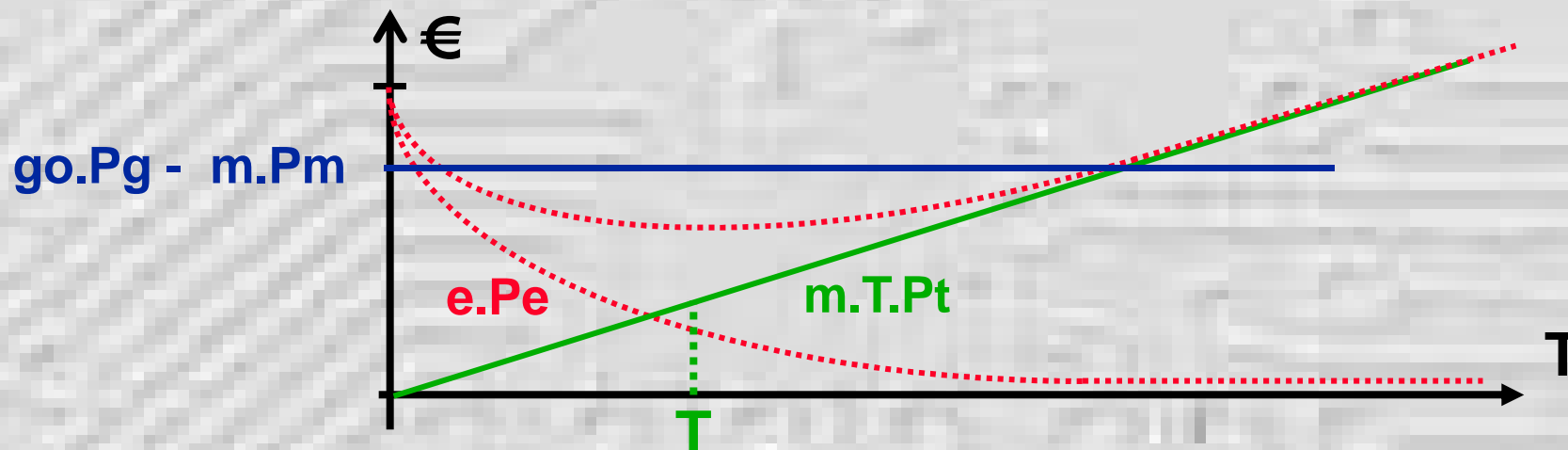
## I) Criteria to stop the test generation

=> Estimate how many faulty circuits not yet detected ( $e$ ?)




# Introduction

IN2P3

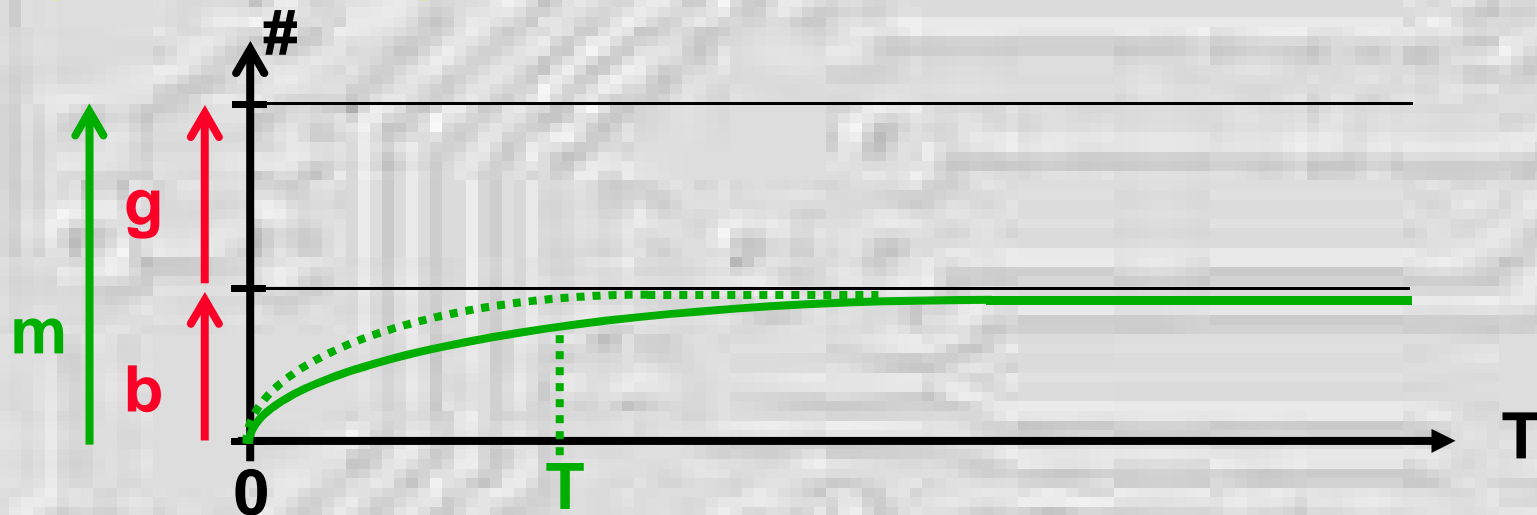

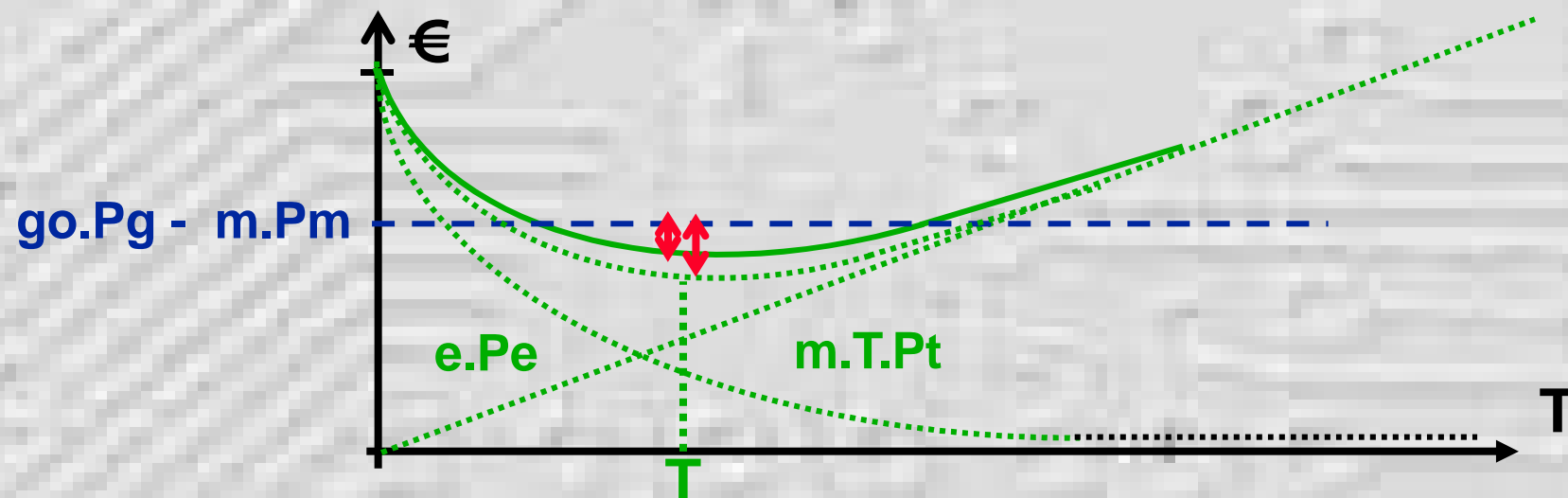
## II) Criteria to optimize the test generation

=> Estimate how many faulty circuits are detected by each vector



# Introduction

IN2P3

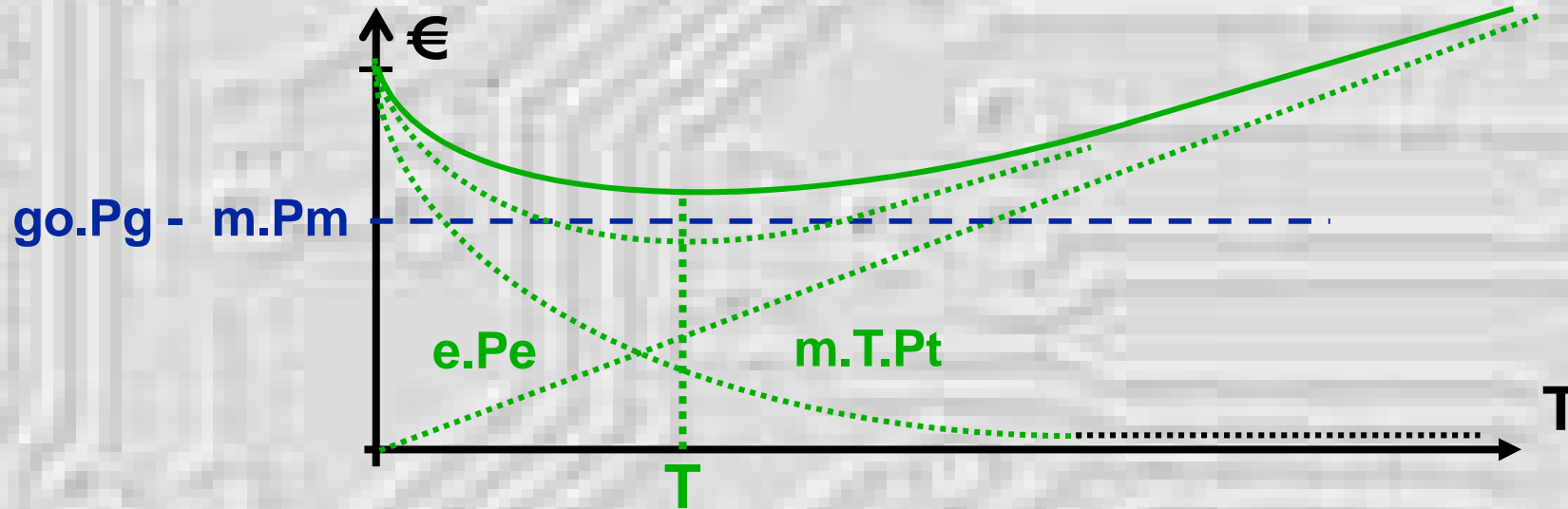

III) Criteria to make circuit Testable


=> Propose circuit modifications



# *Fundamental Properties*

# Fund. Props



IN2P3

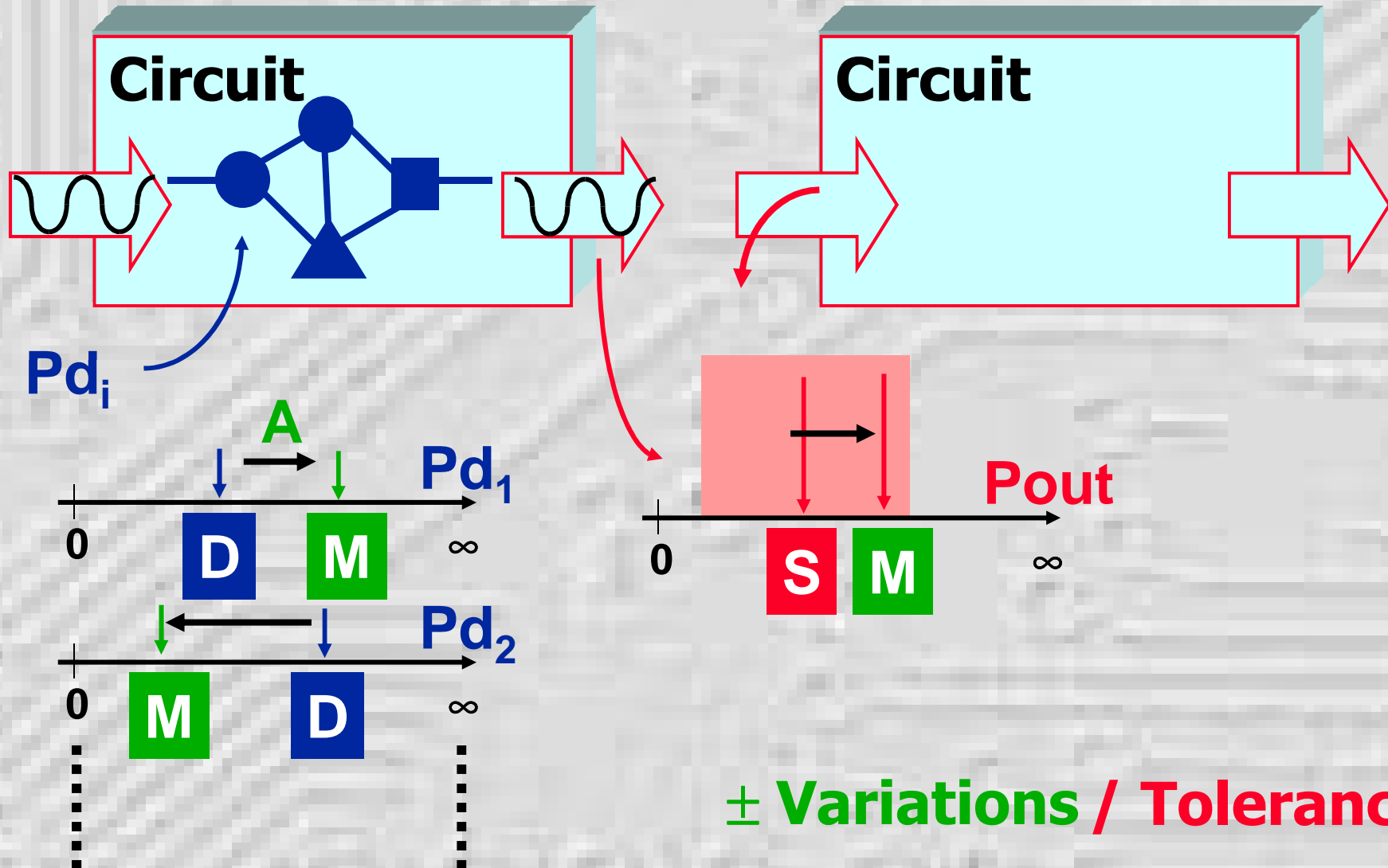


# Fund. Props

IN2P3


± Variations ?

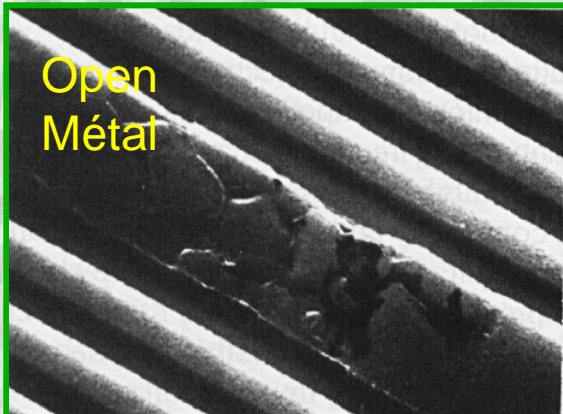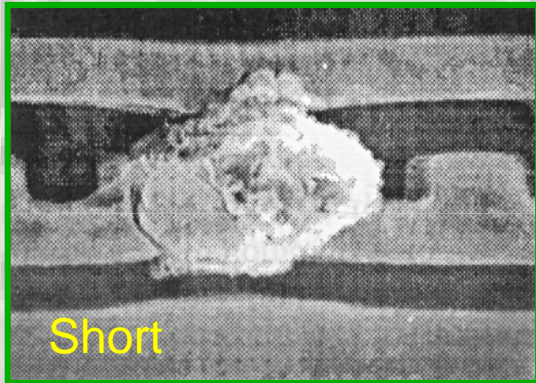

**Deviation**


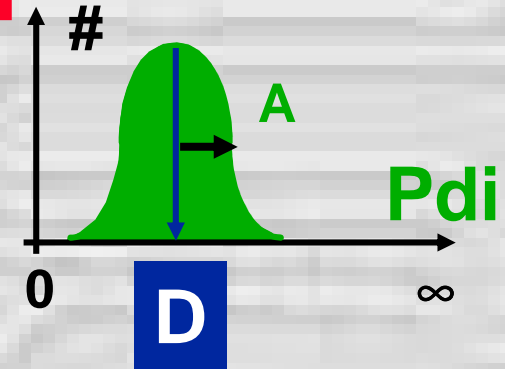


**Spot**

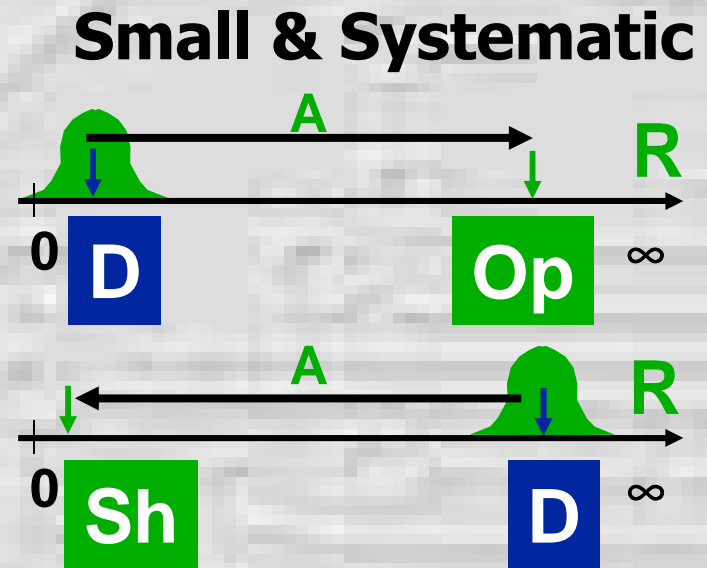

**Large & Scarce**

# Fund. Props

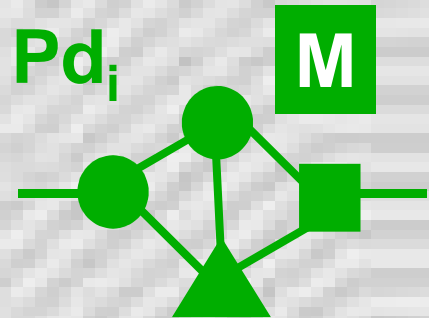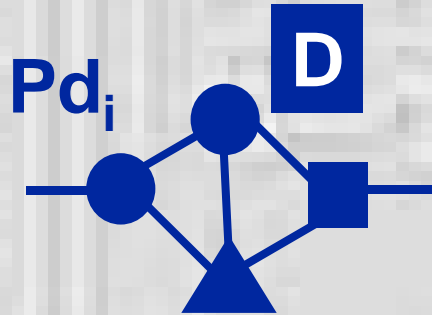





$\pm$  Variations

```
process begin
wait until not
CLOCK'stable
and CLOCK=1;
if(ENABLE='1') then
TOGGLE<= not
TOGGLE;
end if;
end process;
```

**Design**

$$Se = \Delta Pout / \Delta Pdi$$


**Manufacturing**

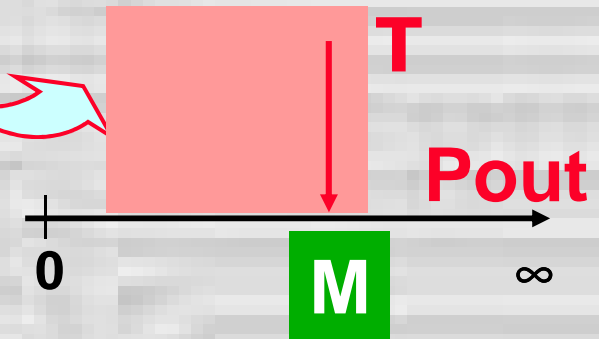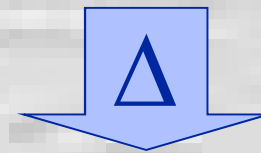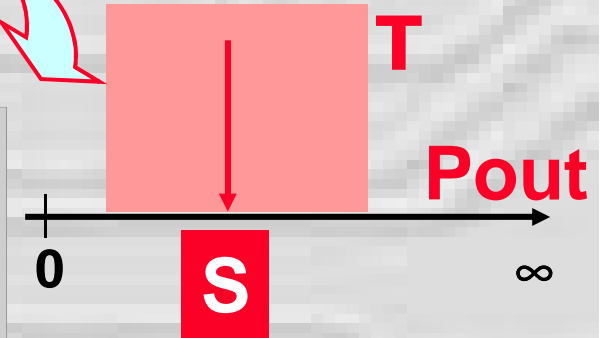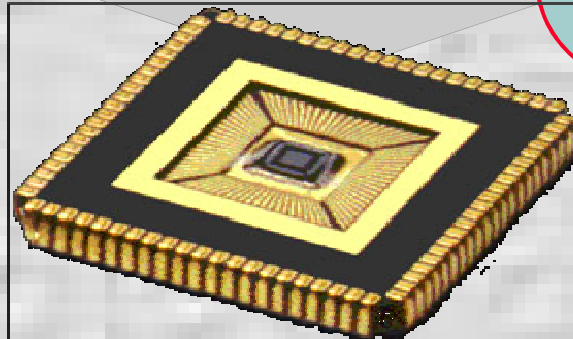

# Fund. Props
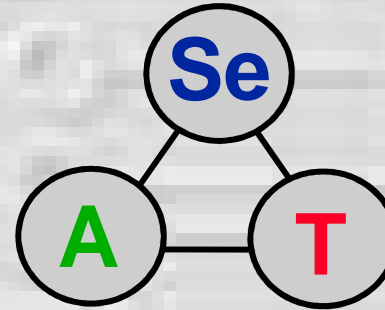
## Specification ?

```
process begin
wait until not
  CLOCK'stable
and CLOCK=1;
if(ENABLE='1') then
  TOGGLE<= not
  TOGGLE;
end if;
end process;
```



➔ **Amplitude** :  $A / D \Rightarrow F$

➔ **Tolerance** :  $Po / S \pm T$

➔ **Sensitivity** :  $Se = \frac{\Delta Ps}{\Delta Pdi}$

$A * Se < T ?$

$A < T / Se ?$



**Robustness**




# Fund. Props

IN2P3

```
process begin
  wait until not
    CLOCK'stable
    and CLOCK=1;
  if(ENABLE='1') then
    TOGGLE<= not
    TOGGLE;
  end if;
end process;
```

Specification ?

$$A < T / Se ?$$

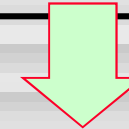

Robustness

Low  $T/Se$

High  $T/Se$

Deviations

Small  
Systematic

Spot

Large  
Scarce

Spot


Large  
Scarce

## Digital


```
process begin
wait until not
  CLOCK'stable
  and CLOCK=1;
if(ENABLE='1') then
  TOGGLE<= not
  TOGGLE;
end if;
end process;
```

## Specification ?

- Logic
- Timing

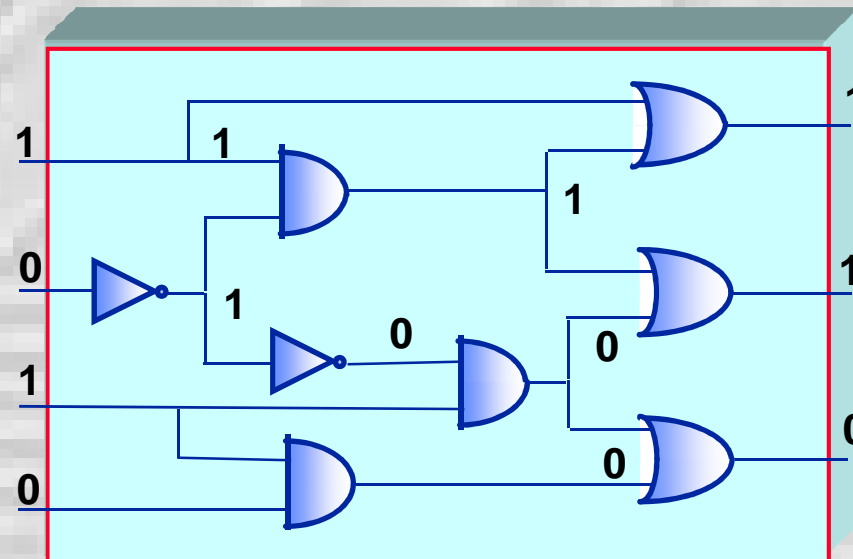

Cl



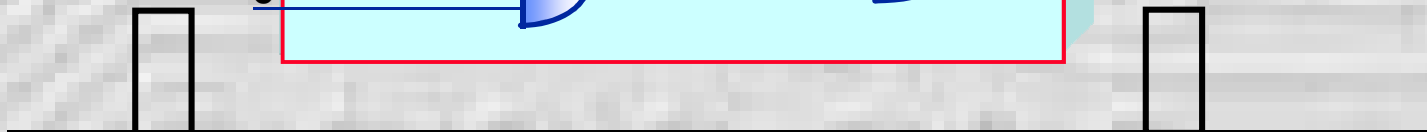


**Digital**

```
process begin
wait until not
  CLOCK'stable
  and CLOCK=1;
if(ENABLE='1') then
  TOGGLE<= not
  TOGGLE;
end if;
end process;
```

**Specification ?**



**- Logic  
- Timing**

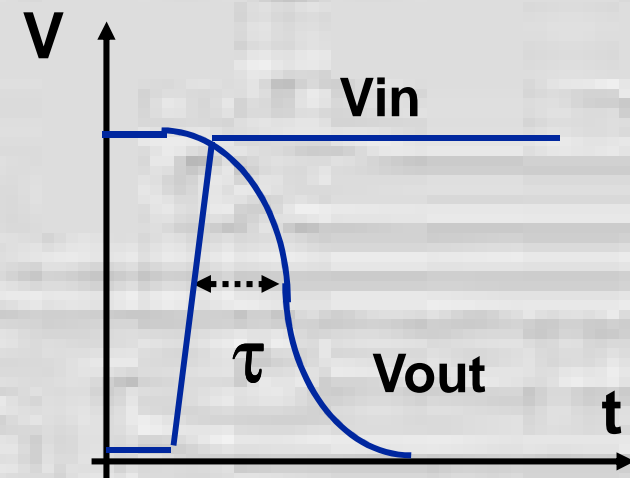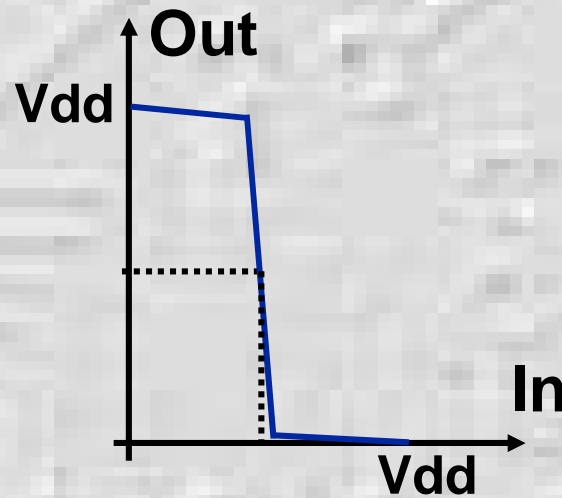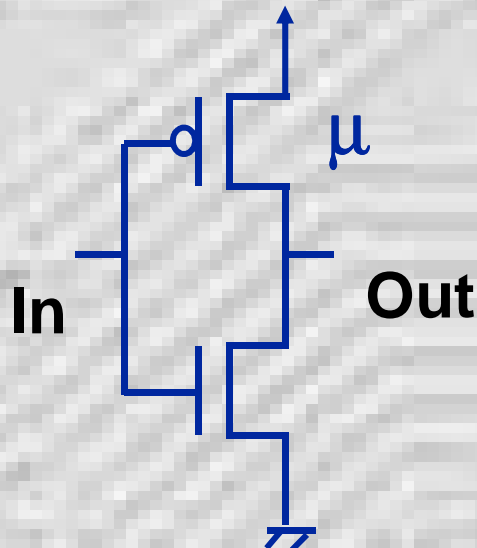

# Fund. Props

IN2P3



## Digital

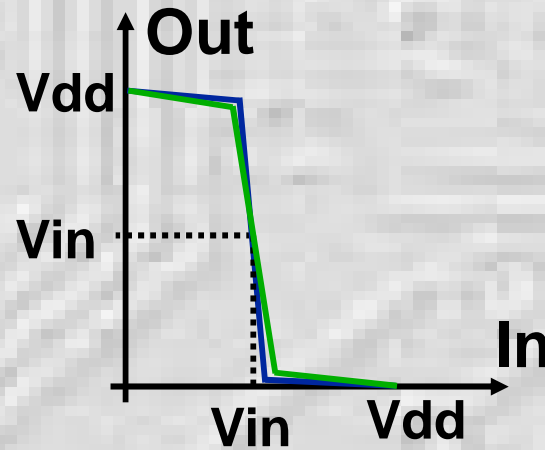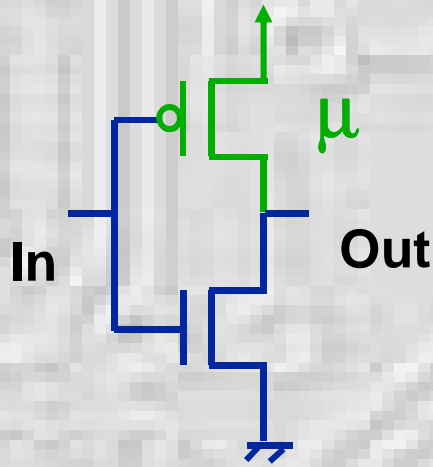

$$Se = \frac{\Delta Ps}{\Delta Pdi}$$

Very High  $T/Se$



Circuit Indpt

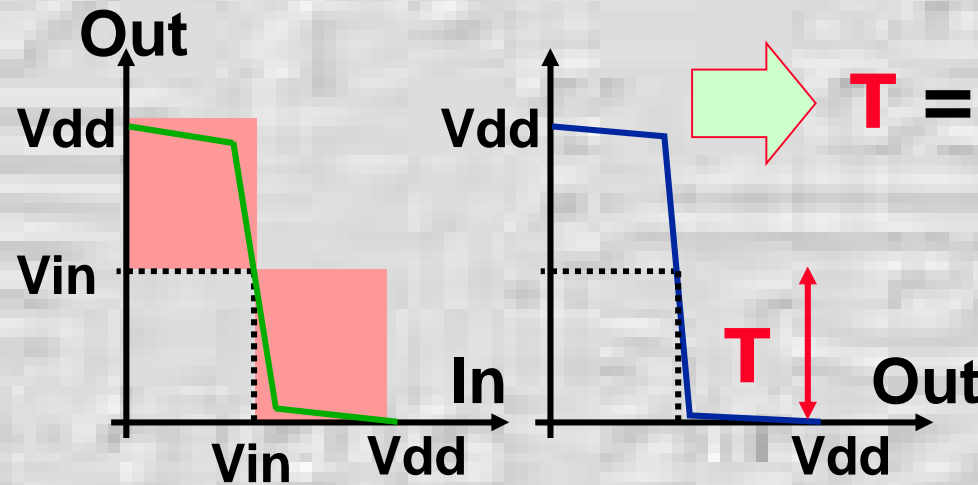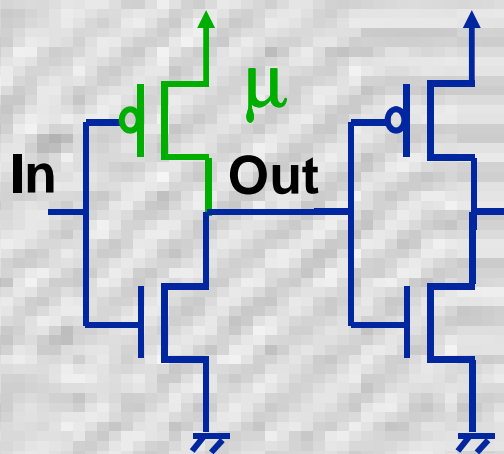



$$T = 50\%$$

## Digital

### Deviation

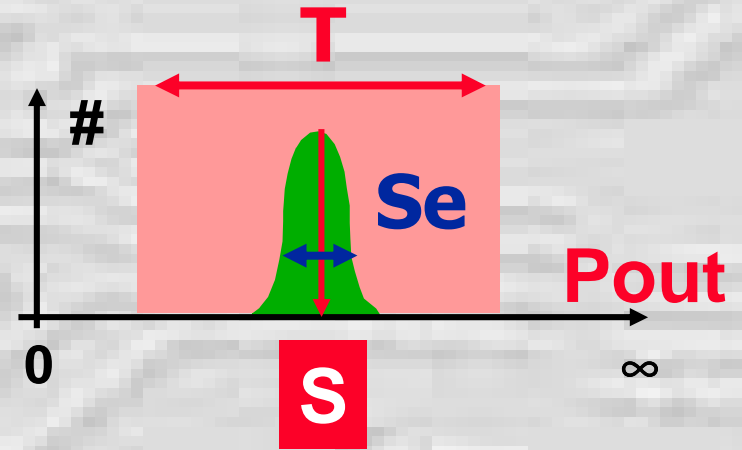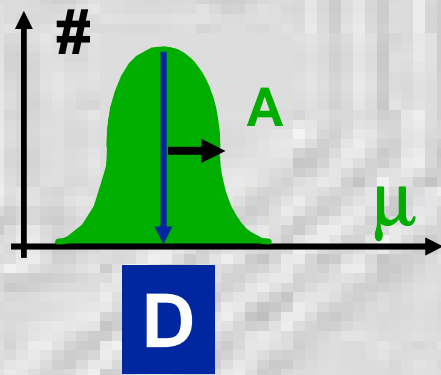


### Spot

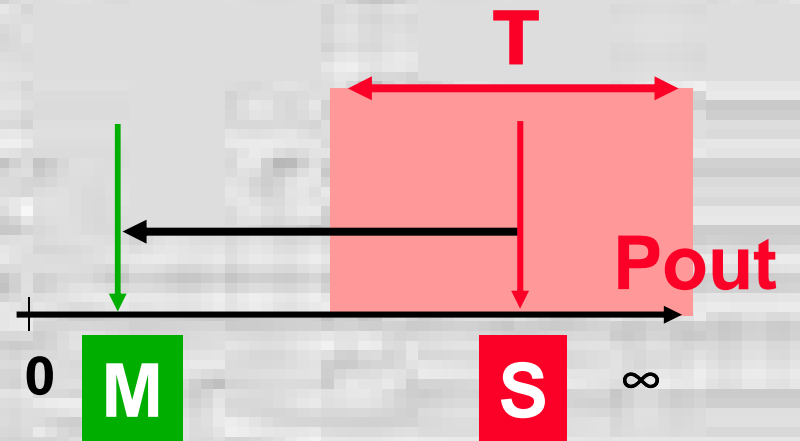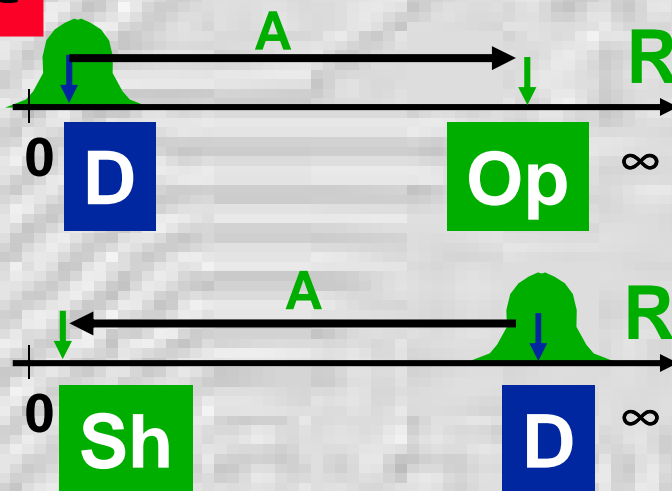

# Fund. Props


IN2P3

**Analog**

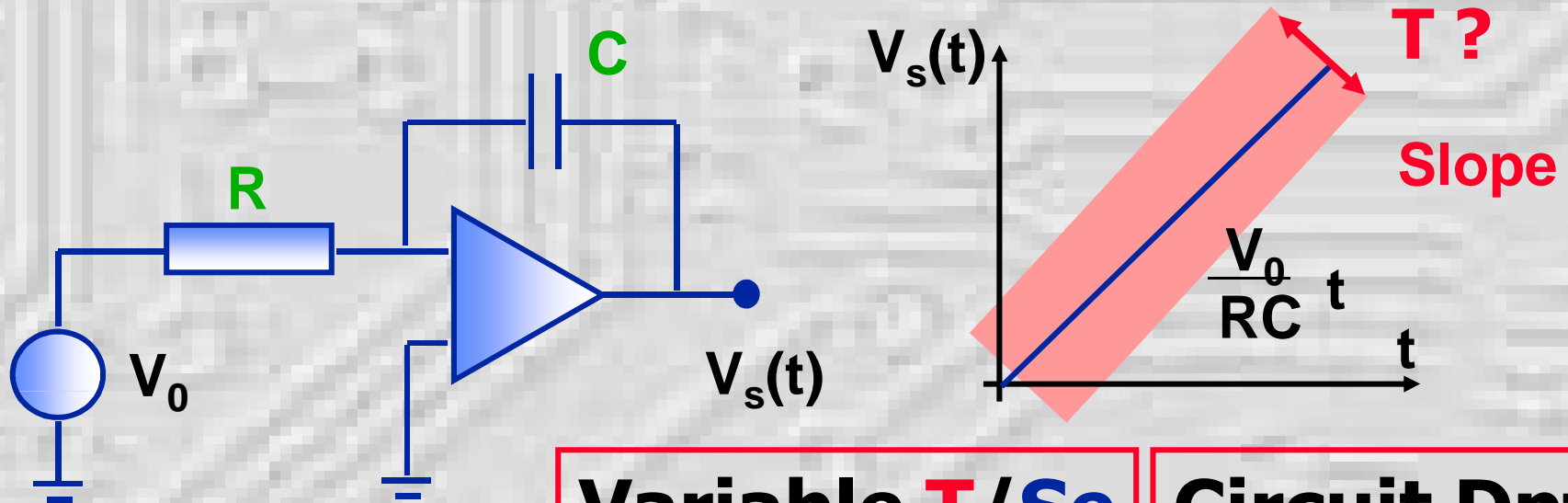

**Variable  $T/Se$**

**Circuit Dpt**

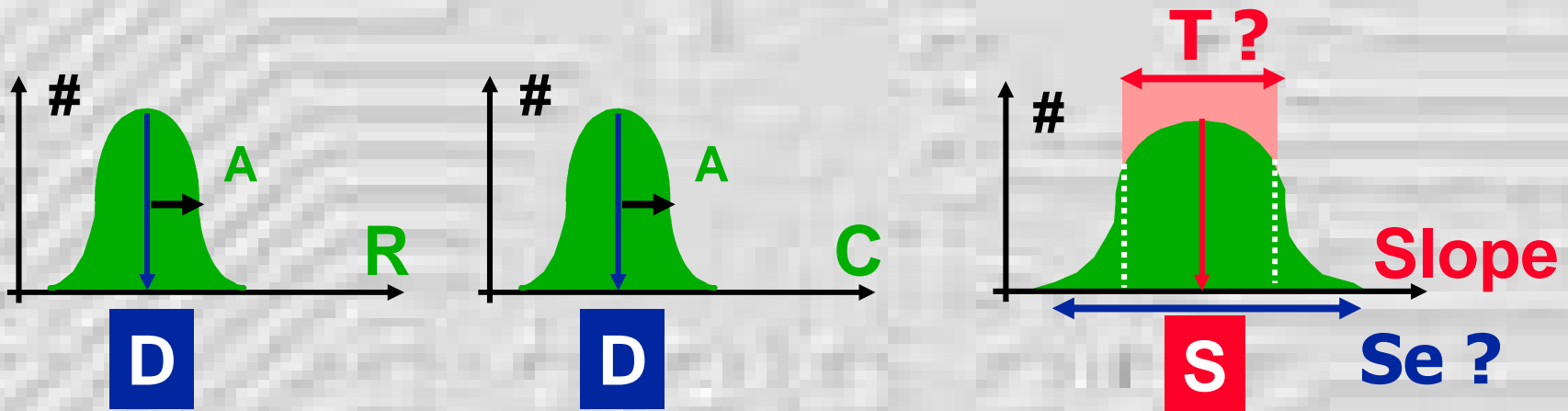

# Fund. Props

IN2P3

Digital

Analog


High T/Se

Low T/Se

Spots


Large & Sc.

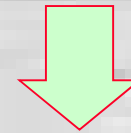Deviations Small & Syst.  
Spots Large & Sc.




Defect Oriented Test

Spec Oriented Test

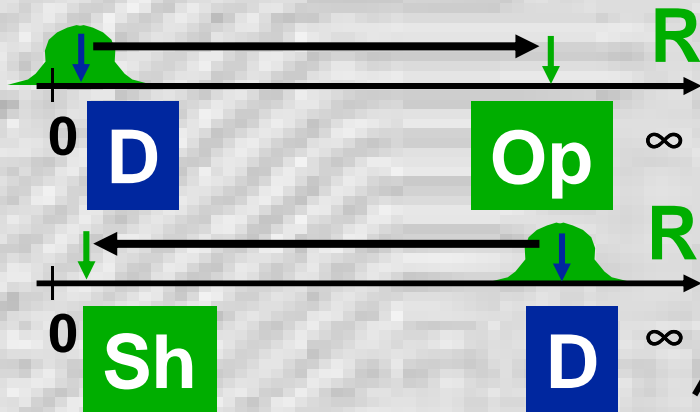

Timing

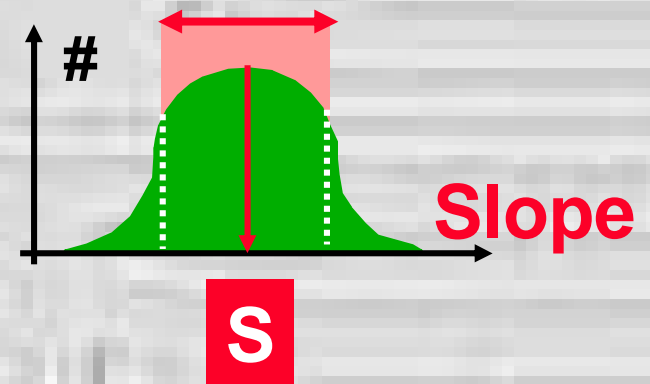



# Fund. Props

Digital

Analog

**Defect Oriented Test**

**Spec Oriented Test**

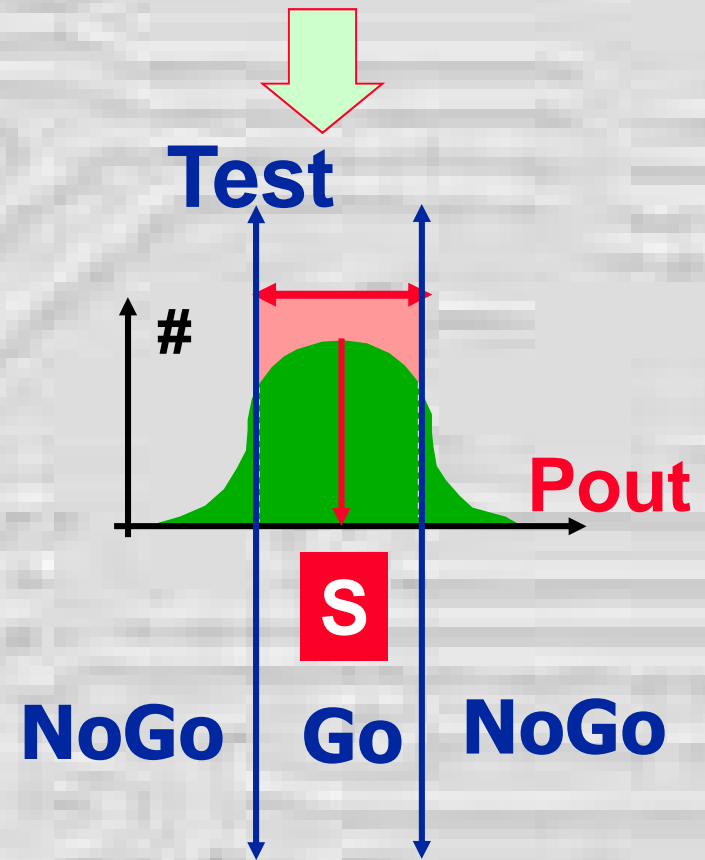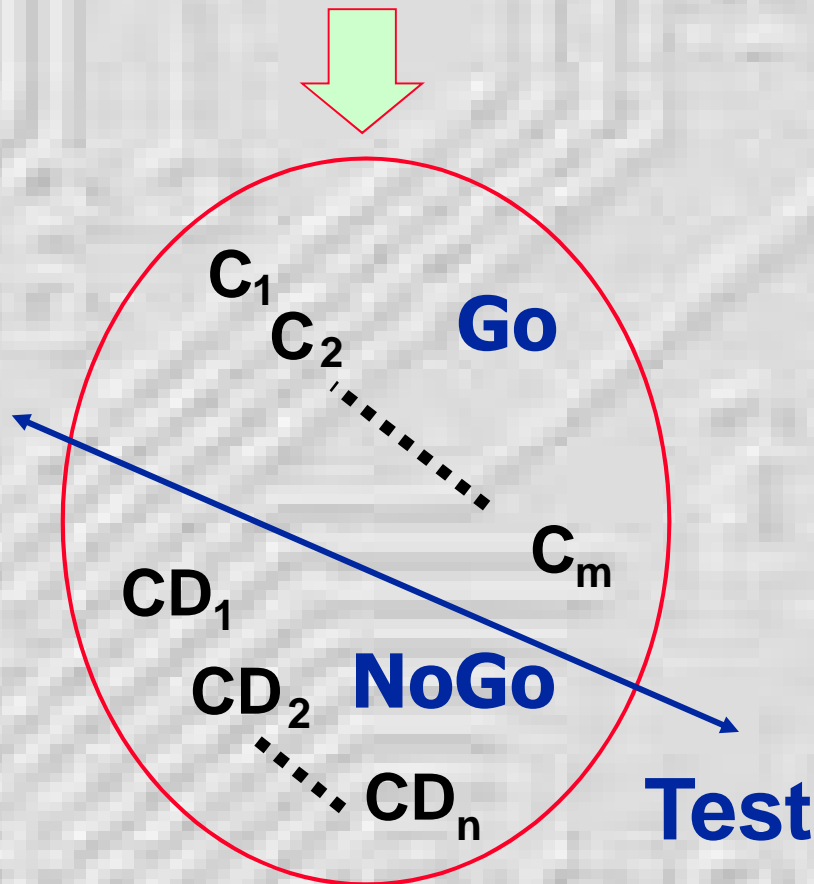





## Digital

## Analog

**Defect Oriented Test**



**Spec Oriented Test**

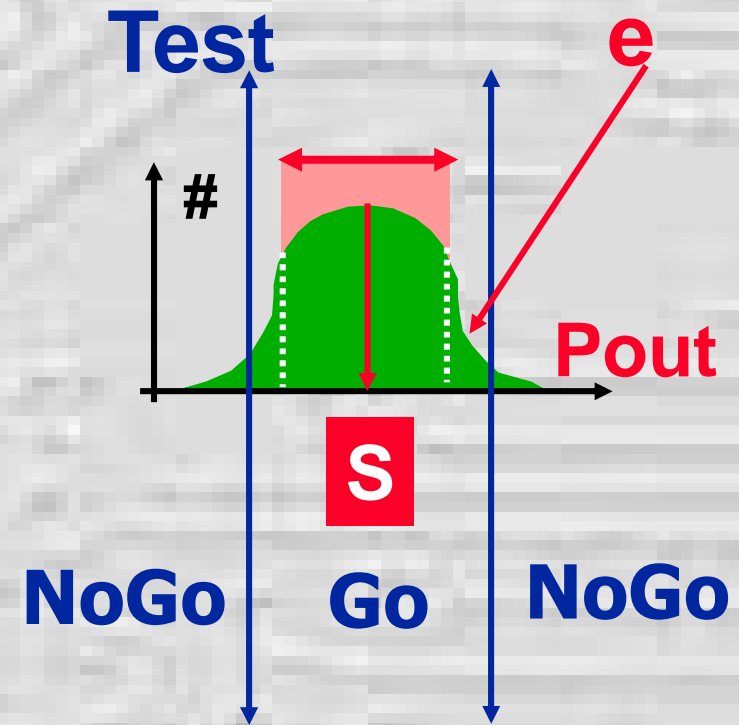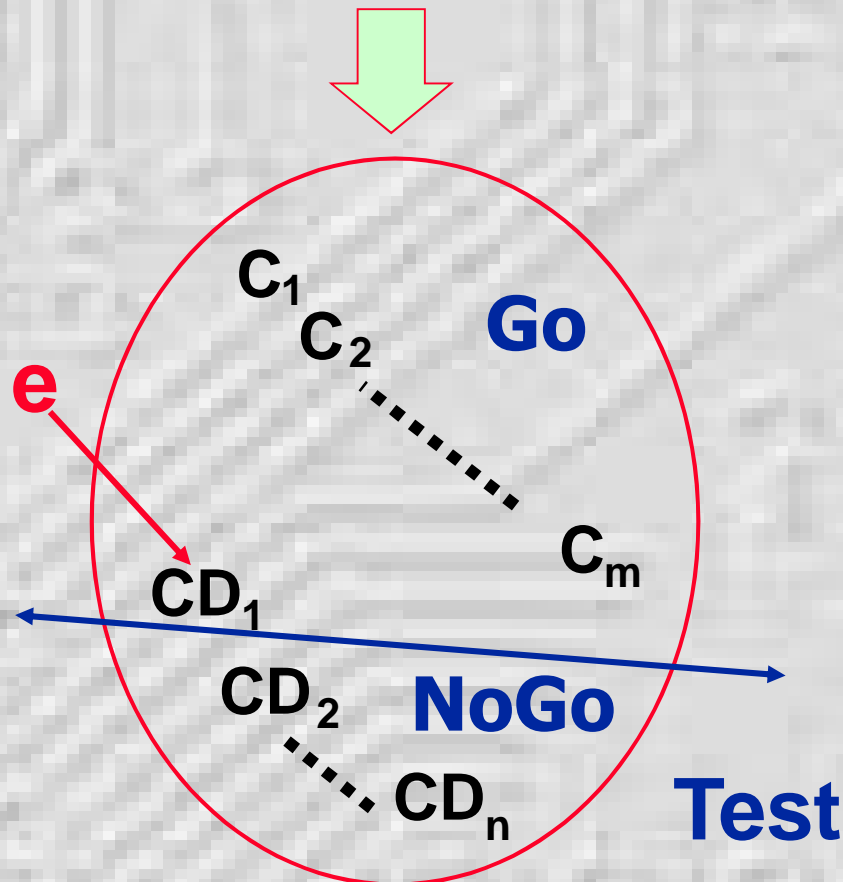


# *Digital Approach*

# Digital Approach


IN2P3

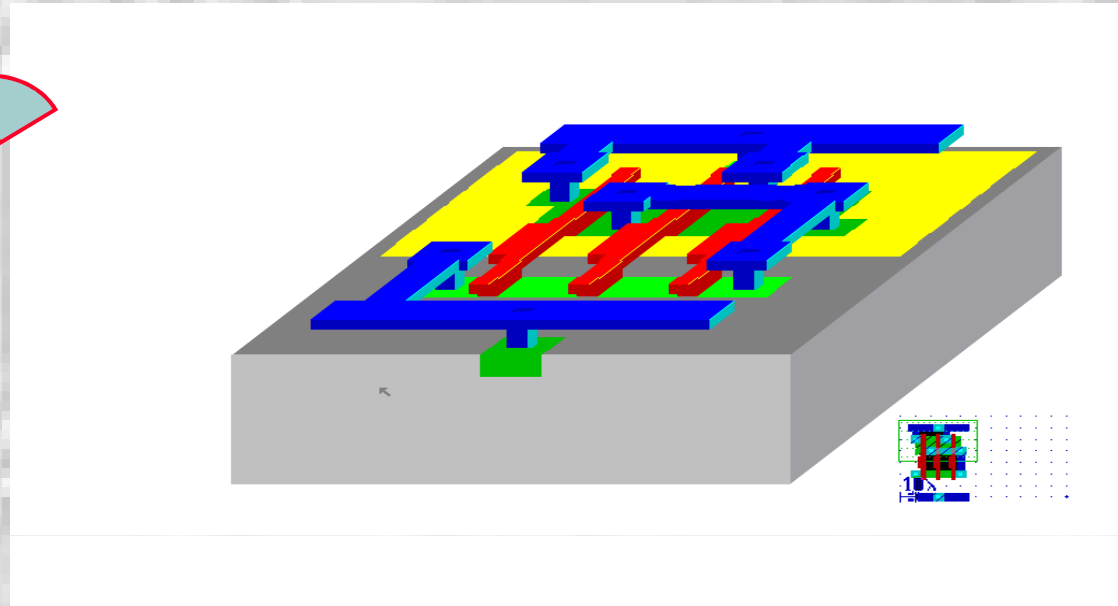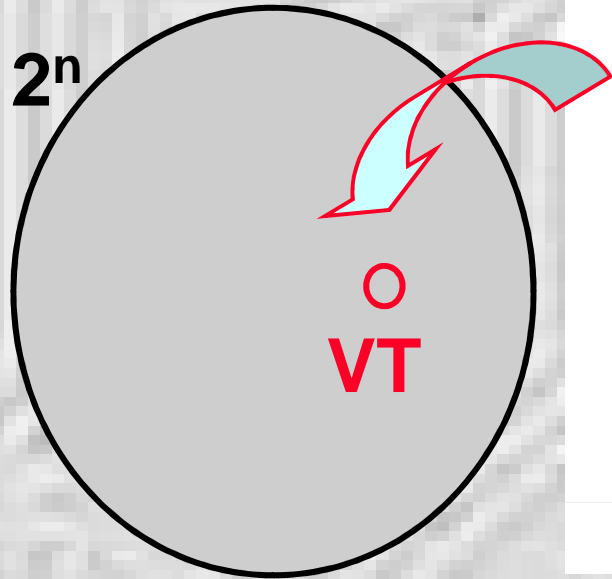

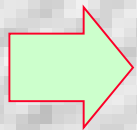Spot-Free Digital Circuit  $\Leftrightarrow$  In Specification





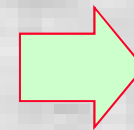
For each possible spot  
Compute a stimuli  
that reveals its presence



Test Pattern  
List


# Digital Approach

IN2P3

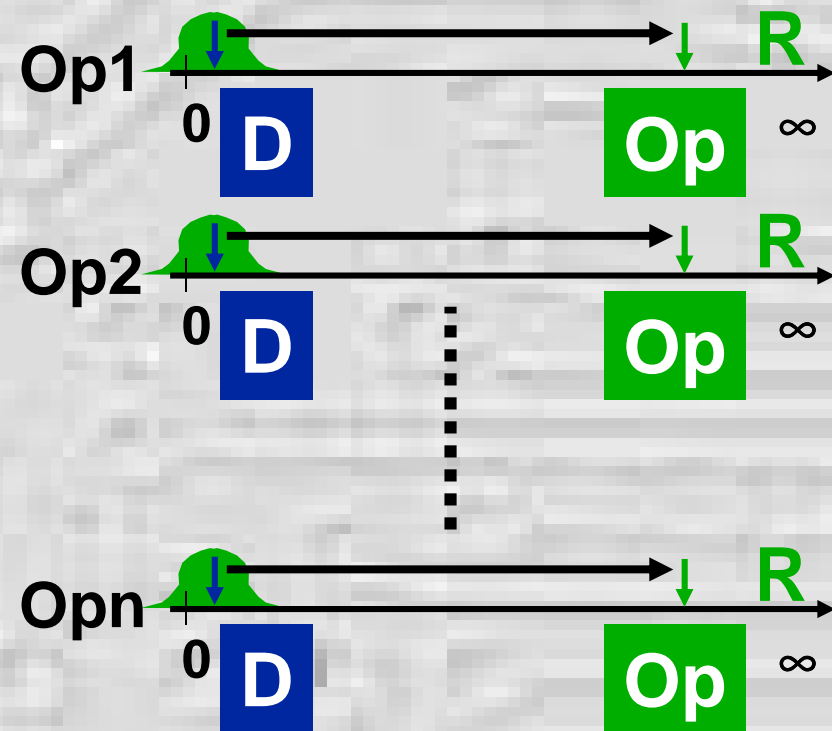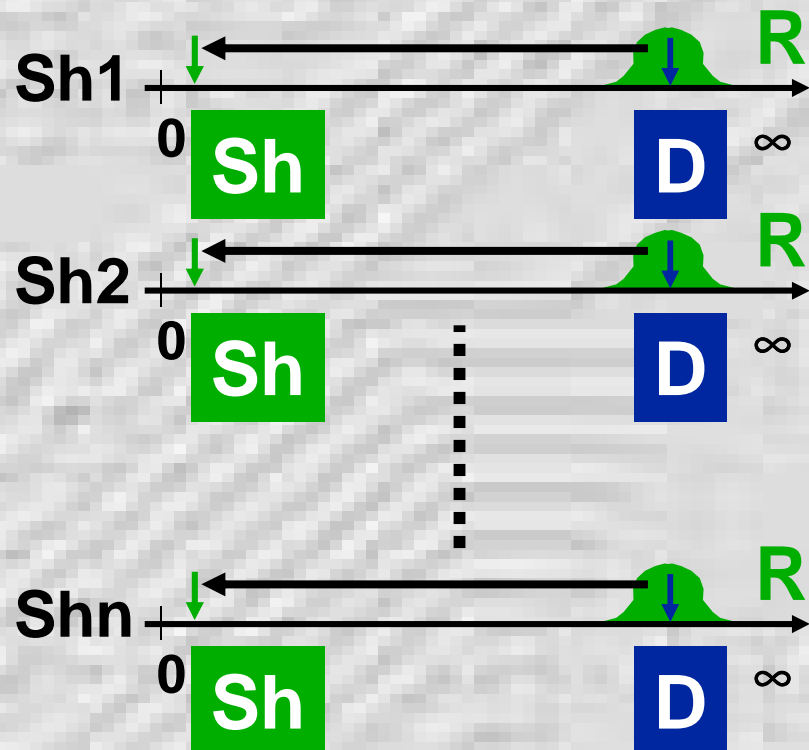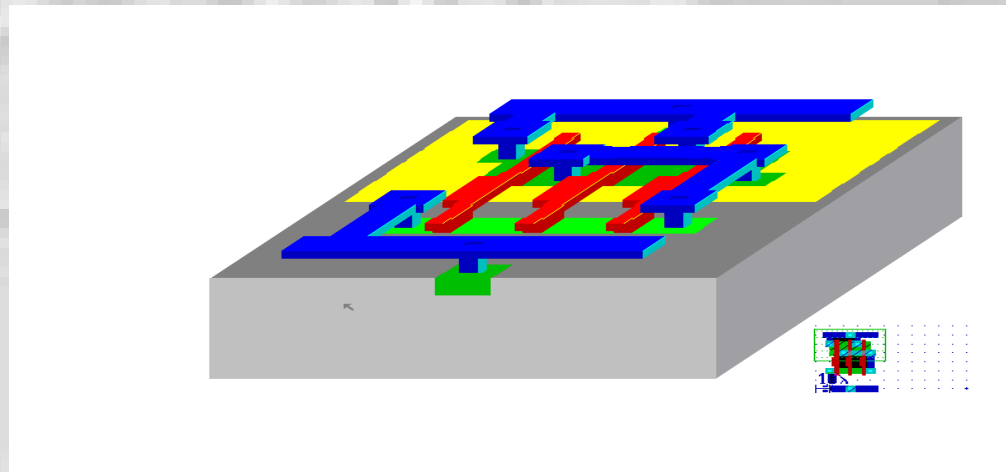



# Digital Approach

IN2P3

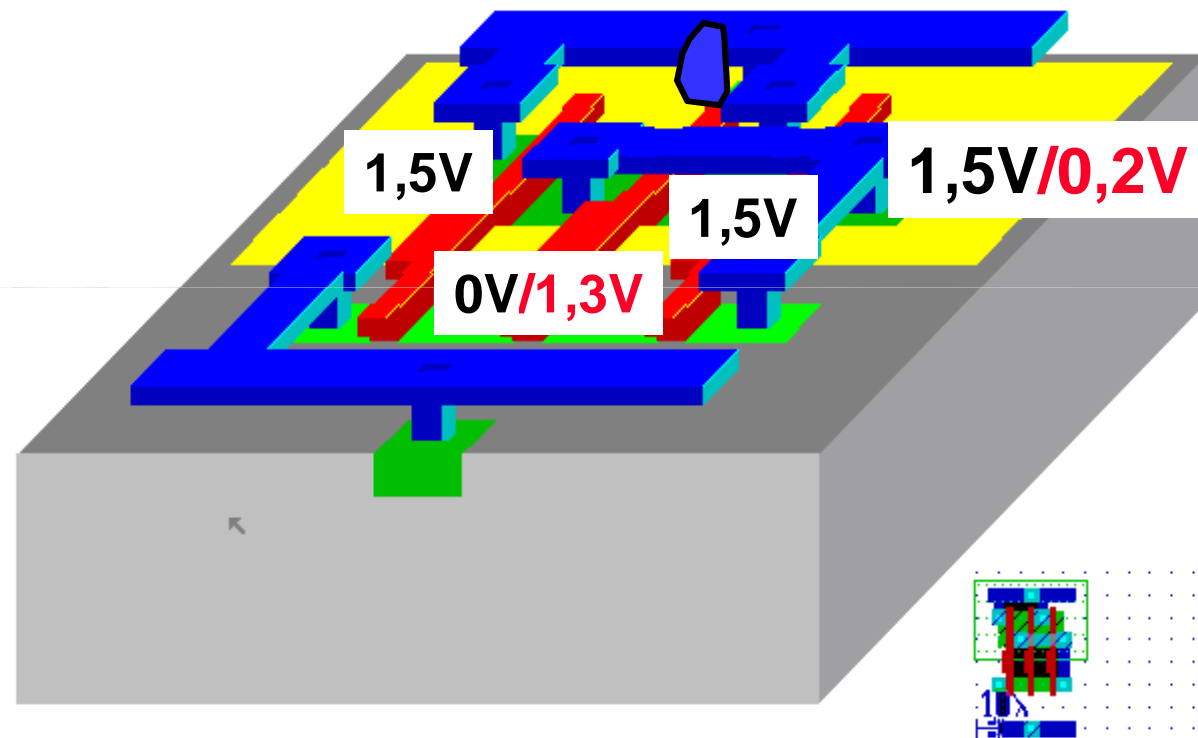

# Digital Approach

IN2P3

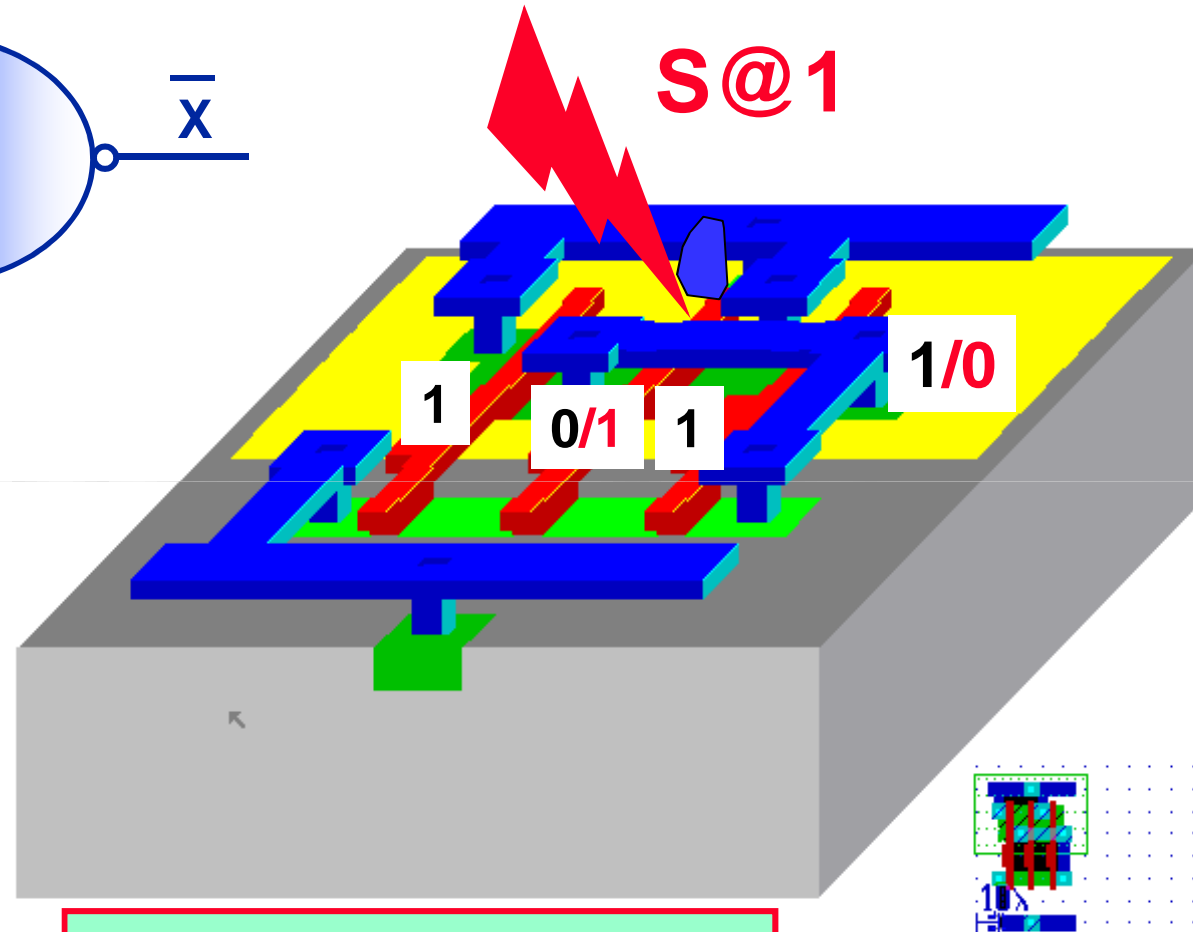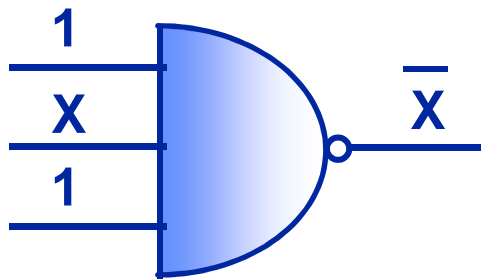


**Spot  $\Leftrightarrow$  Fault Model**

- $S@0$
- $S@1$

# Digital Approach

IN2P3

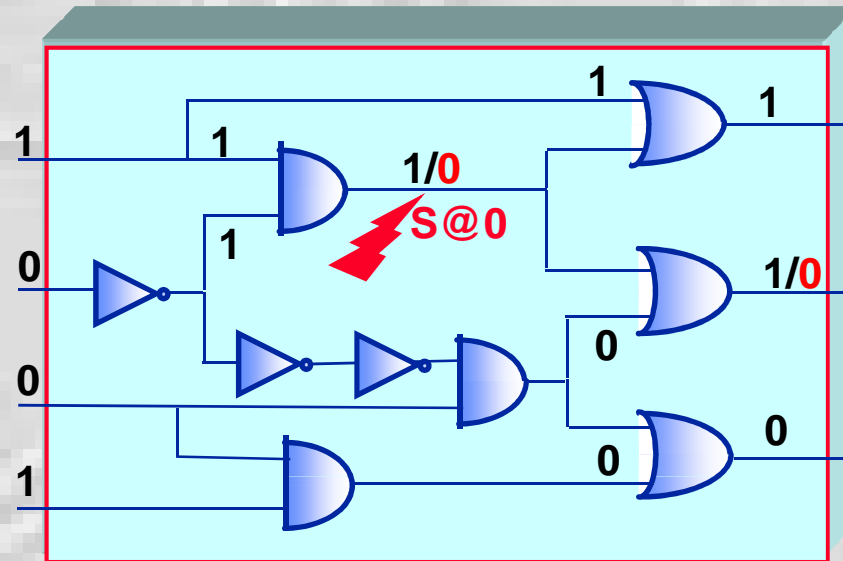



## Cost

- $10^6$  gates
- $10^6$  nodes
- $10^6$  S@0
- $10^6$  S@1
- $2 \cdot 10^6$  vectors
- 100Mhz

## Physical Structure $\Leftrightarrow$ Logical Structure

- Each Logic node S@0
- Each Logic node S@1
- TPG


# Digital Approach

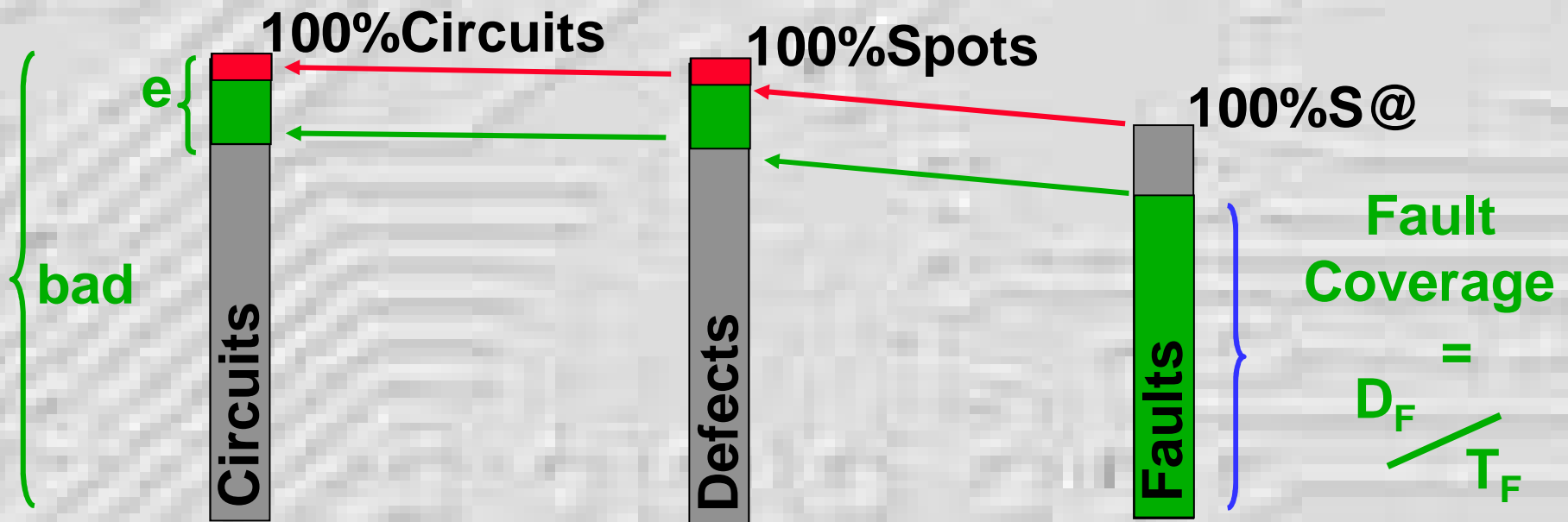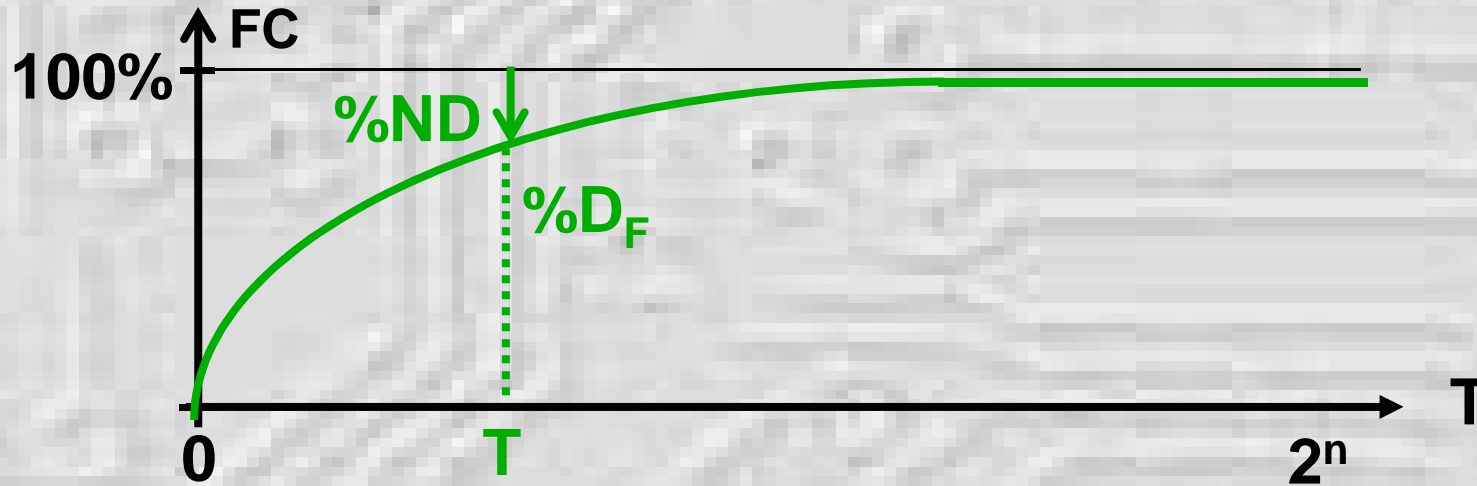





# Digital Approach

IN2P3

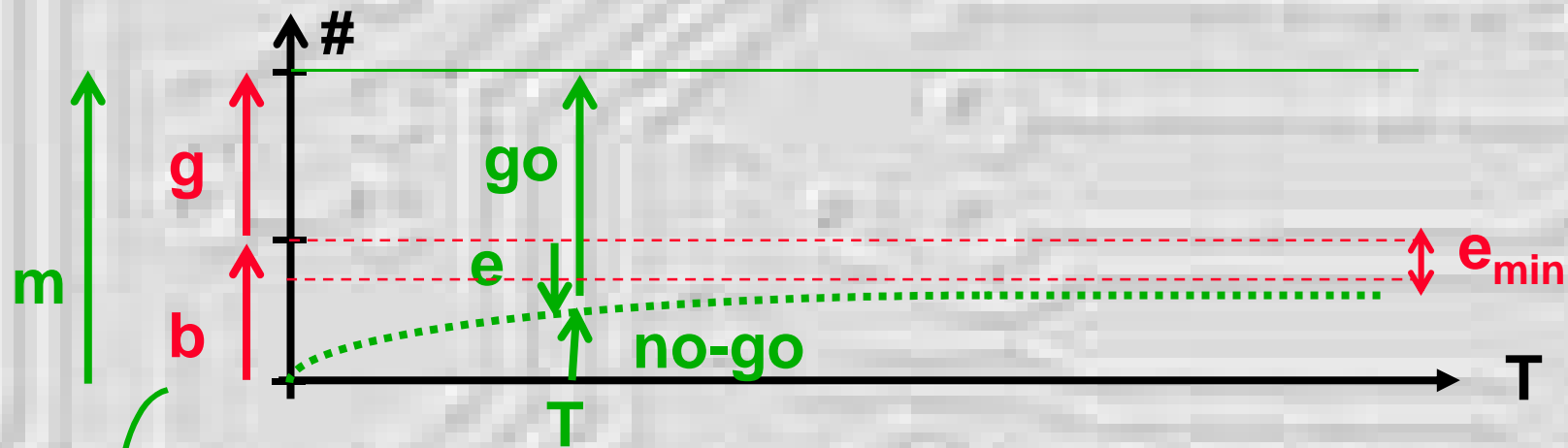


Quality

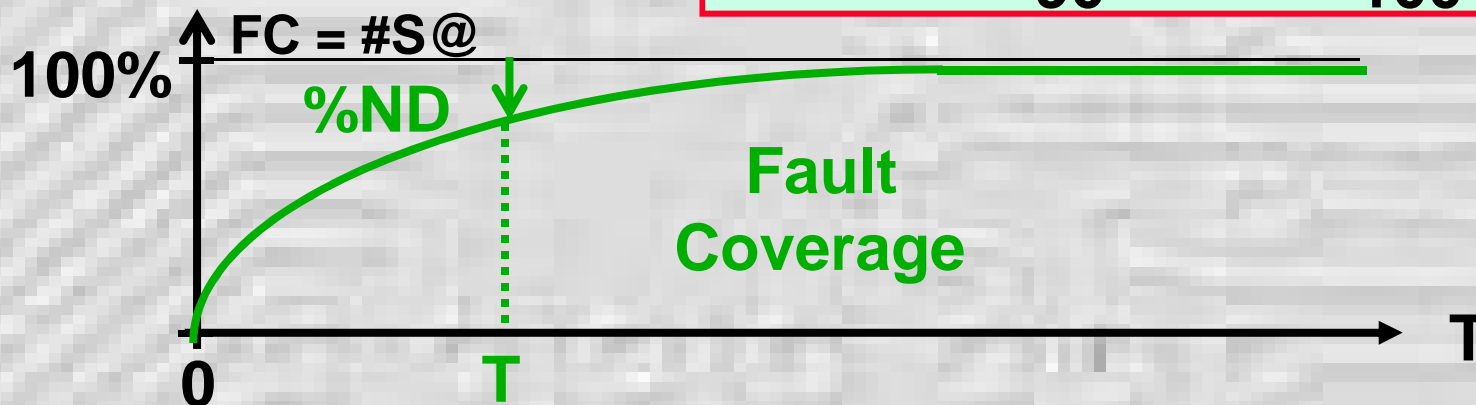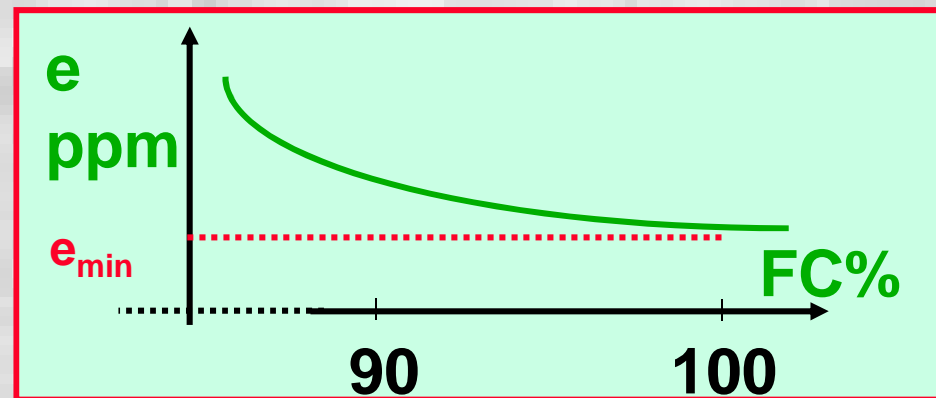


# Digital Approach

IN2P3

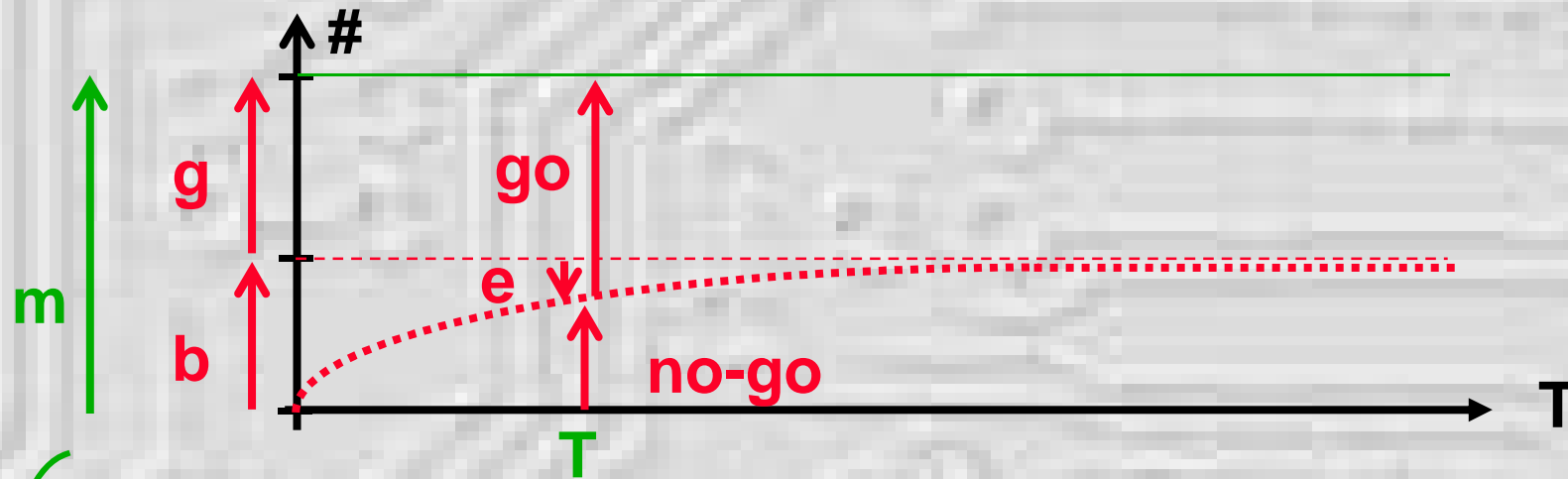

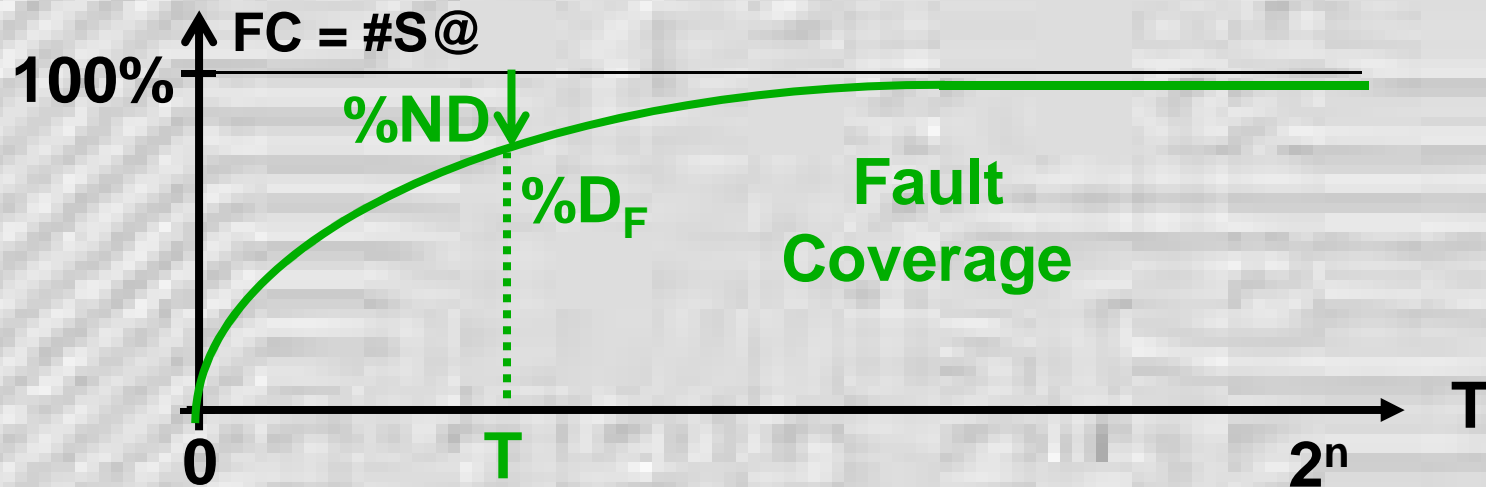
I) Criteria to stop the test generation

=> Estimate how many faulty circuits not yet detected (e?)




# *Test Generation*

# Test Generation

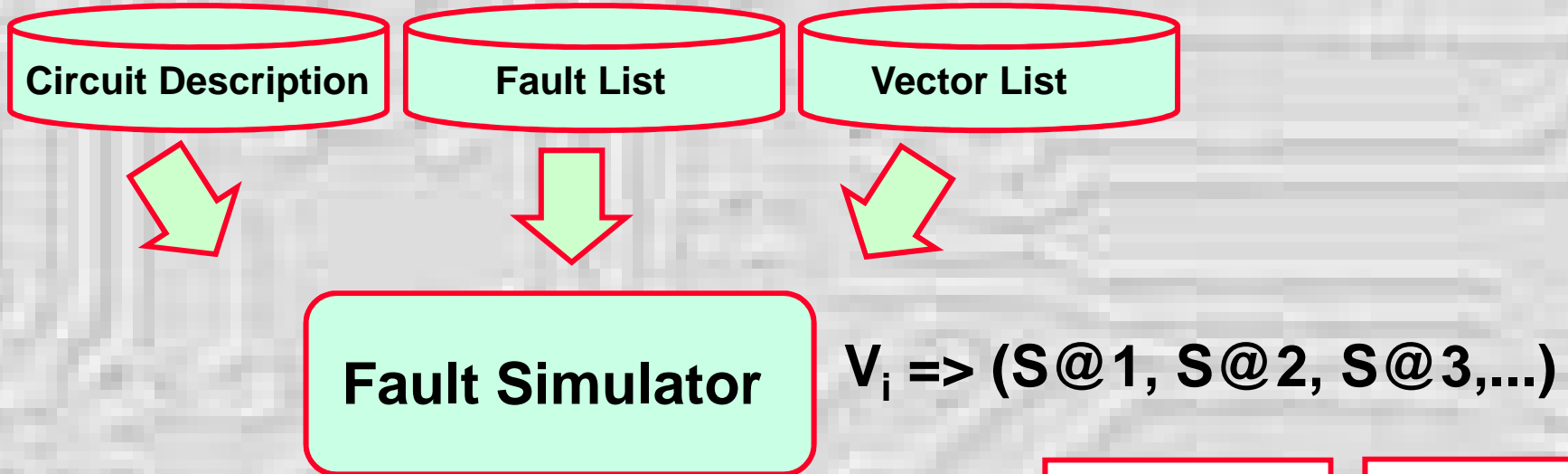


$$FC = \frac{D_F}{T_F}$$


**Compute**    **Select**

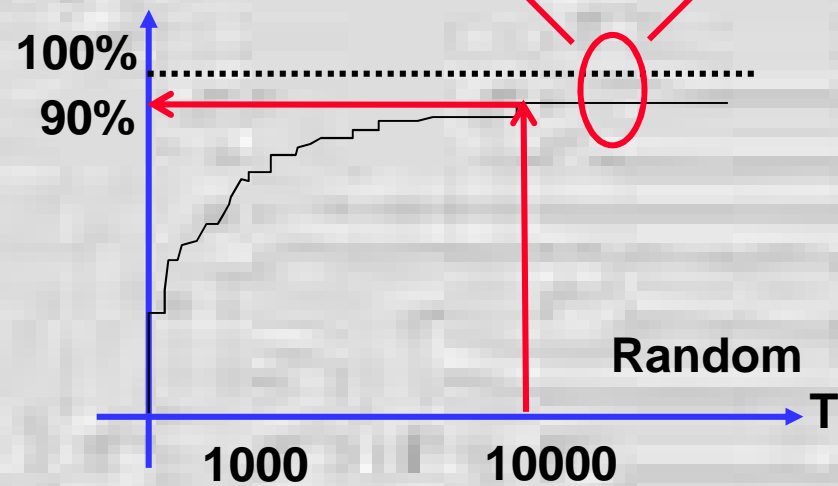

# Test Generation

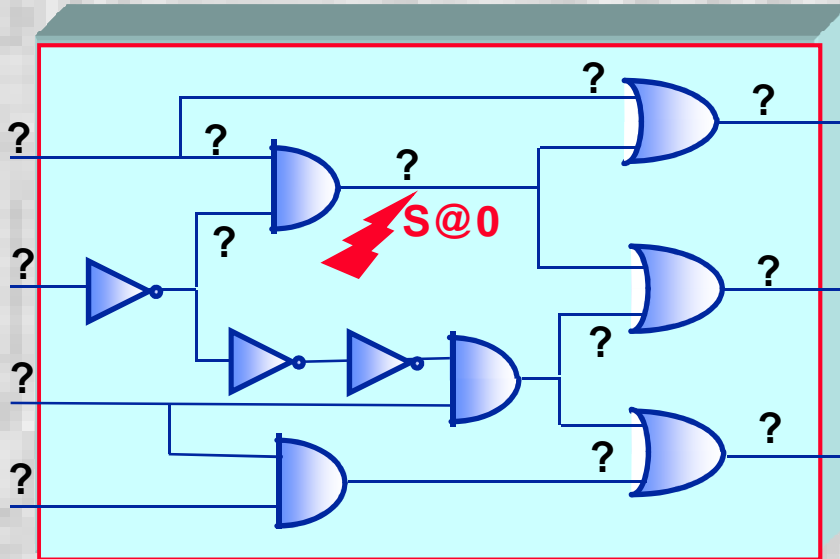


Compute  $\Leftarrow \Rightarrow$  ATPG

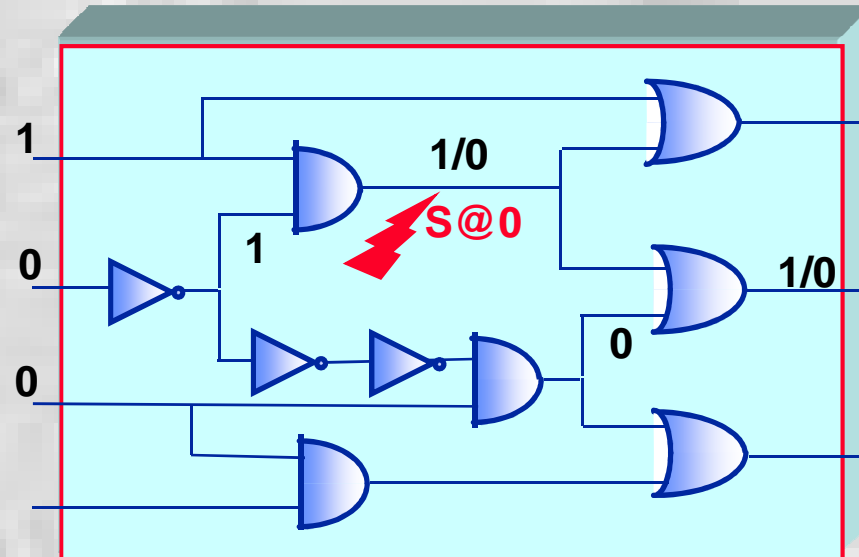


# Test Generation


IN2P3

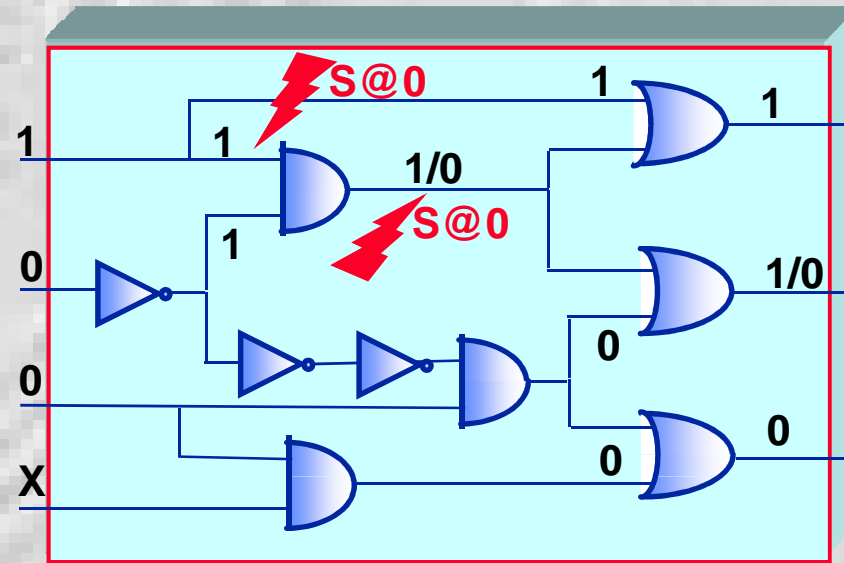

$T_9$

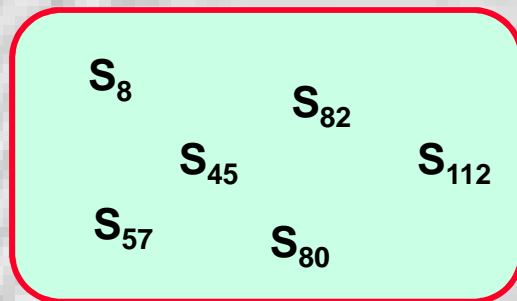


$S_{13}$

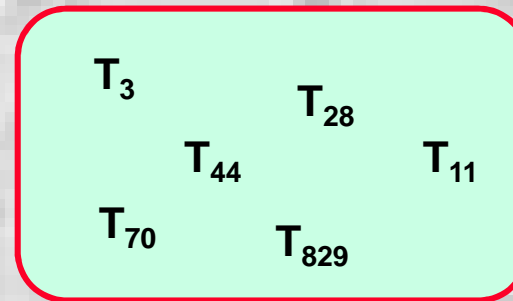


# Test Generation

IN2P3

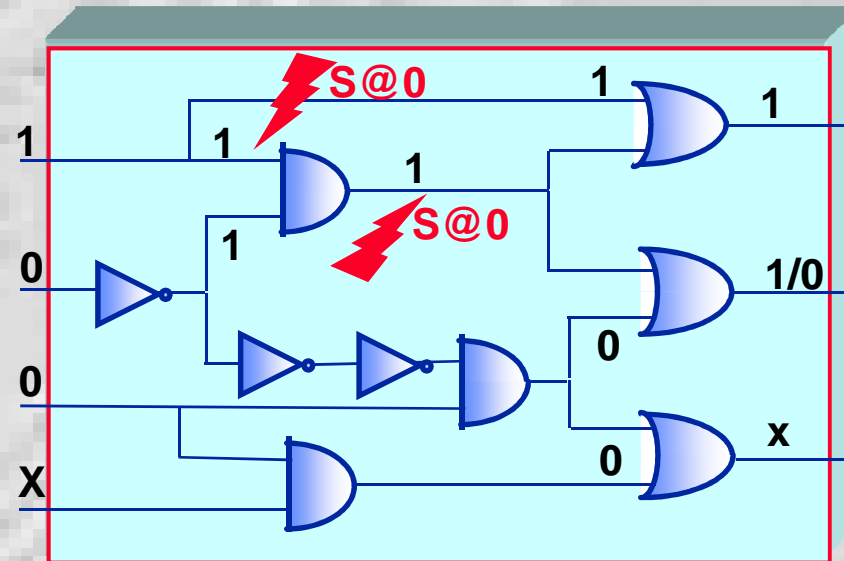


Cost

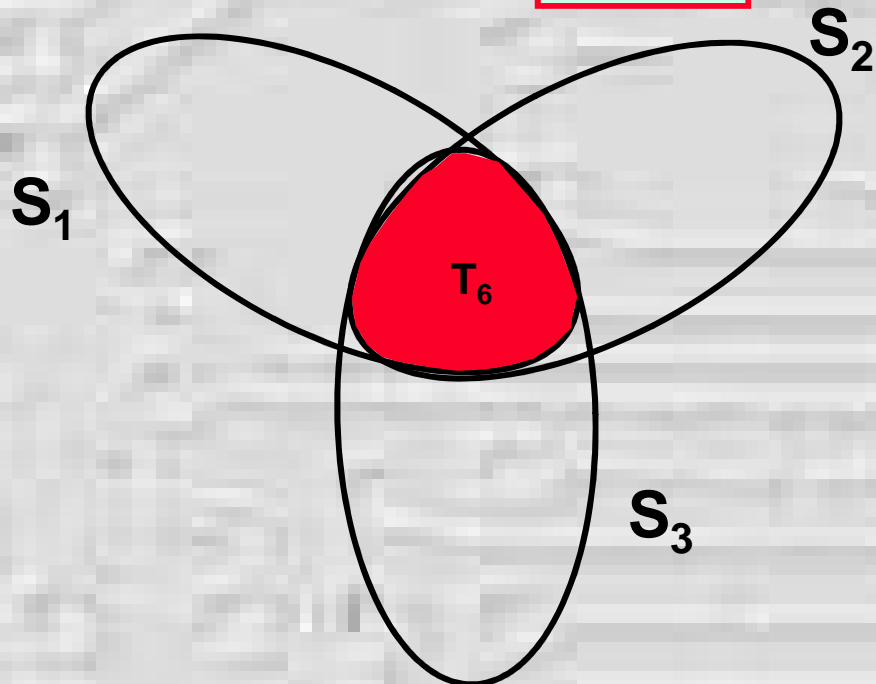- Desired e (Application)
- Desired FC%
- Structural ATPG => Vectors
- Minimal number



# Test Generation

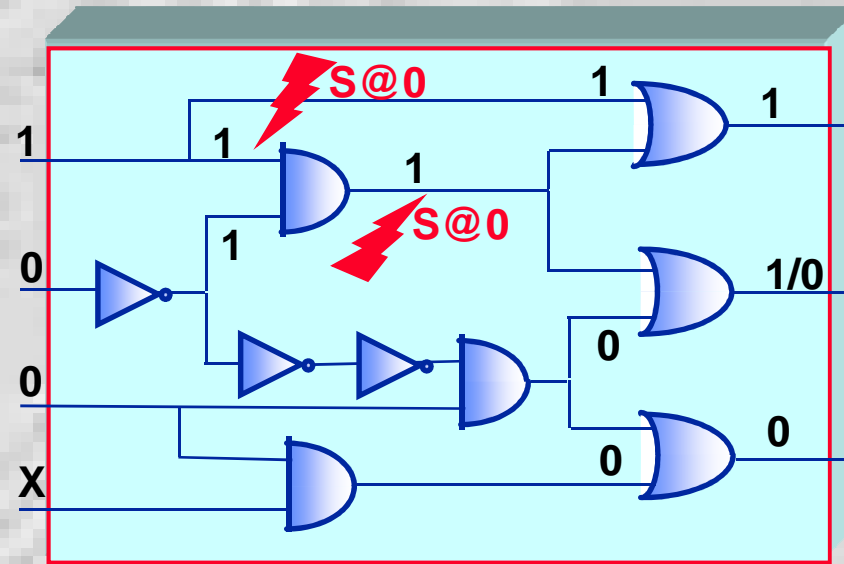

FC 90%

- $S@1 \Rightarrow S1 = (T_{11} \text{ or } T_{12} \text{ or } T_{13} \dots)$
- $S@2 \Rightarrow S2 = (T_{21} \text{ or } T_{22} \text{ or } T_{23} \dots)$
- $S@3 \Rightarrow S3 = (T_{31} \text{ or } T_{32} \text{ or } T_{33} \dots)$
- .....

**S1 and S2 and S3 and ..**

$$T = (T_1 + T_2 + T_3) (T_1) (T_2 + T_4)$$

$$T = T_1 T_2 + T_1 T_2 T_3 + T_1 T_4$$


$$+ T_1 T_2 T_4 + T_1 T_3 T_4$$

FC 98%



# Test Generation

IN2P3

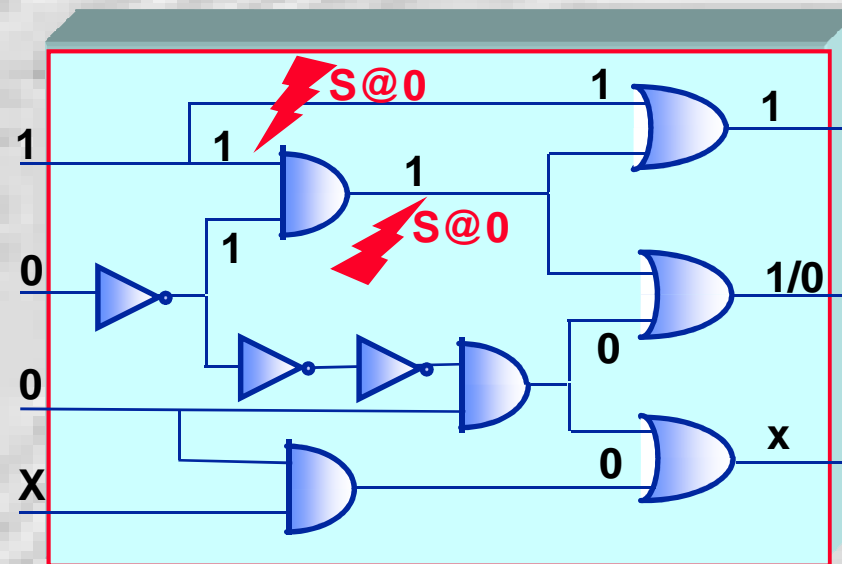

**Cost**


- ATPG :

$S@1 \Rightarrow T_{11}$  (np)

- Fault Simulation :


$V_{ij} \Rightarrow (S@1, S@2, S@3, S@4 \dots)$  (ok)

# Test Generation

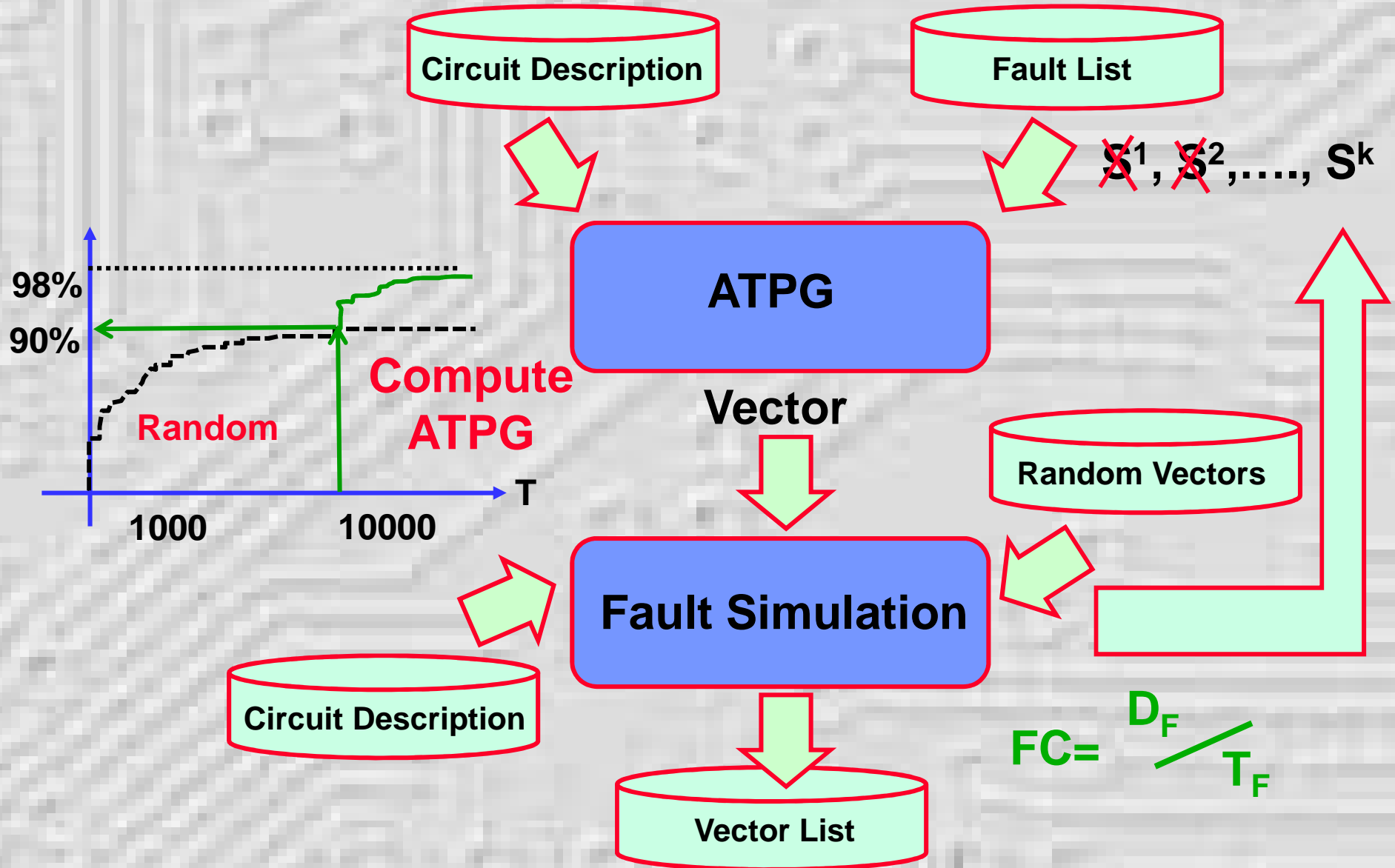

# Test Generation

IN2P3

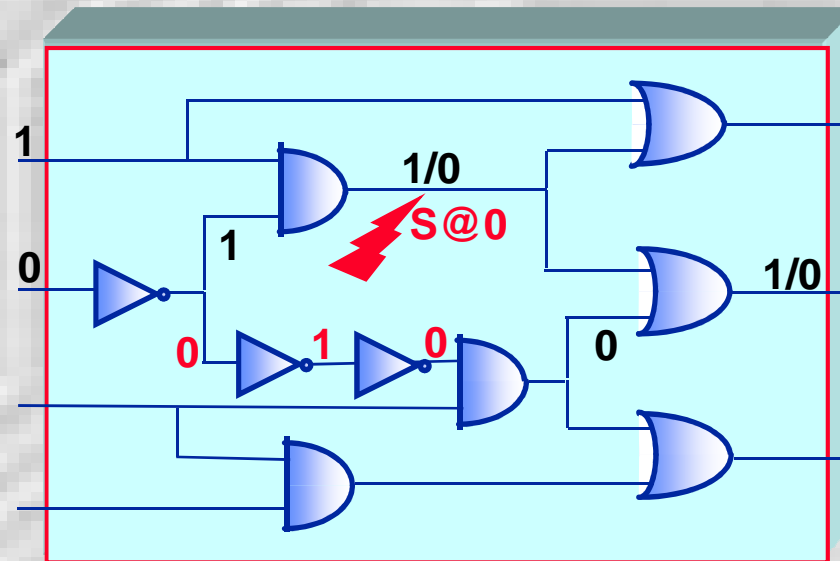

- Backward justification
- Conflict
- Backtrack



- Limited number Backtrack
-


# Test Generation

IN2P3




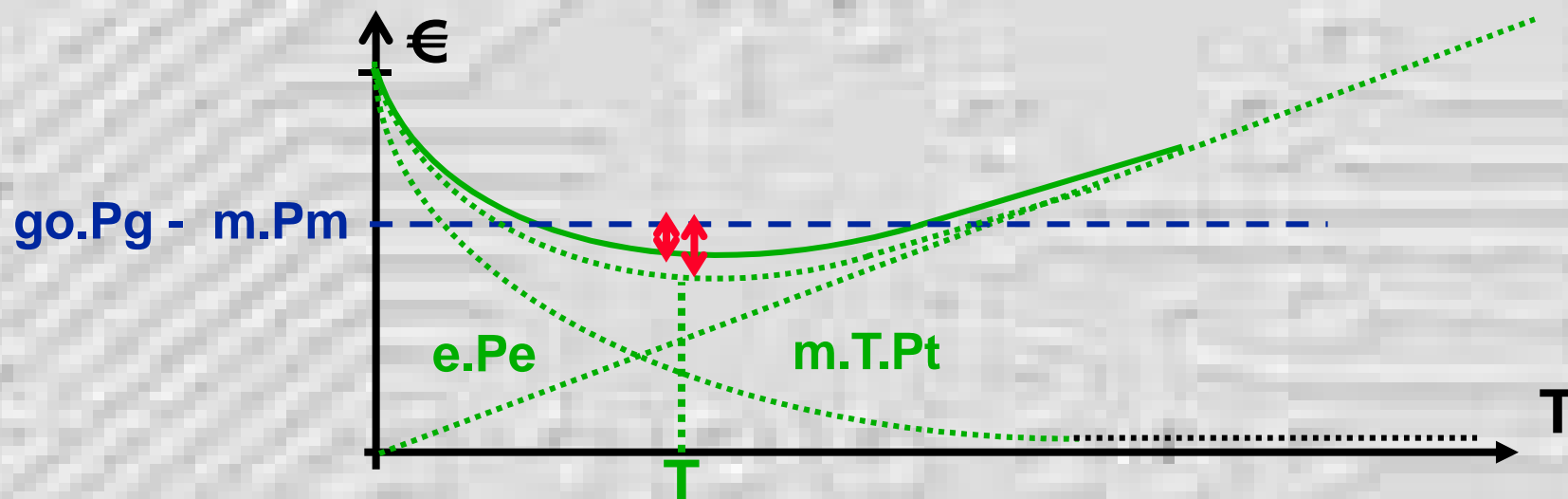
## II) Criteria to optimize the test generation


=> Estimate how many faulty circuits are detected by each vector



*Design  
For  
Testability*

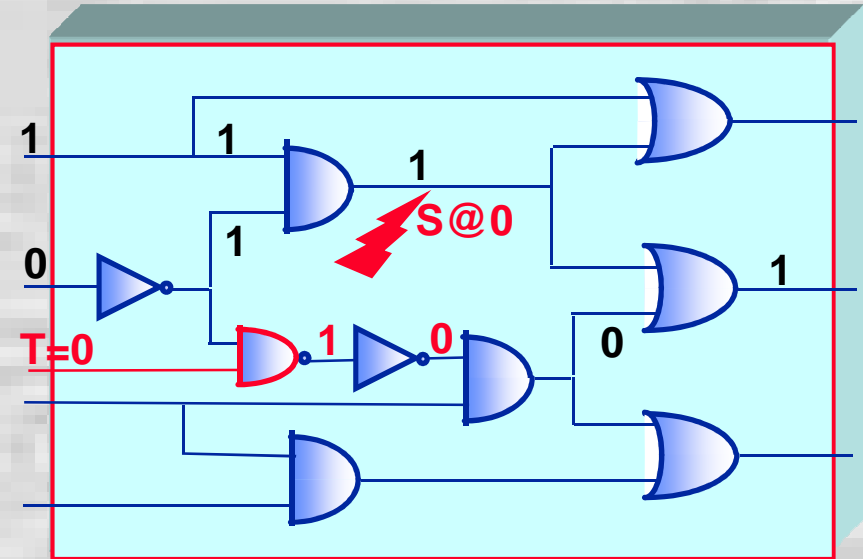
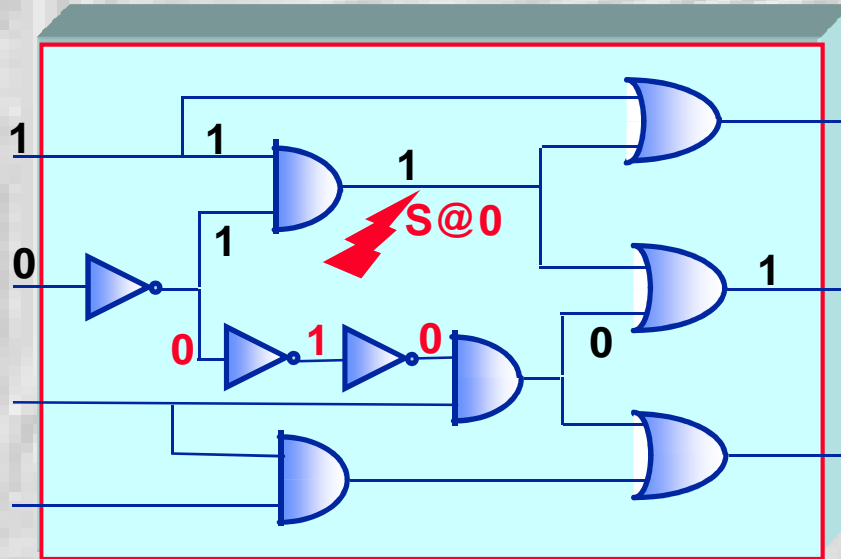


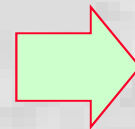- ATPG / Backtrack
- FC < Desired FC (98%)
- Modify the Structure




**Design For Test**

## Combinational Logic

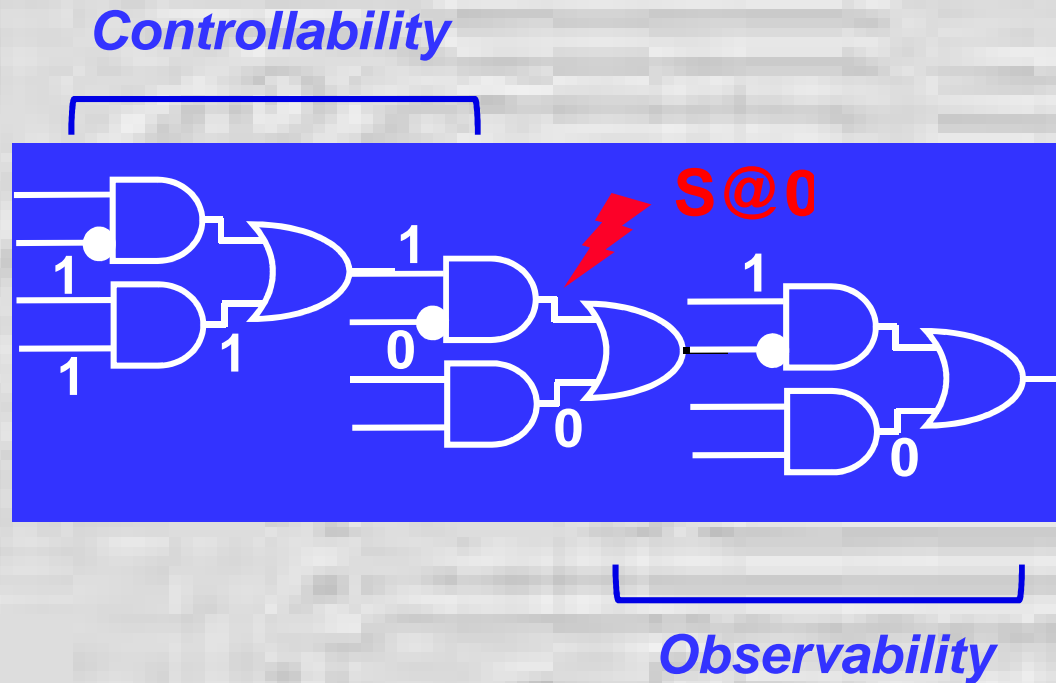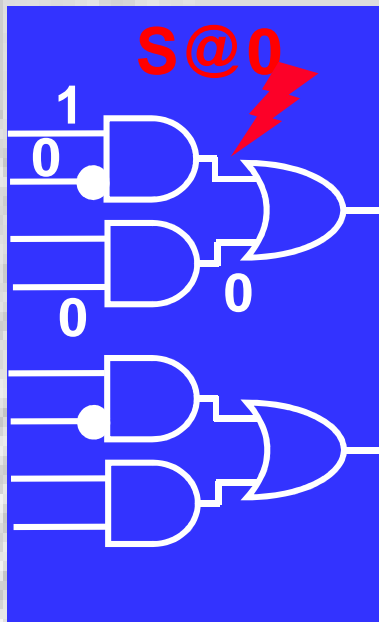

# Structured DFT

## Sequential Logic

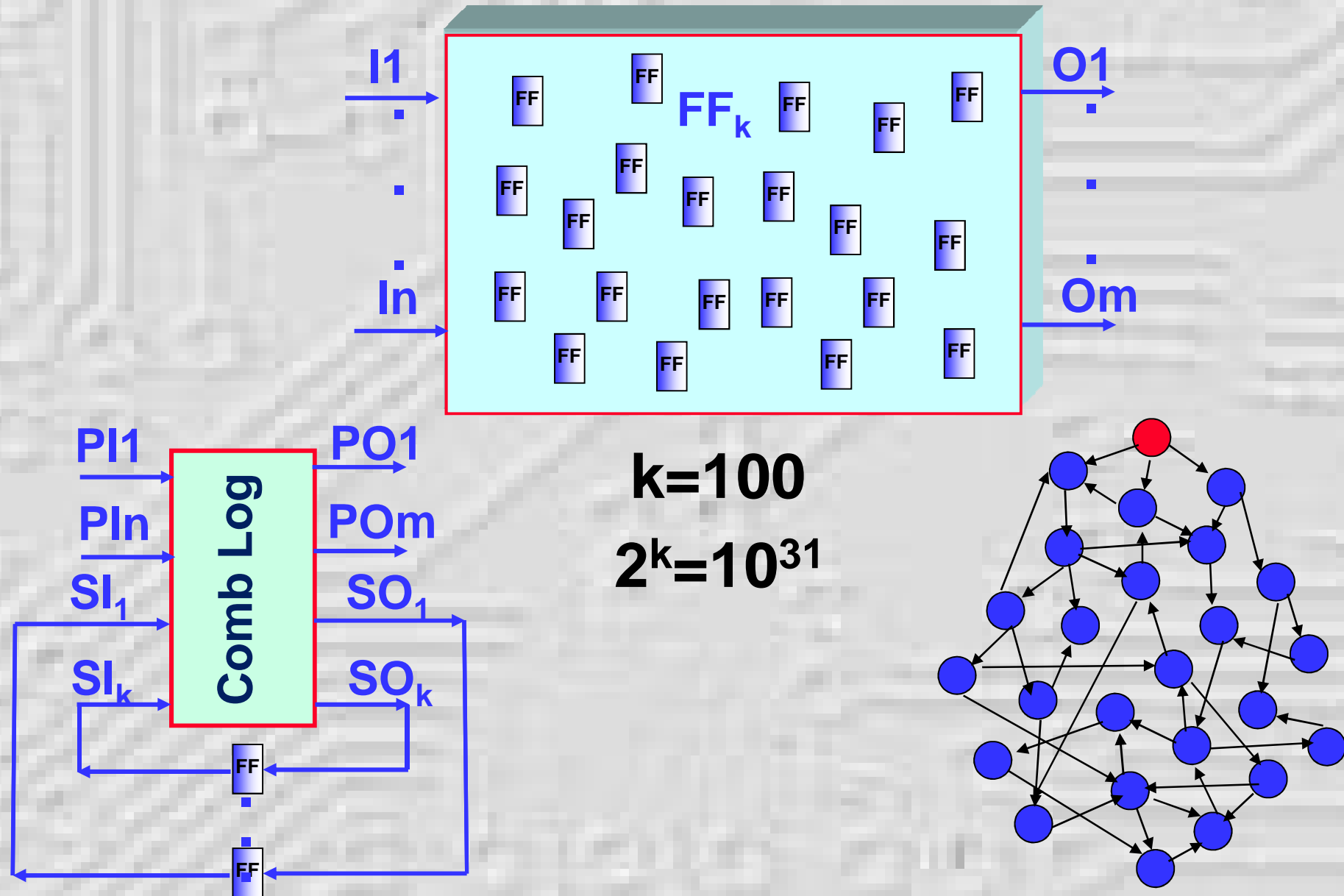




# Structured DFT


IN2P3

## Sequential Logic

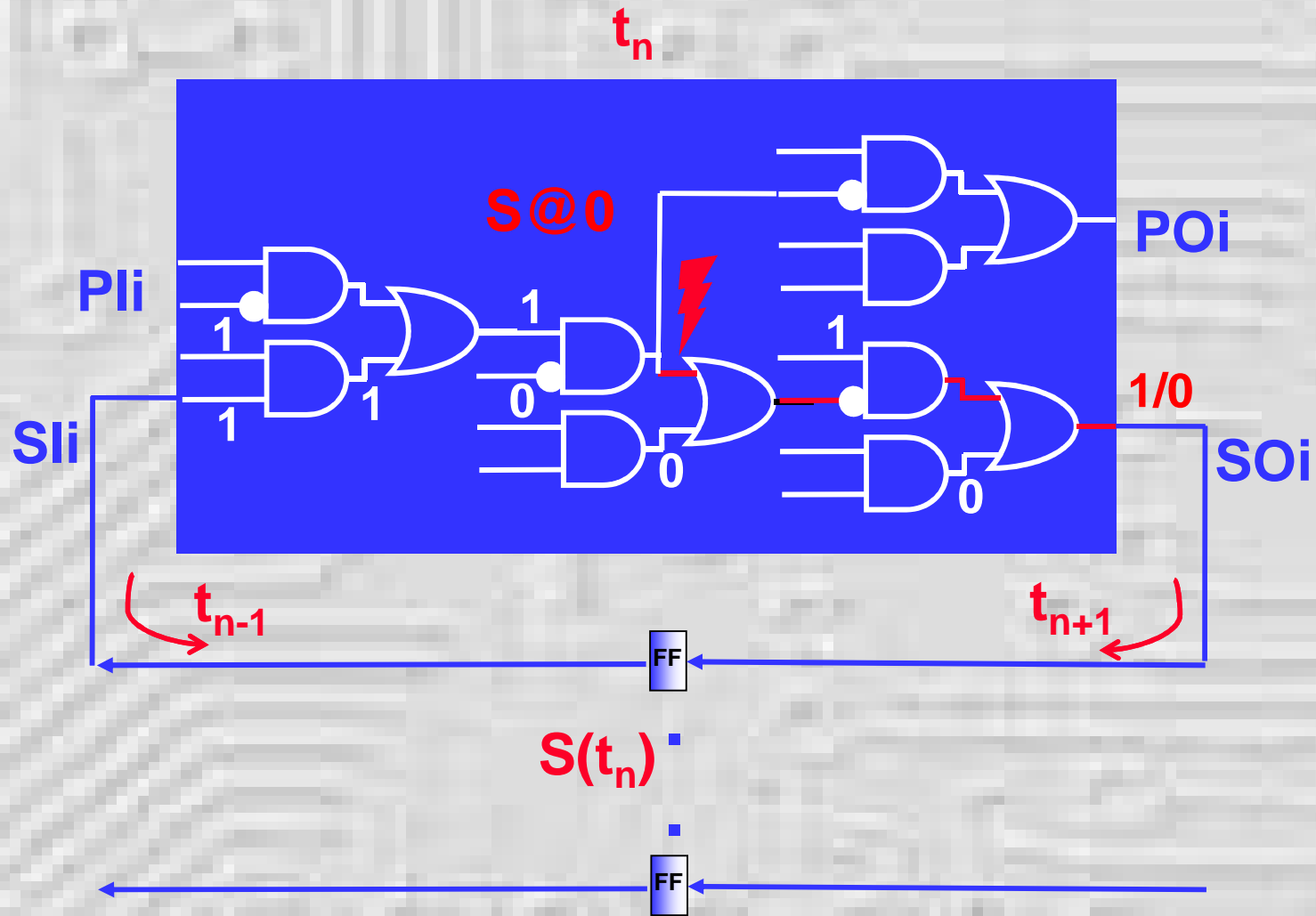


# Structured DFT

IN2P3

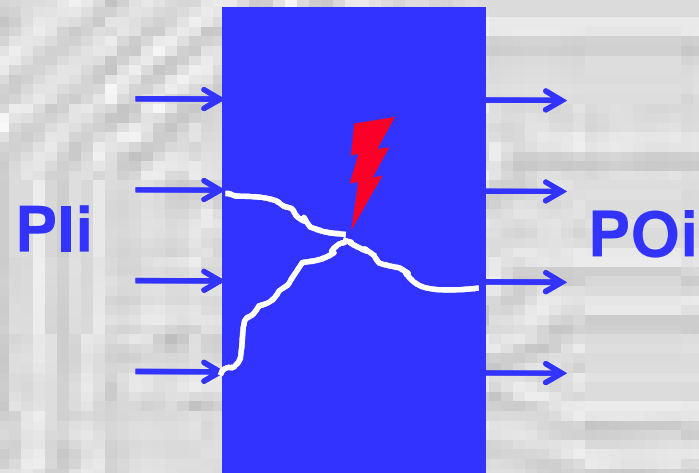


## Sequential Logic

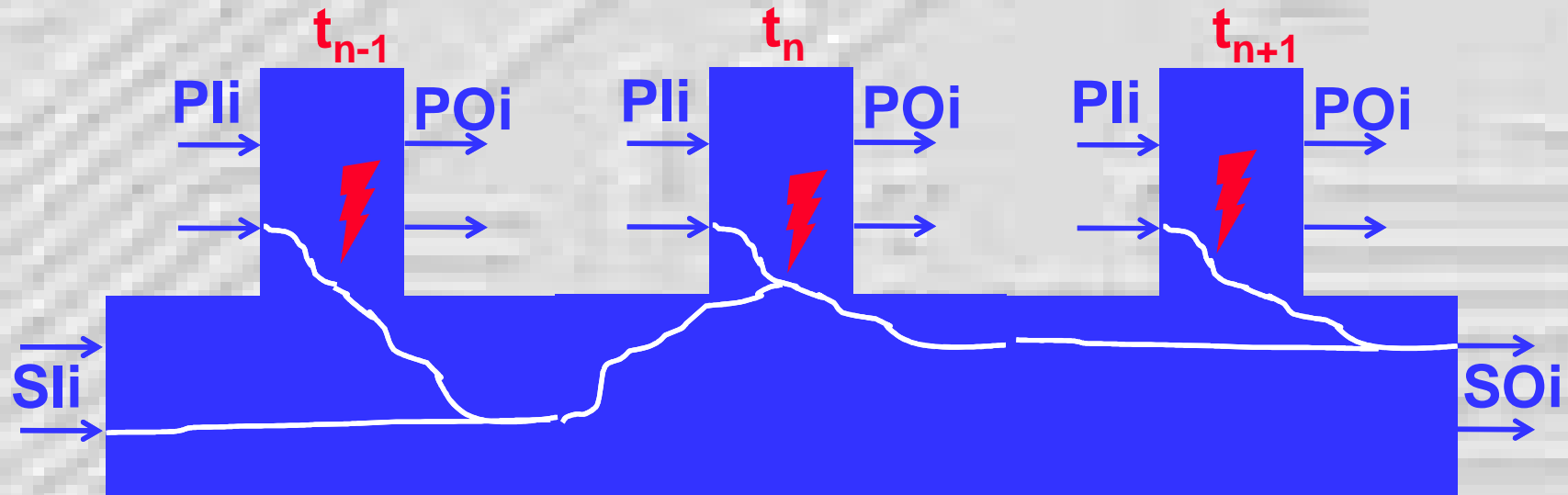


**ATPG unfeasible**

# Structured DFT

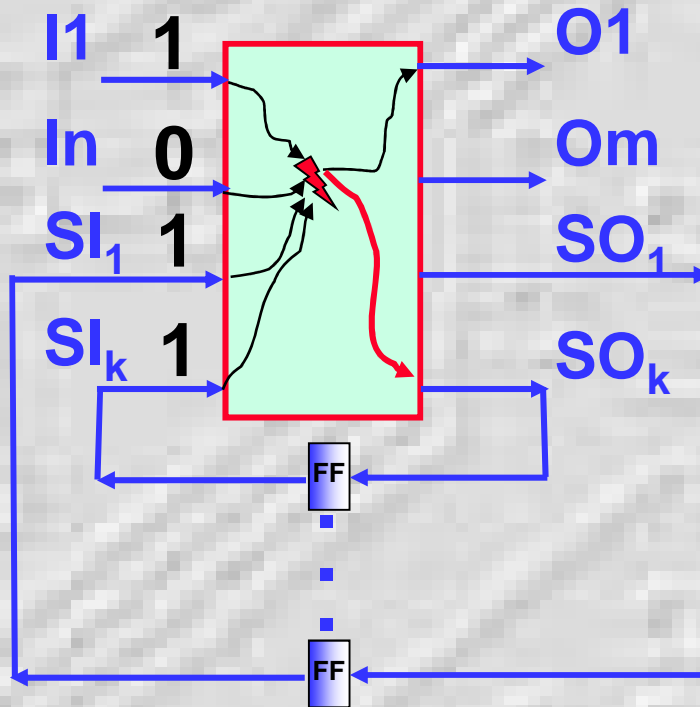

$L_{seq} = 10^7 \times L_{comb}$

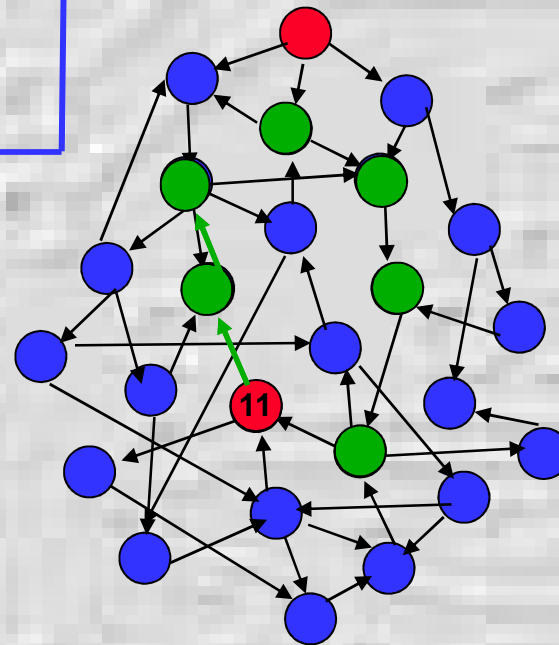


$k=100$

$2^k=10^{31}$


$N_T=2^{k/4}$   
 $\sim 10^7$

# Structured DFT

IN2P3

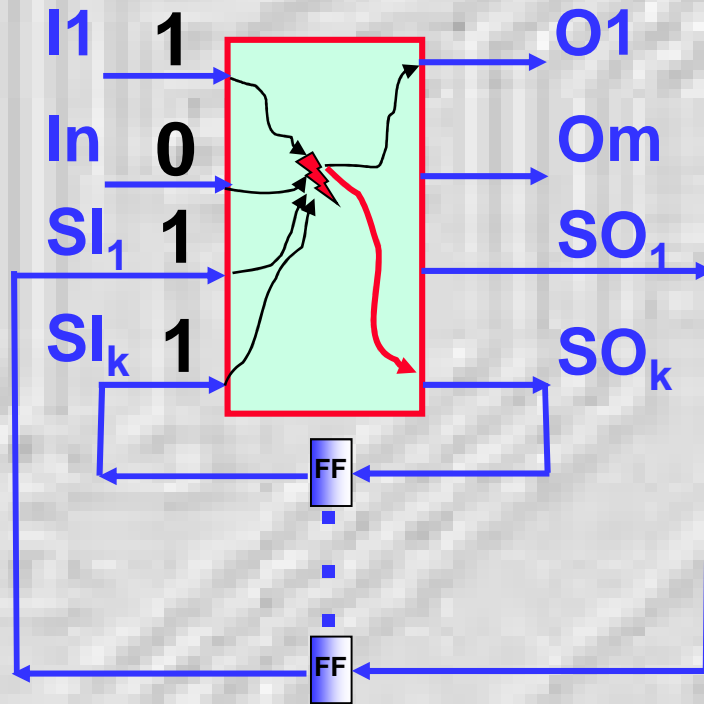

## Combinational ATPG



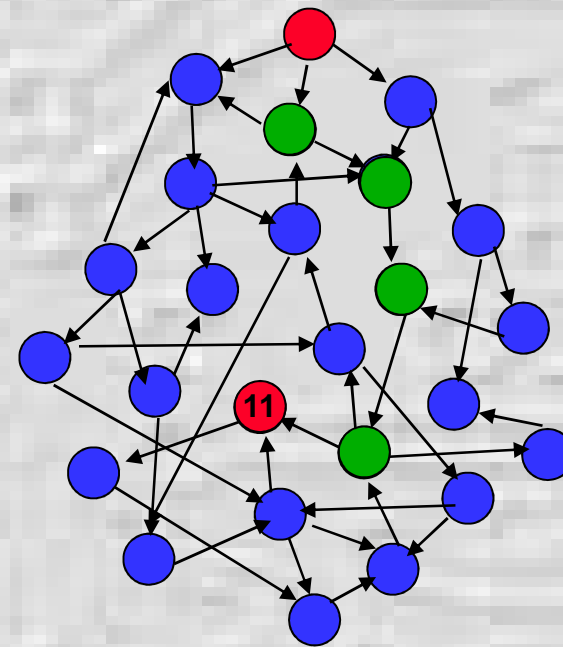


$$k=100$$



$$2^k=10^{31}$$

$$N_T=2^{k/4}$$
$$\sim 10^7$$

# Structured DFT

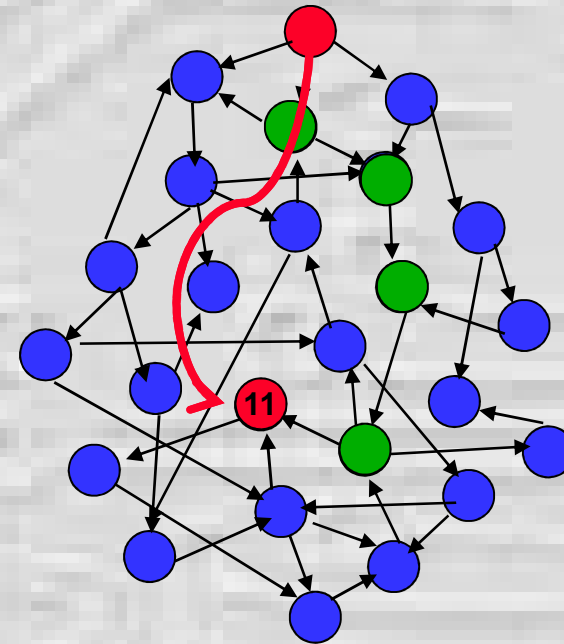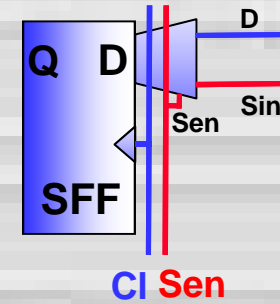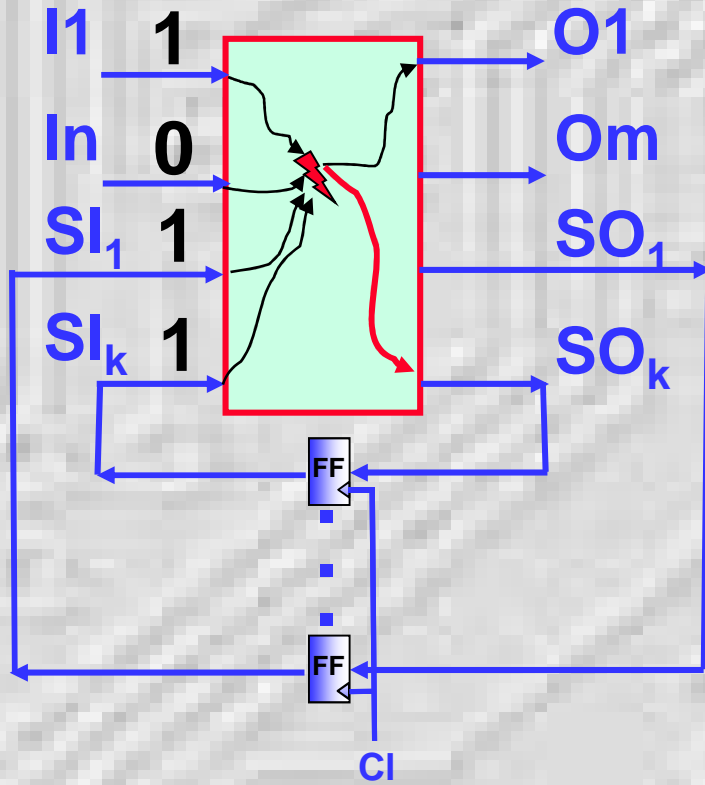



# Structured DFT

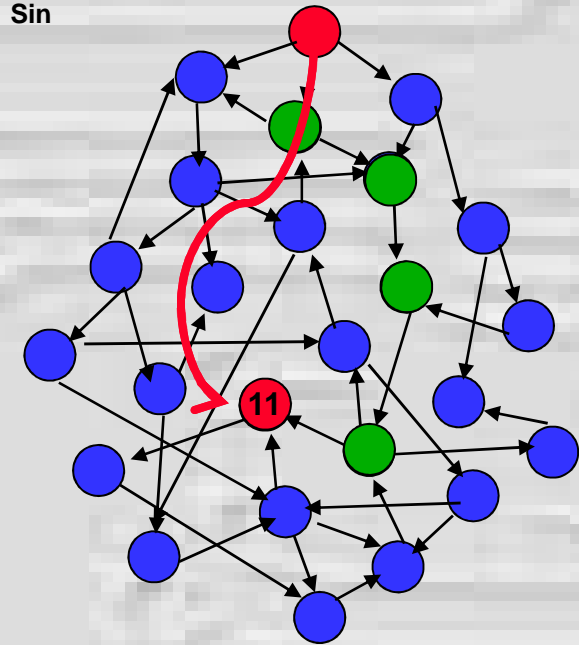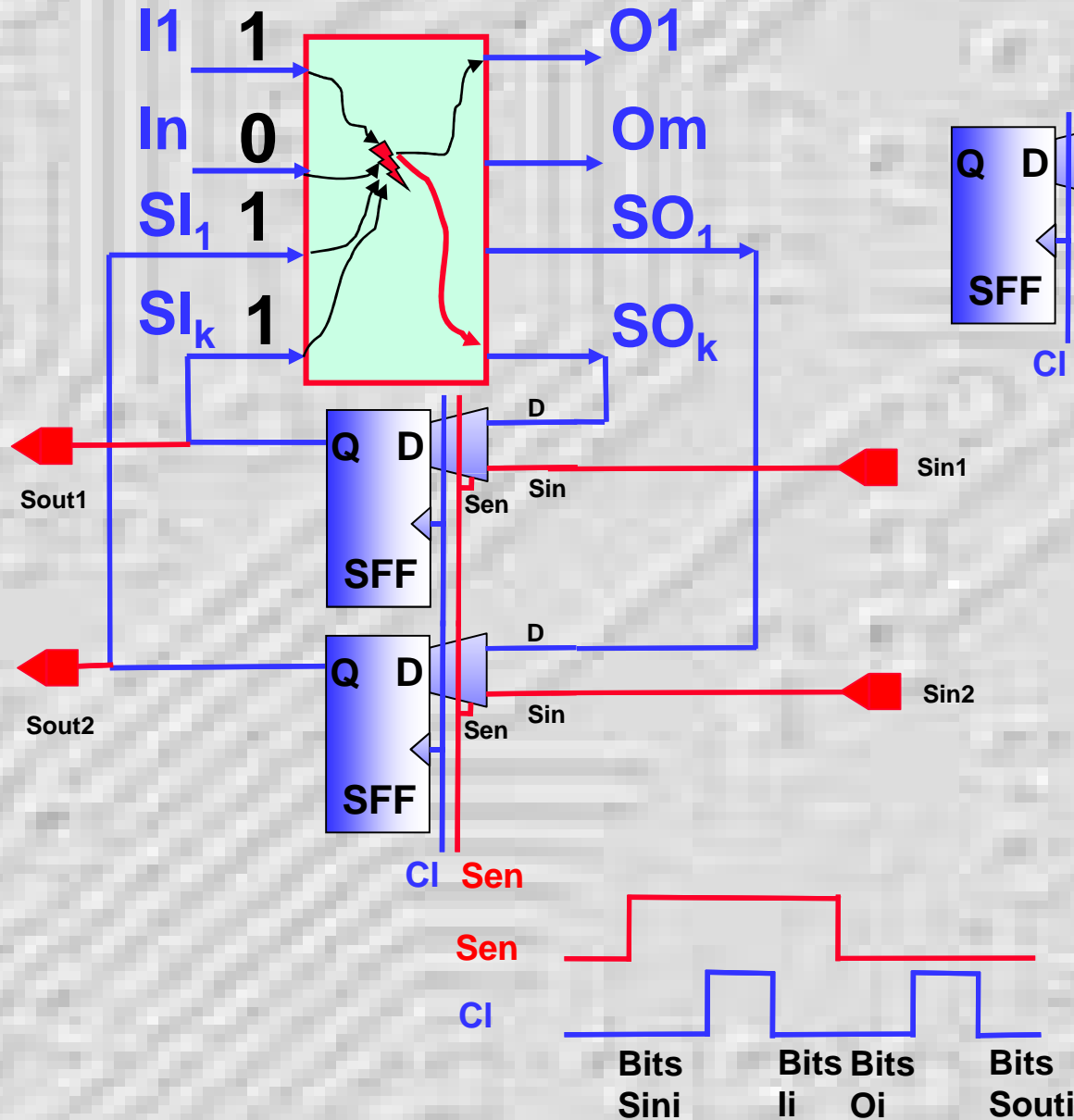


- $L_{seq} = 2 \times L_{comb}$
- $N_{pin} = 2k+1$

# Structured DFT

## SCAN Design

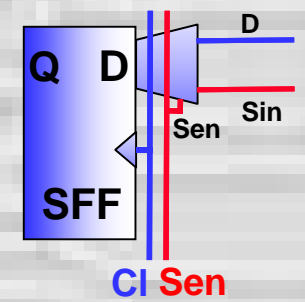
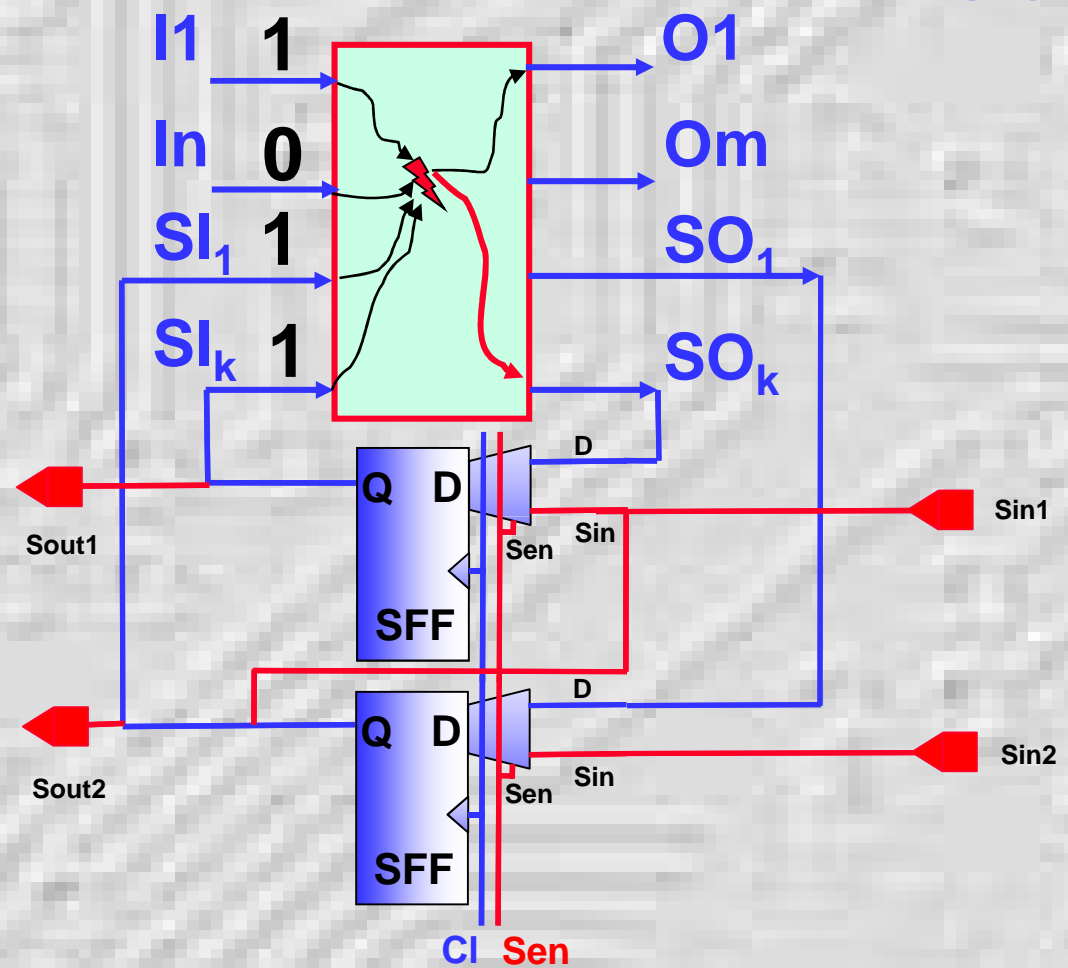


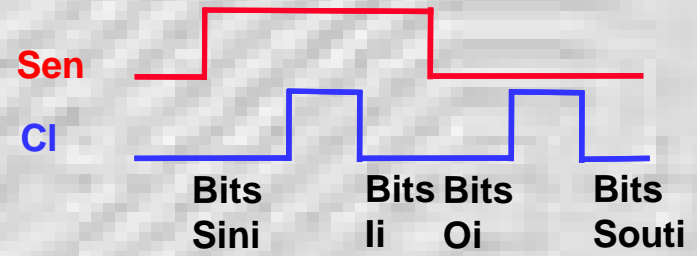- $L_{seq} = k \times L_{comb}$
- $N_{pin} = 2+1$




# Structured DFT

## Sequential Logic

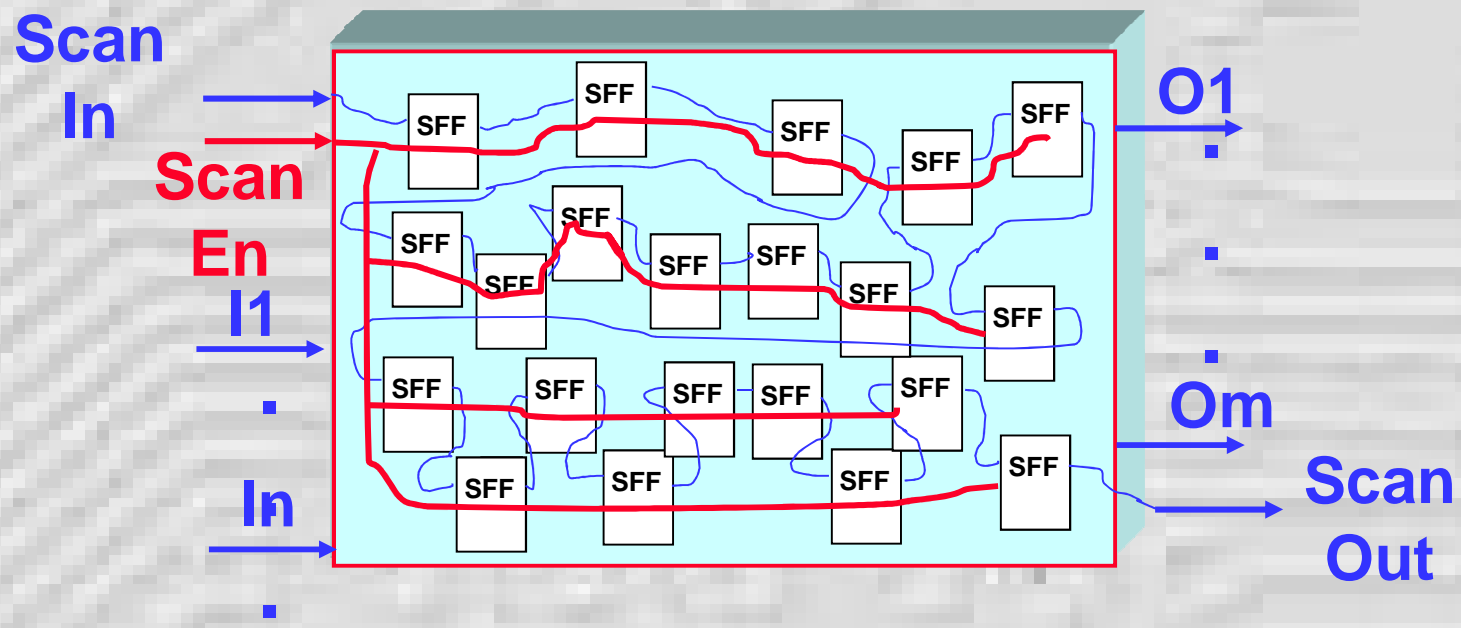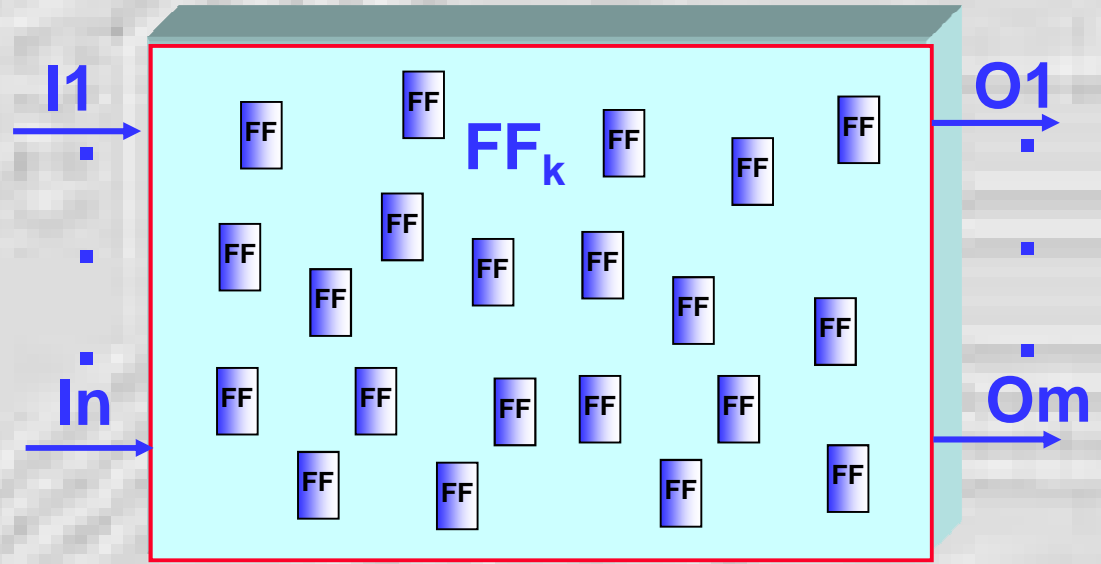




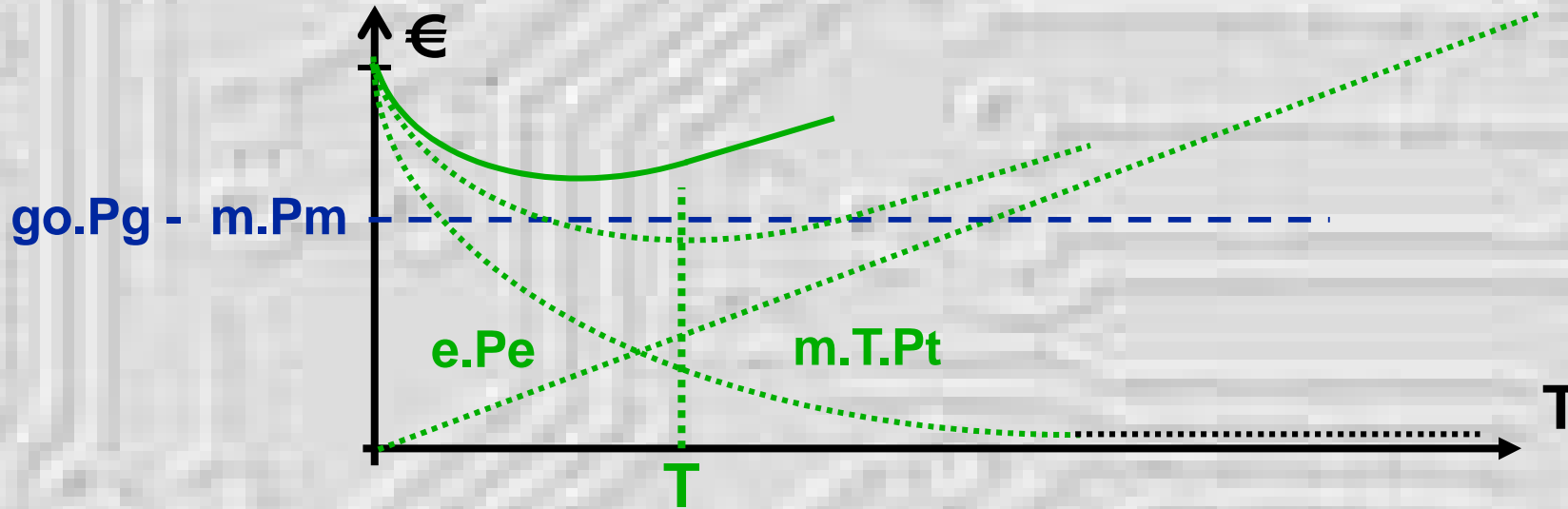

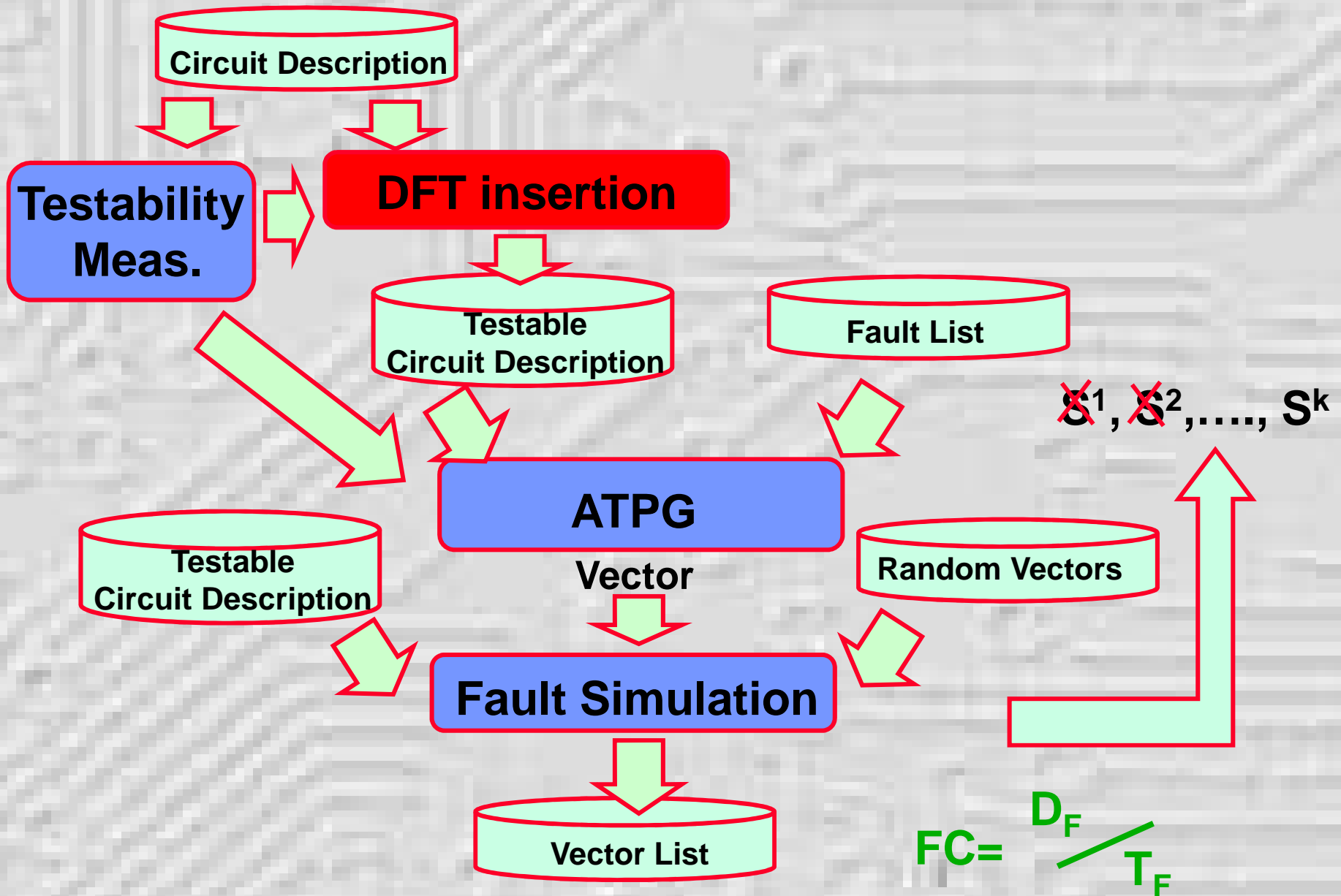**III) Criteria to make circuit Testable**  
**=> Propose circuit modifications**






***Built –In  
Self-Test***


# BIST

IN2P3




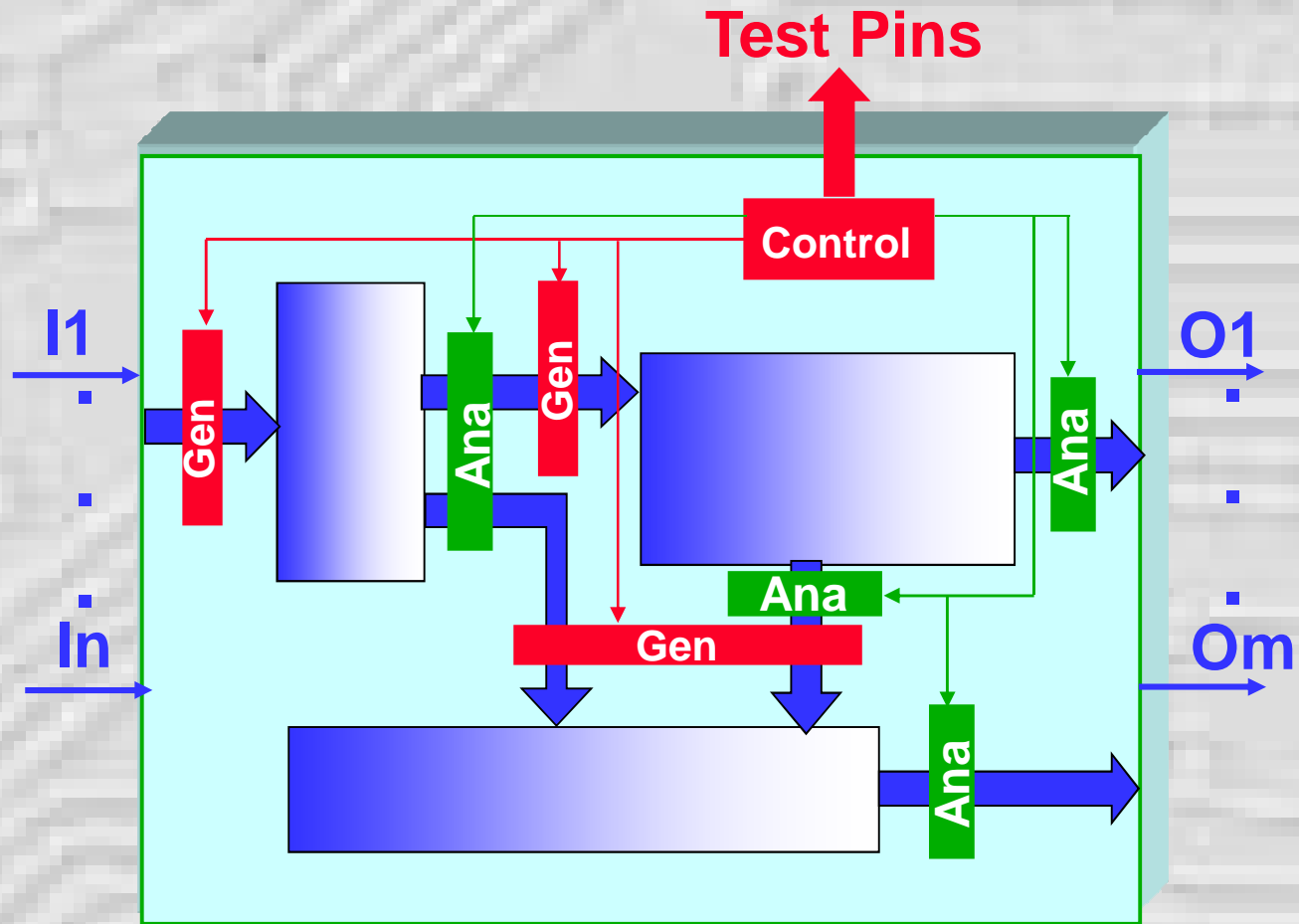


# BIST

IN2P3

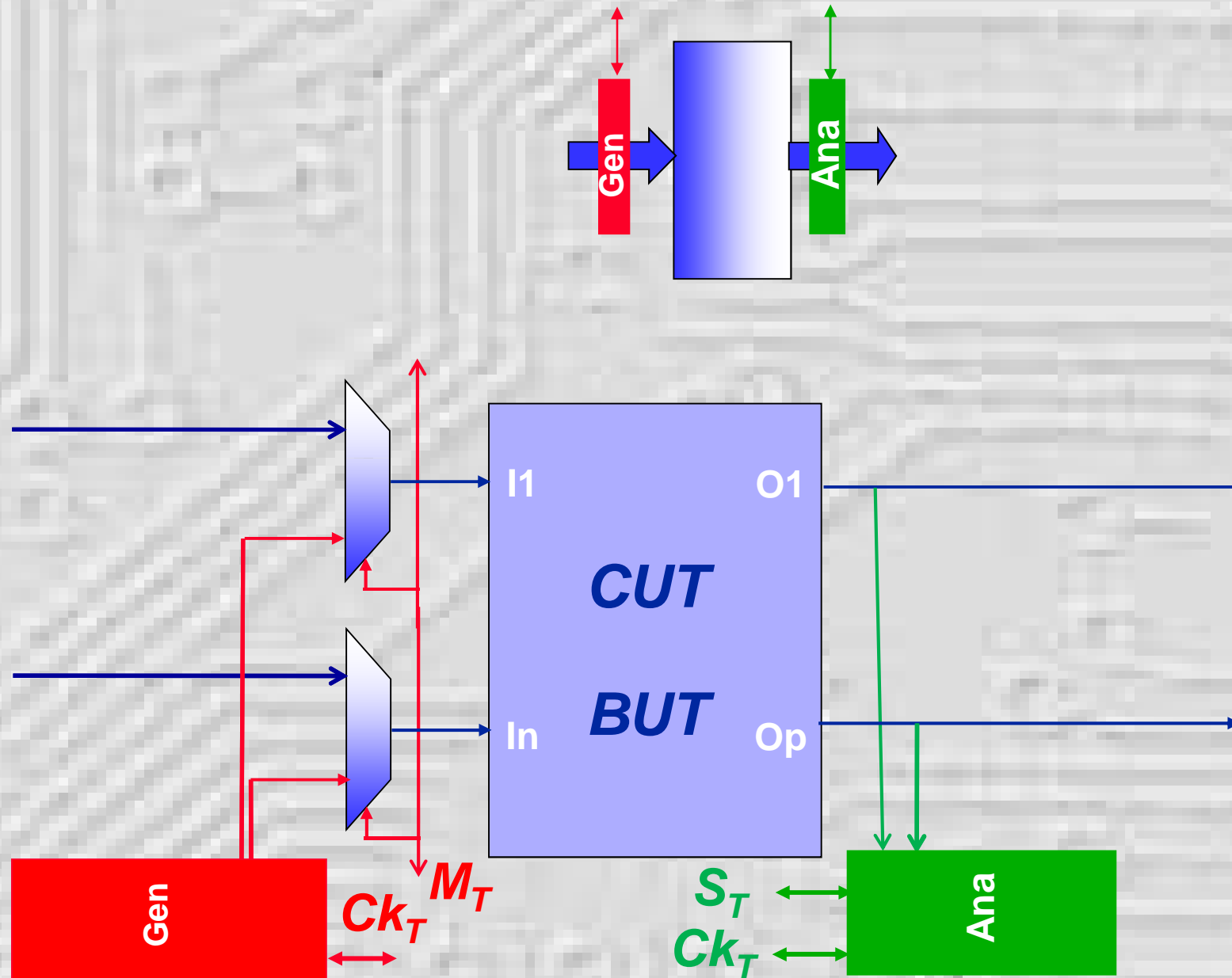


# BIST

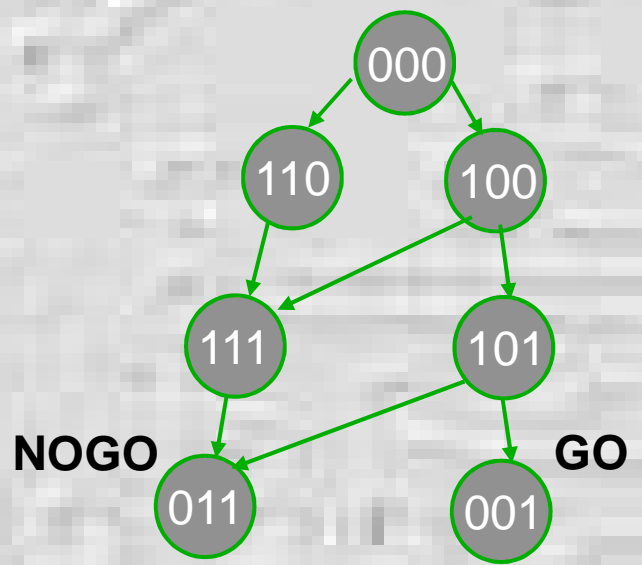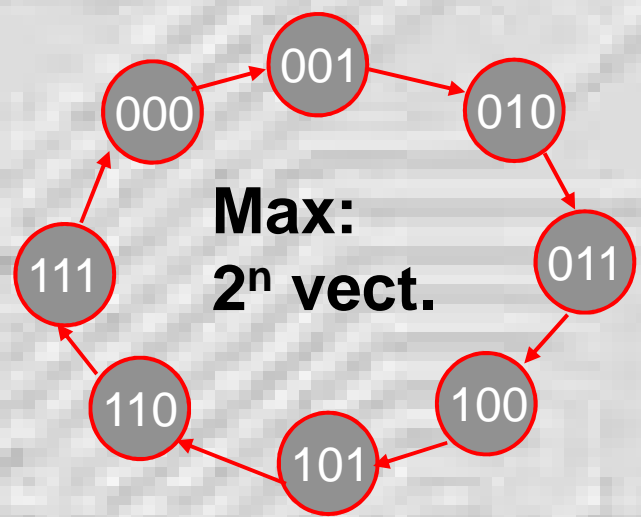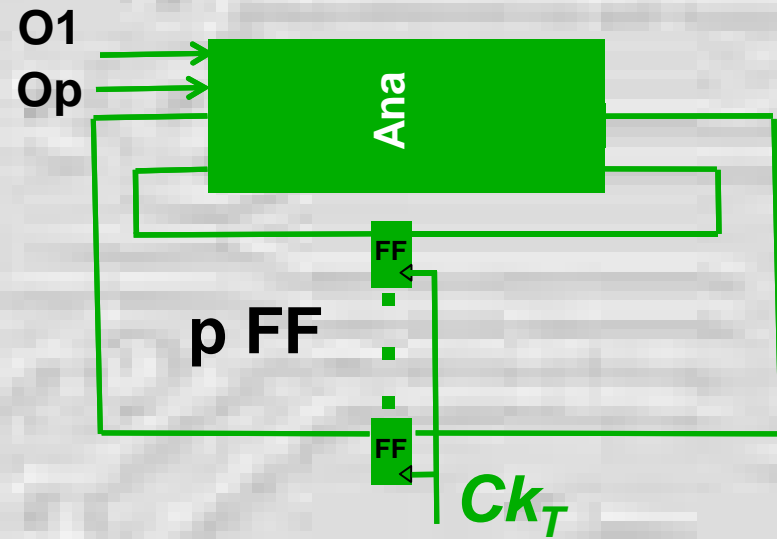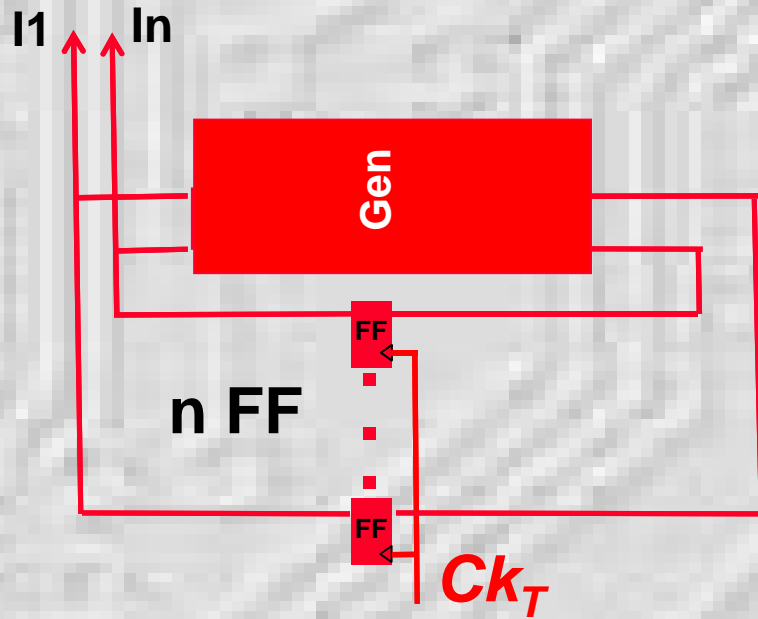


# BIST

IN2P3

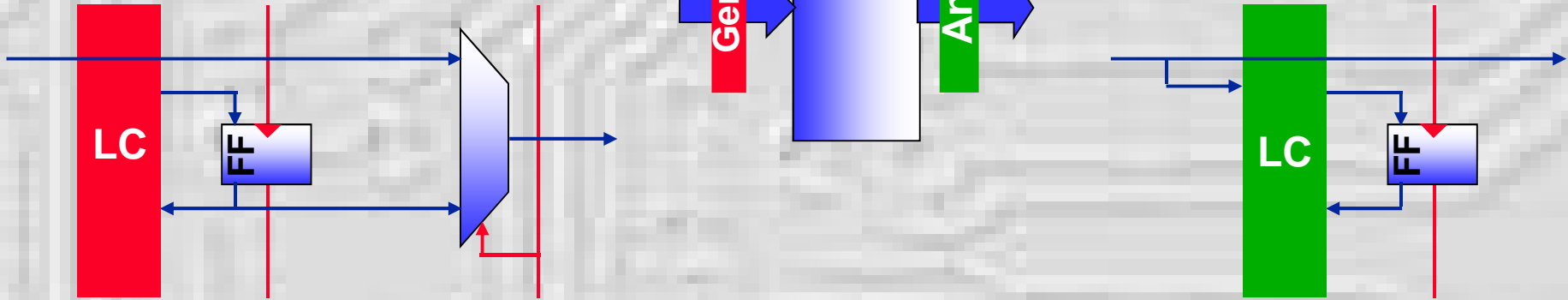


n FF  
Max:  
2<sup>n</sup> vect.

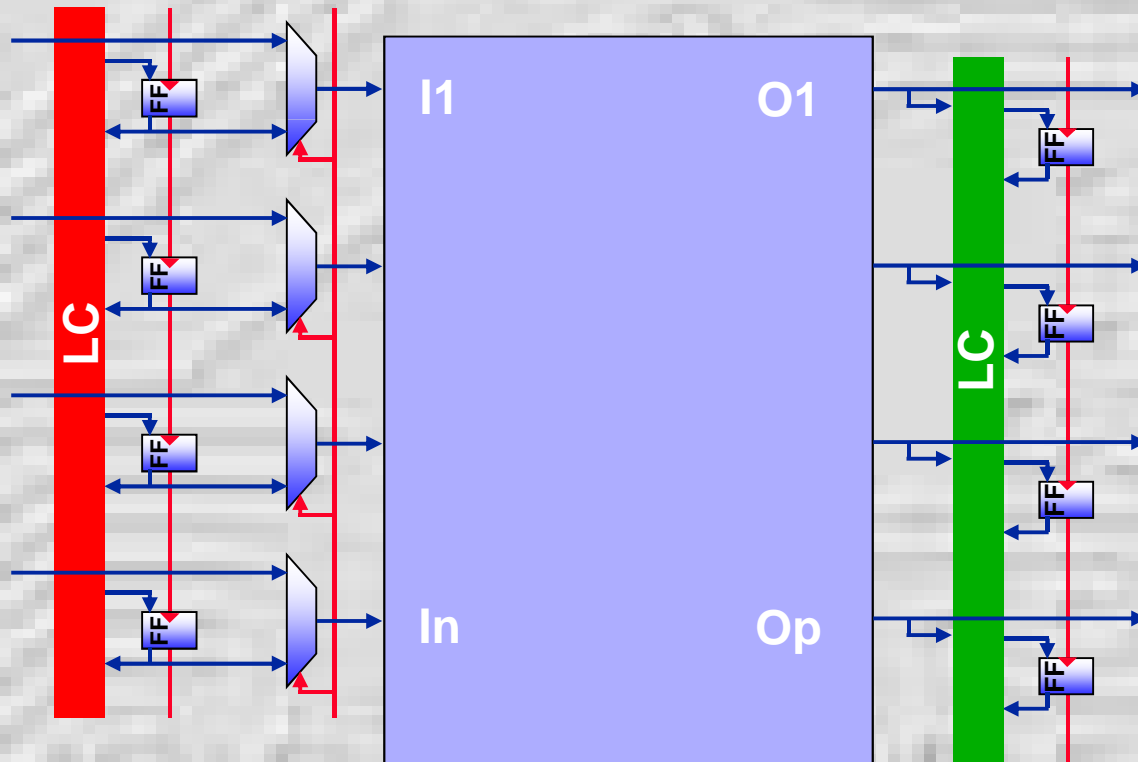

# BIST



IN2P3

Counter

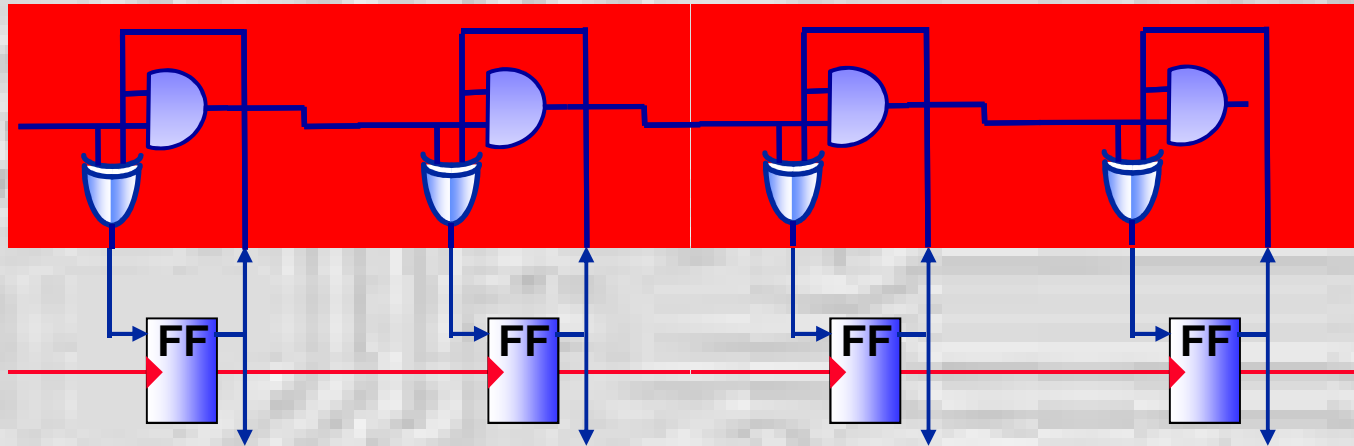

Max:  
 $2^4$  vect.

Feedback  
Shift  
Register

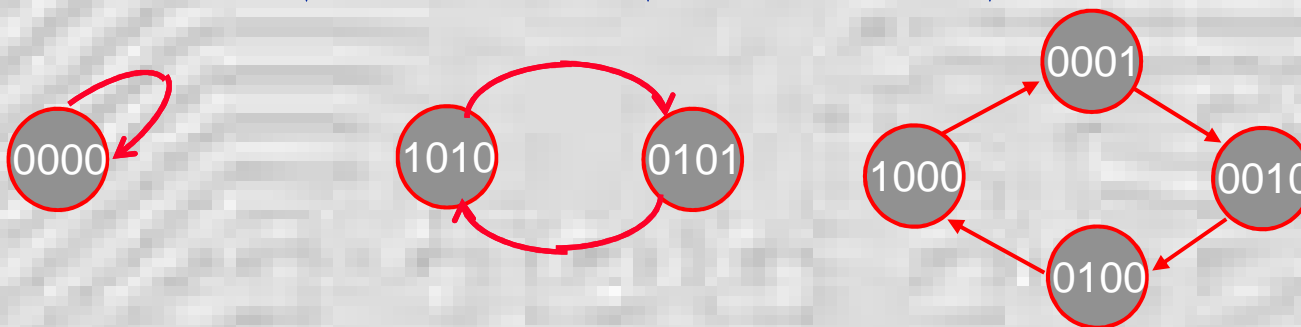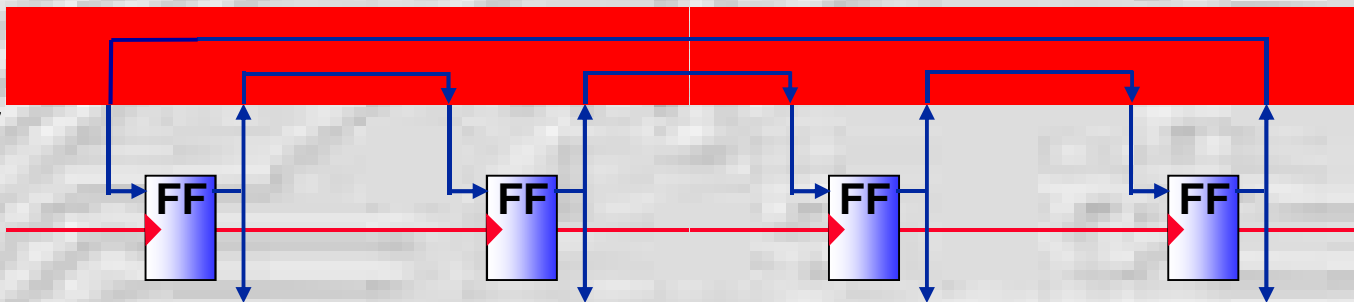




# BIST


IN2P3

Feedback  
Shift  
Register

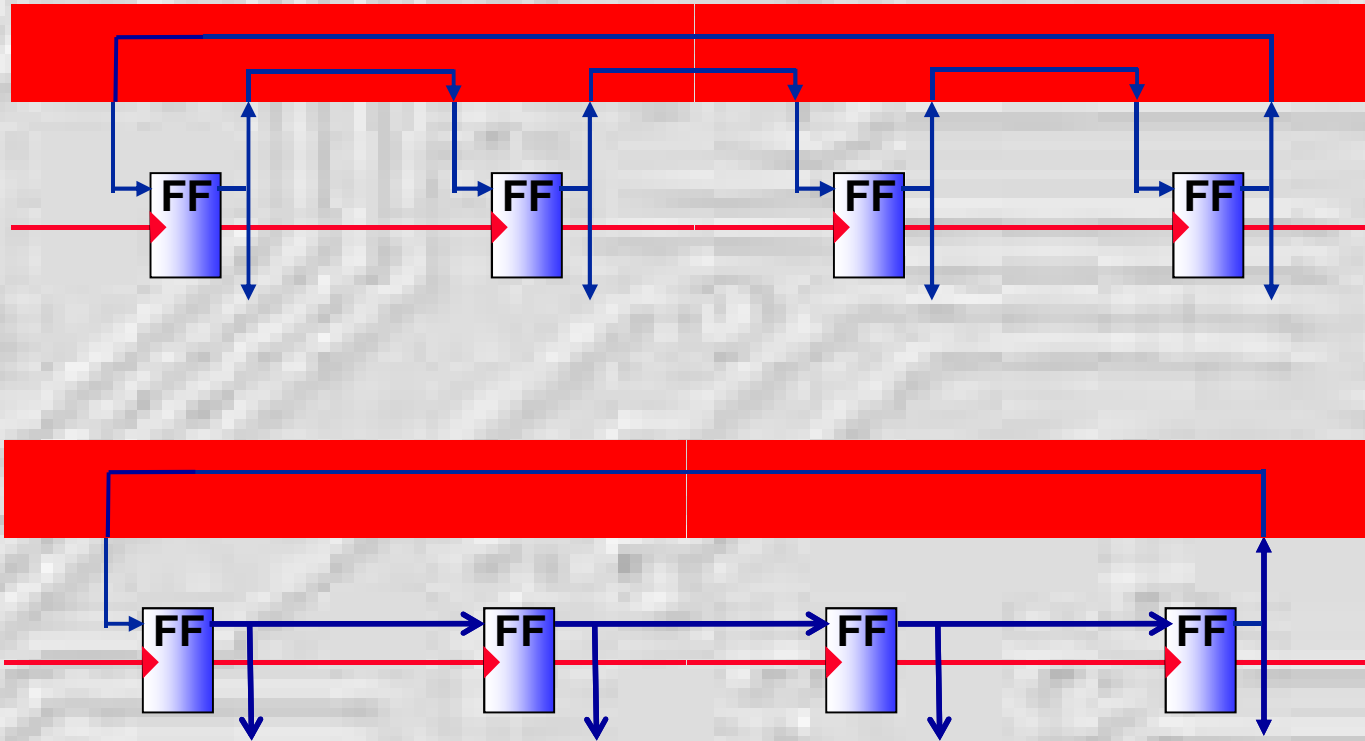

# BIST


IN2P3

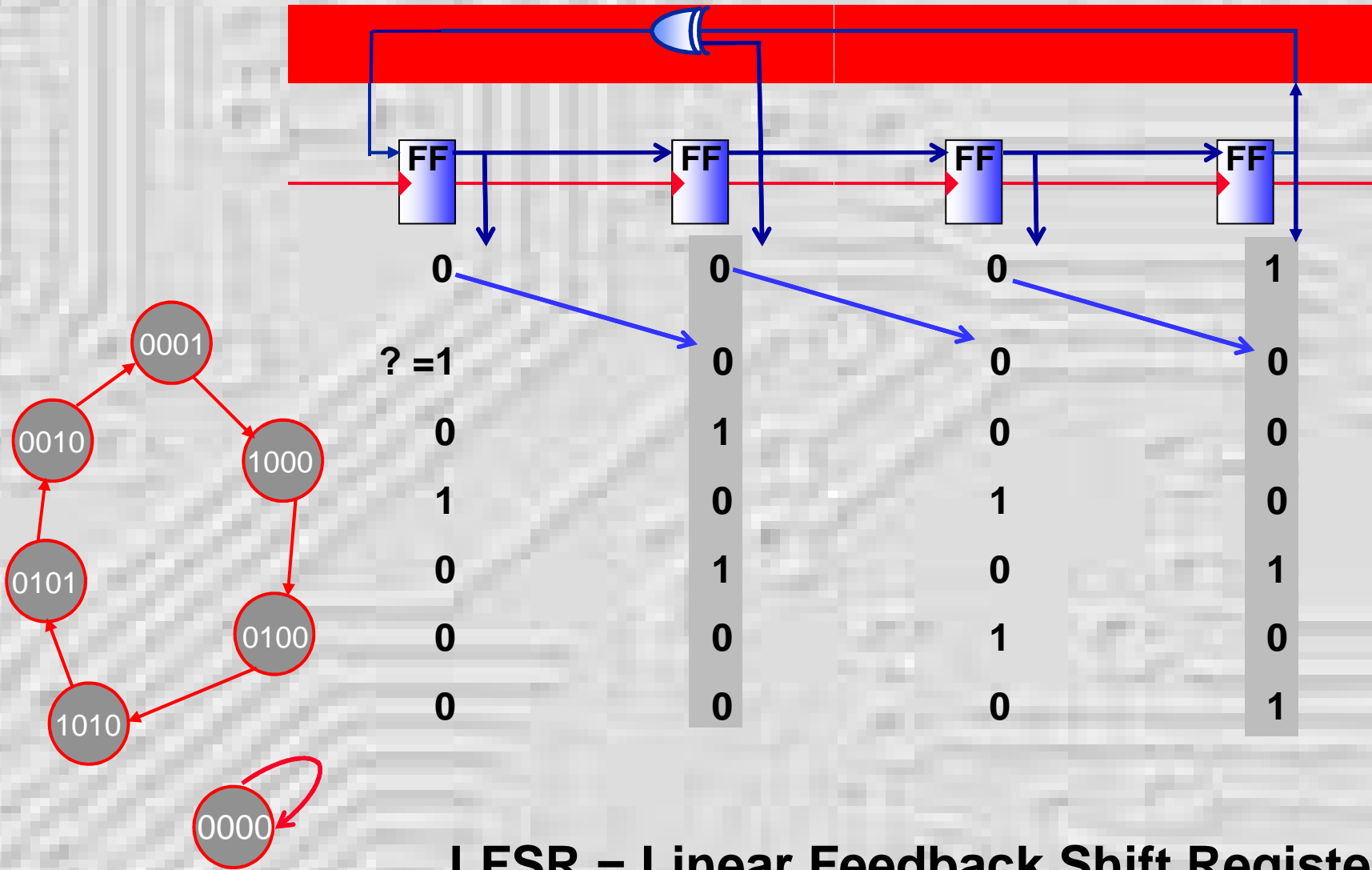

LFSR = Linear Feedback Shift Register

# BIST

IN2P3

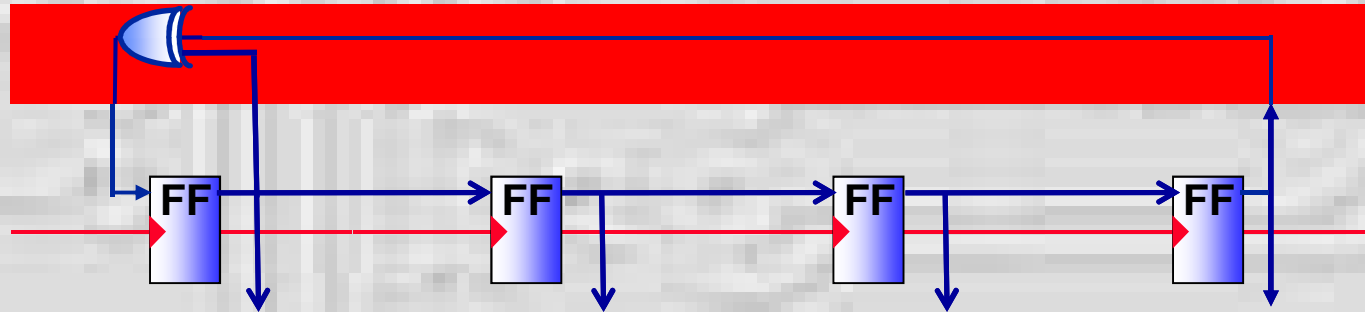


$2^4 - 1$   
Vectors !


0	0	0	1
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
1	0	1	1
0	1	0	1
1	0	1	0
1	1	0	1
0	1	1	0
0	0	1	1
1	0	0	1
0	1	0	0
0	0	1	0
0	0	0	1

# BIST

LFSR2  
15 vect.

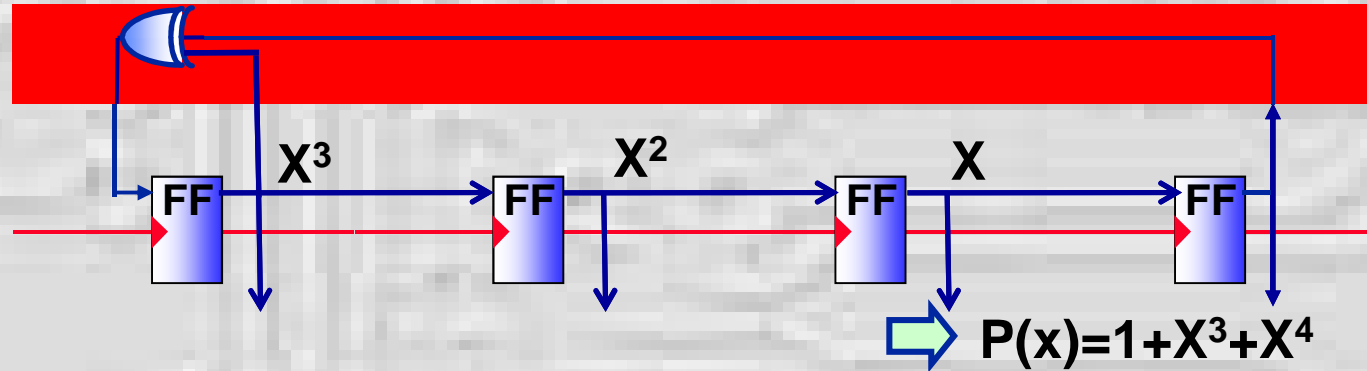

LFSR1  
6 vect.

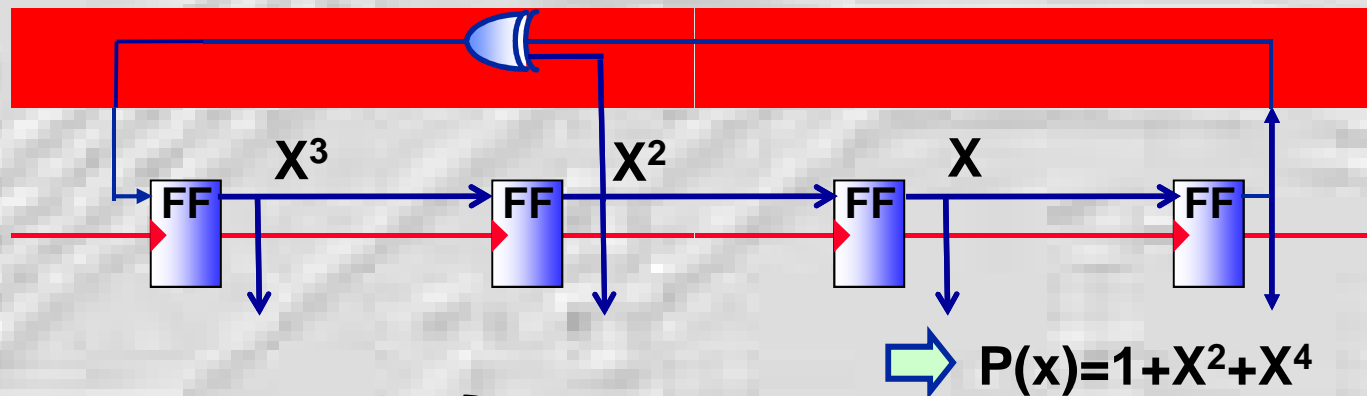

$P(X) = \sum X_i$  with  $X$  in  $B = \{0,1\}$

XOR, AND      Galois Field

Primitive  $P(x) \Rightarrow 2^n - 1$

$$\begin{array}{r|l}
 X^4 + X^2 + 1 & X^2 + X + 1 \\
 \hline
 X^4 + X^3 + X^2 & \\
 \hline
 X^3 + 1 & \\
 X^3 + X^2 + X & \\
 \hline
 X^2 + X + 1 & \\
 X^2 + X + 1 & \\
 \hline
 0 &
 \end{array}$$


degré					degré					degré				
1	0				13	4	3	1	0	25	3	0		
2	1	0			14	12	11	1	0	26	8	7	1	0
3	1	0			15	1	0			27	8	7	1	0
4	1	0			16	5	3	2	0	28	3	0		
5	2	0			17	3	0			29	2	0		
6	1	0			18	7	0			30	16	15	1	0
7	1	0			19	6	5	1	0	31	3	0		
8	6	5	1	0	20	3	0			32	28	27	1	0
9	4	0			21	2	0			33	13	0		
10	3	0			22	1	0			34	15	14	1	0
11	2	0			23	5	0			35	2	0		
12	7	4		0	24	4	3	1	0	36	11	0		

$$P(x) = x^{34} + x^{15} + x^{14} + x + 1$$

$$P(x) = x^{22} + x + 1$$


# BIST

IN2P3

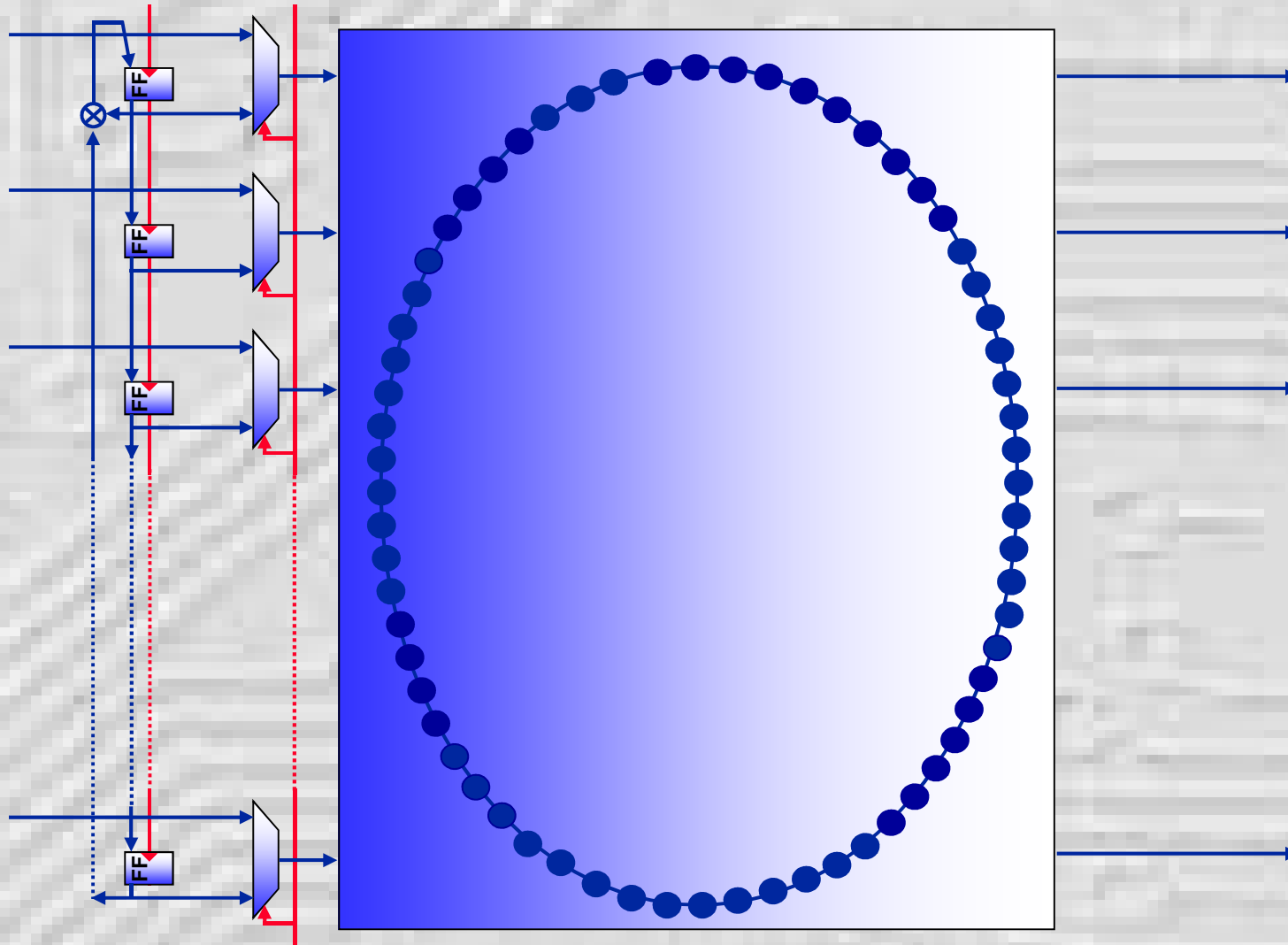

# BIST

IN2P3

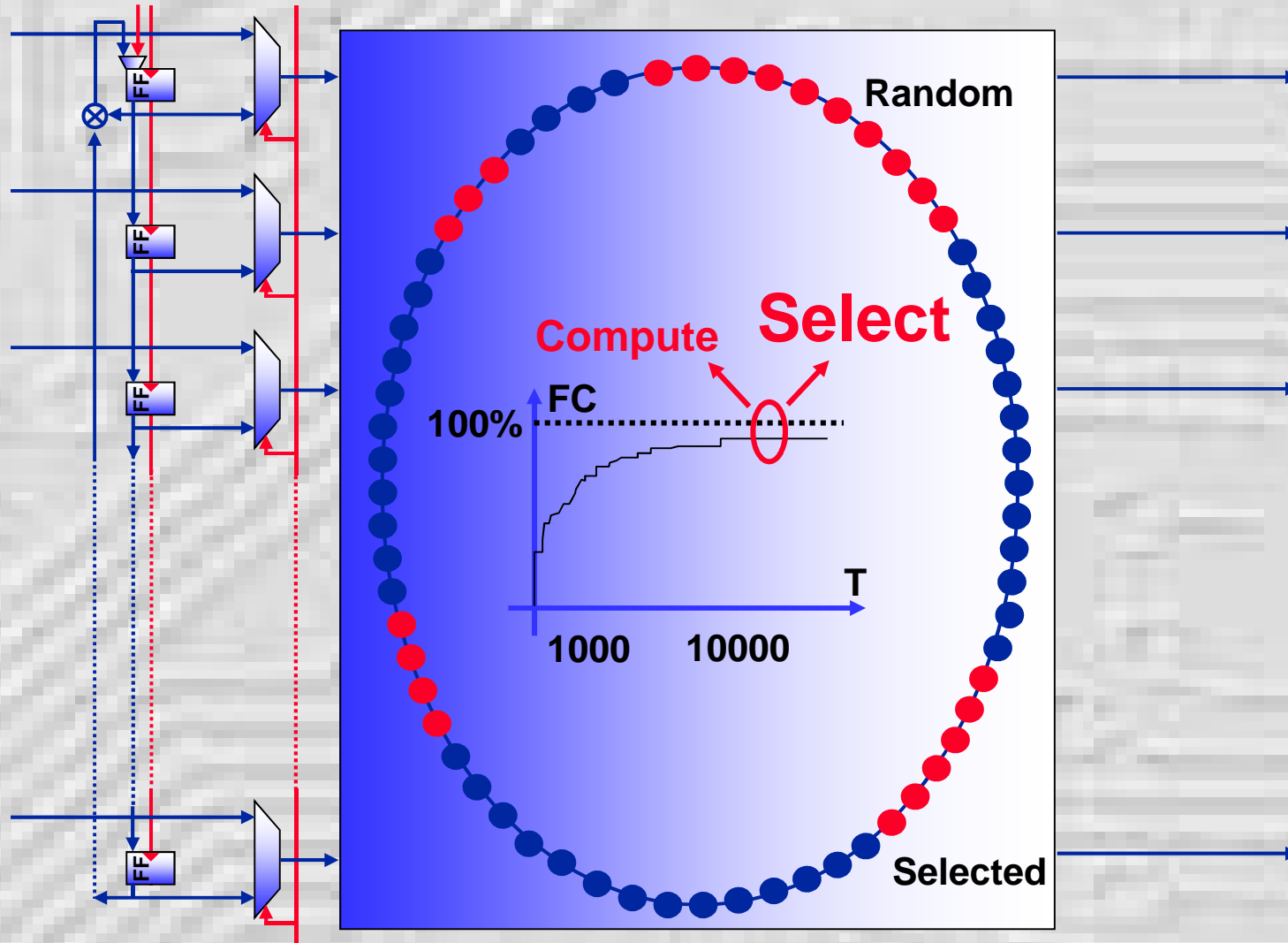


■ Test Length<sup>2</sup>

■ Seed/Clock

■ Reconf Polyn


# BIST

IN2P3

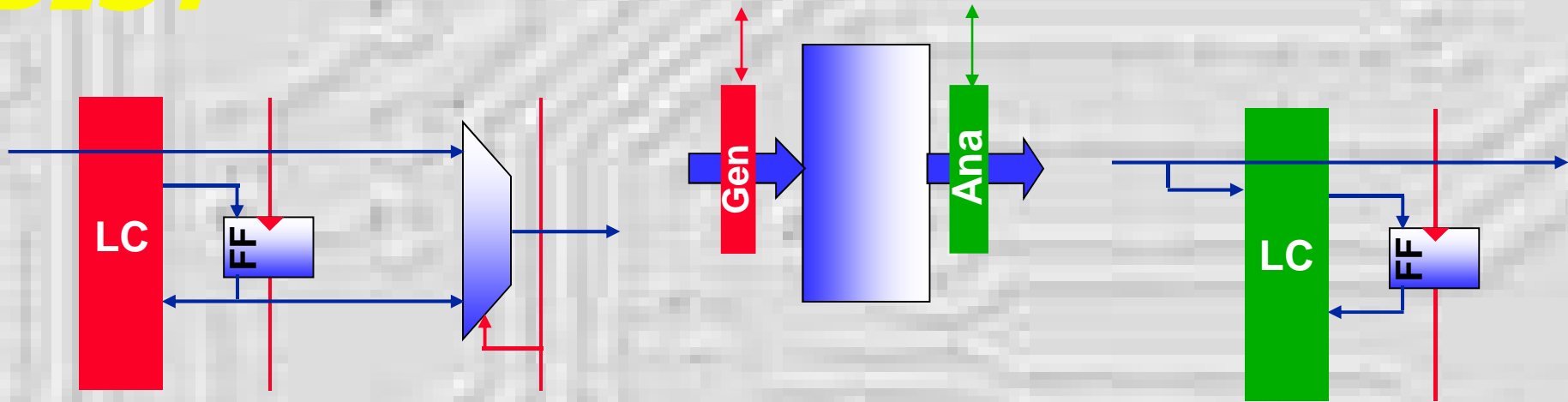

n FF




Max:  
2<sup>n</sup> vect.

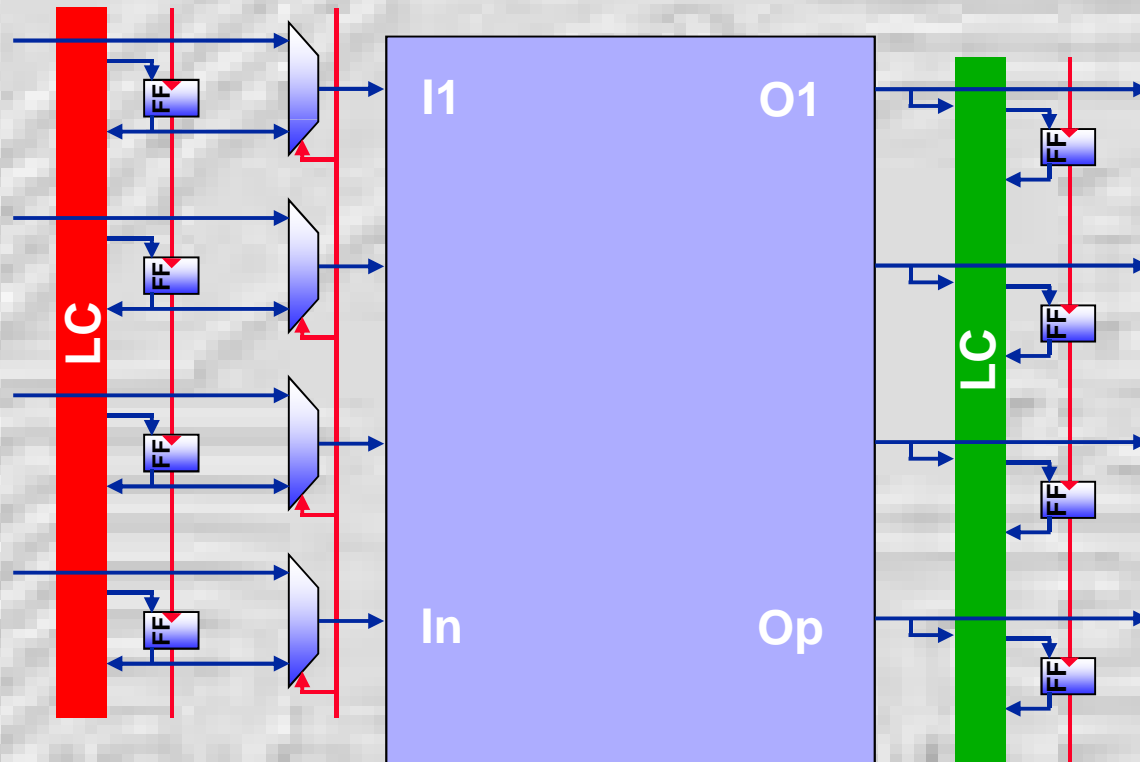



# BIST


IN2P3

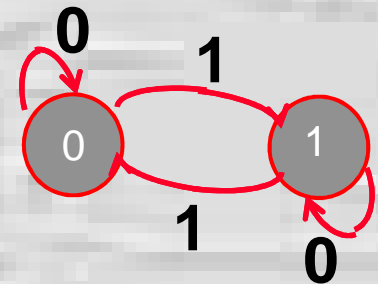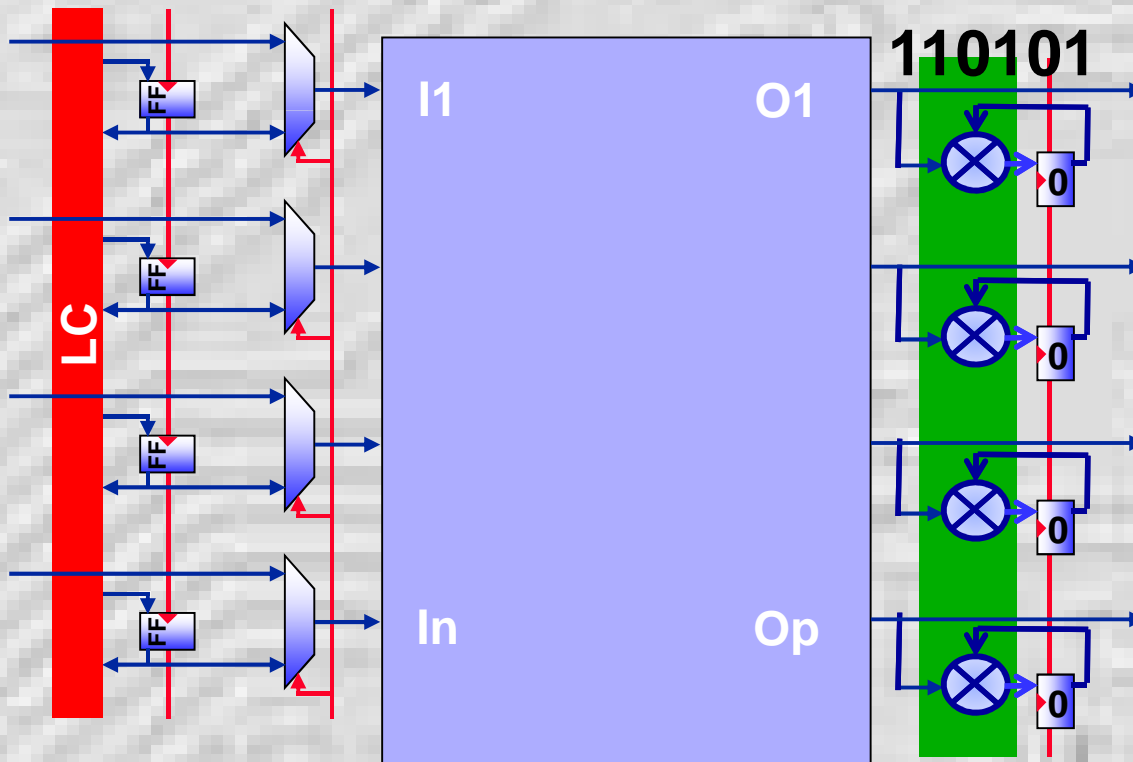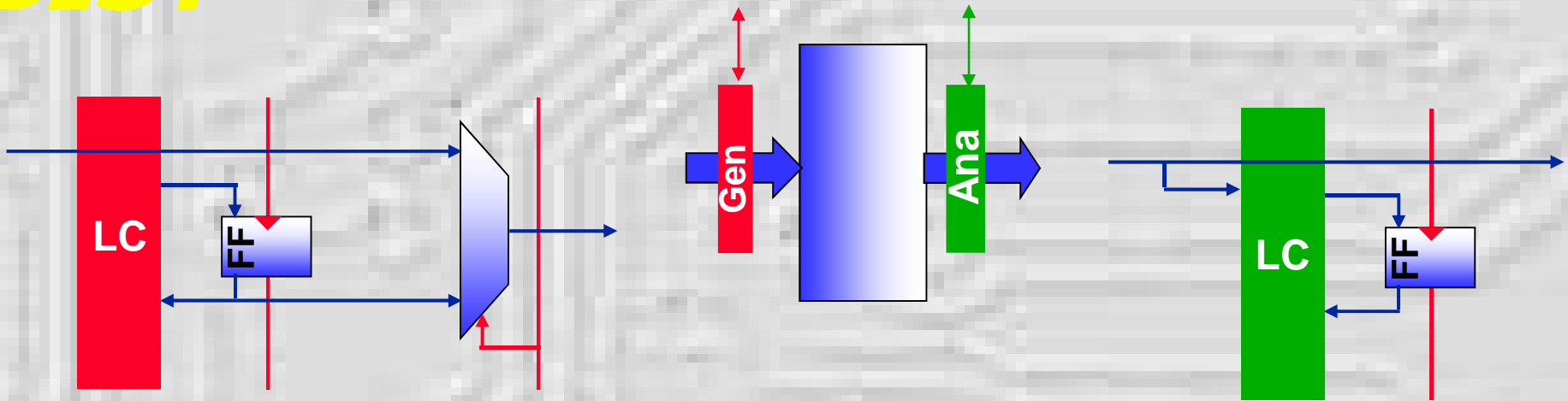


Aliasing  
 $P=1/2$

# BIST

Internal  
LFSR  
 $P(x)=1+X^2+X^4$

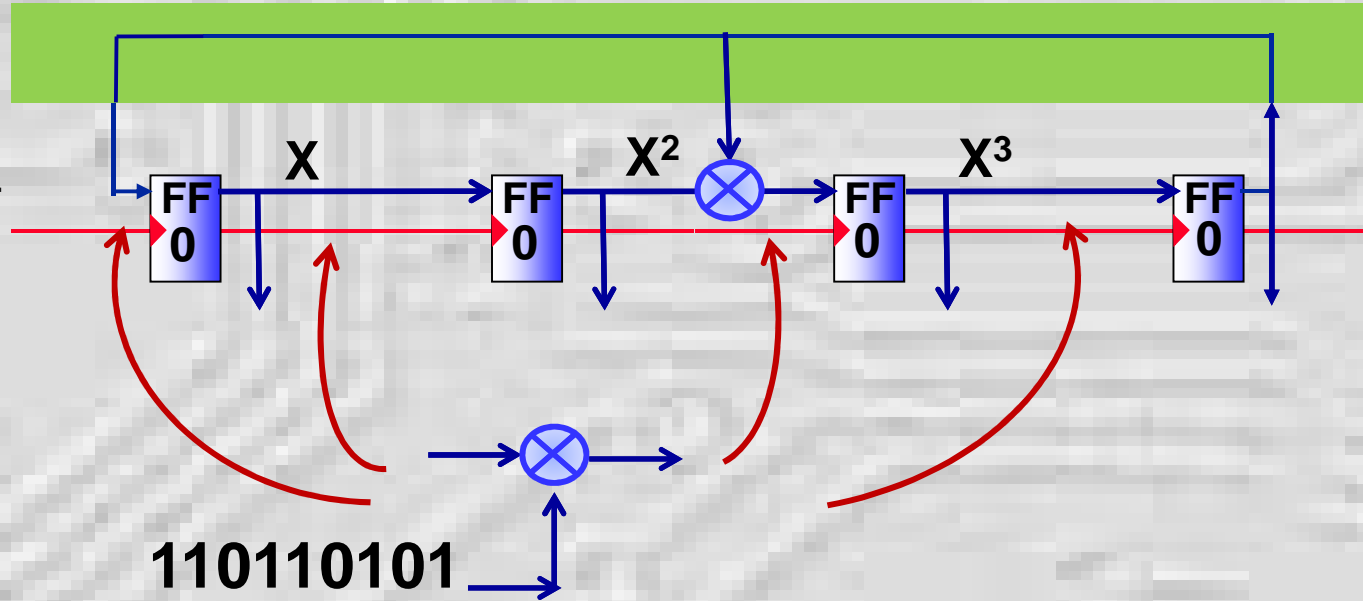


$P(x)=1+X^2+X^4$

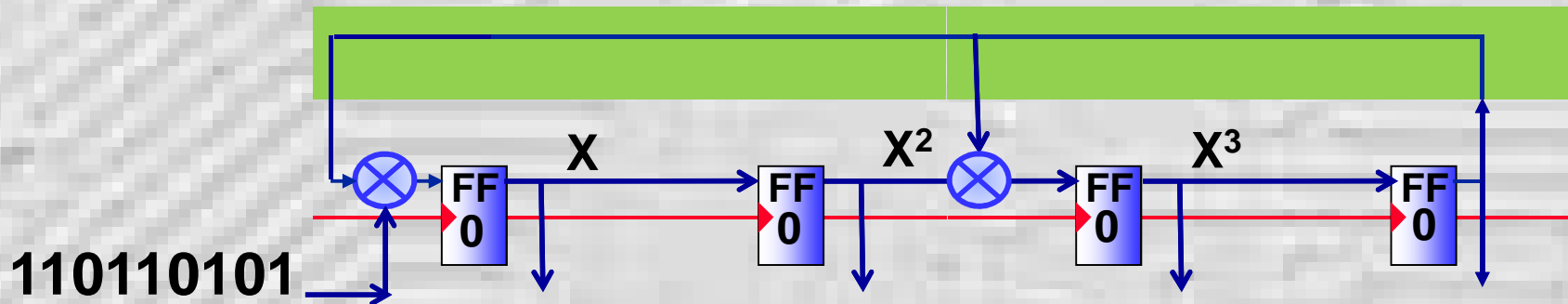

# BIST


IN2P3

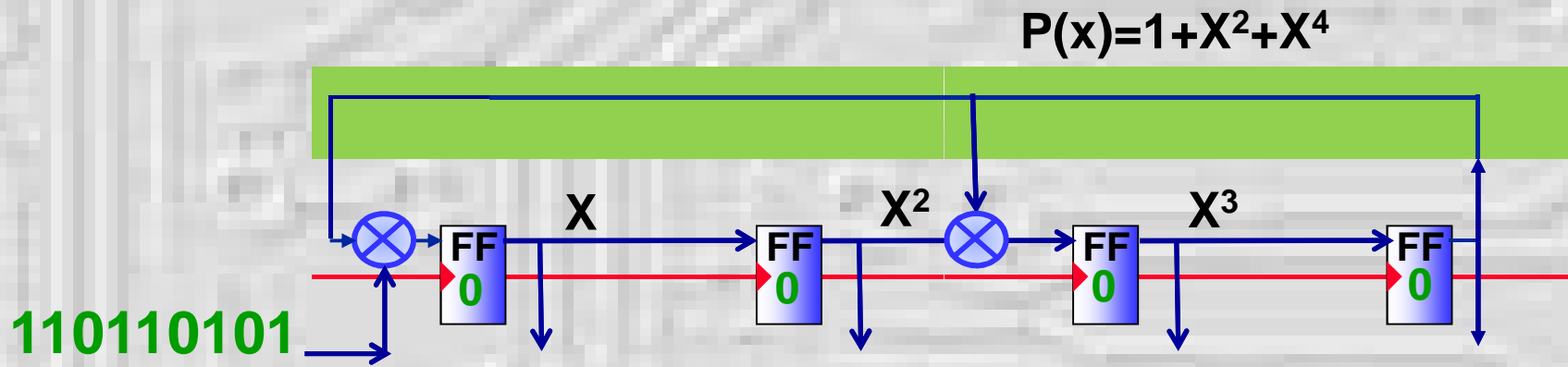

# BIST

IN2P3

$$P(x) = 1 + X^2 + X^4$$


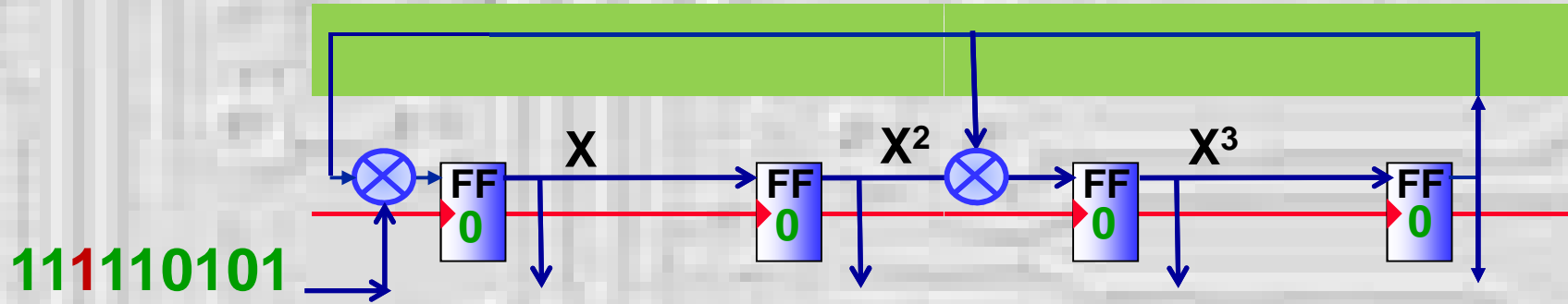


111110101




# BIST

IN2P3

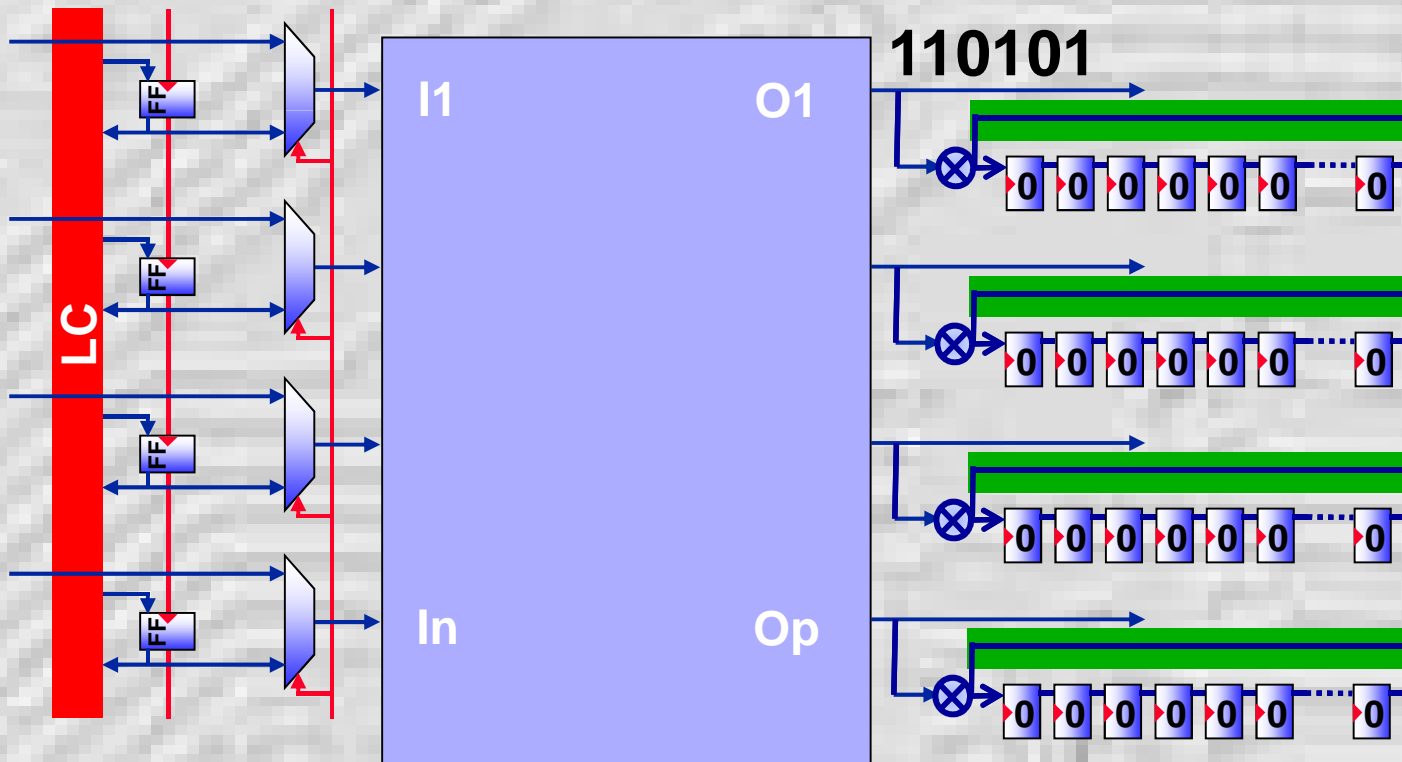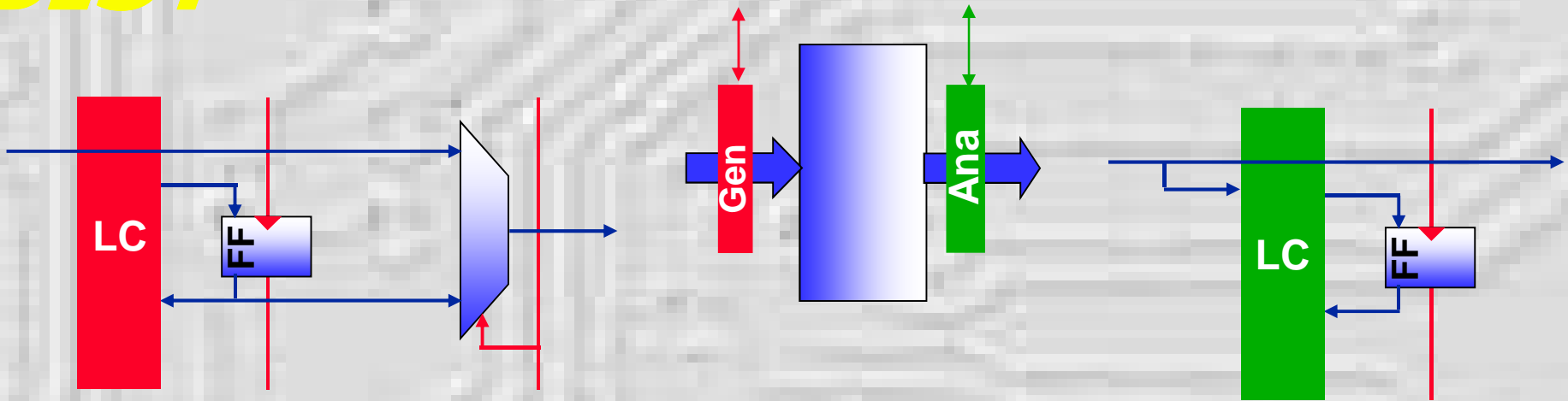

# BIST

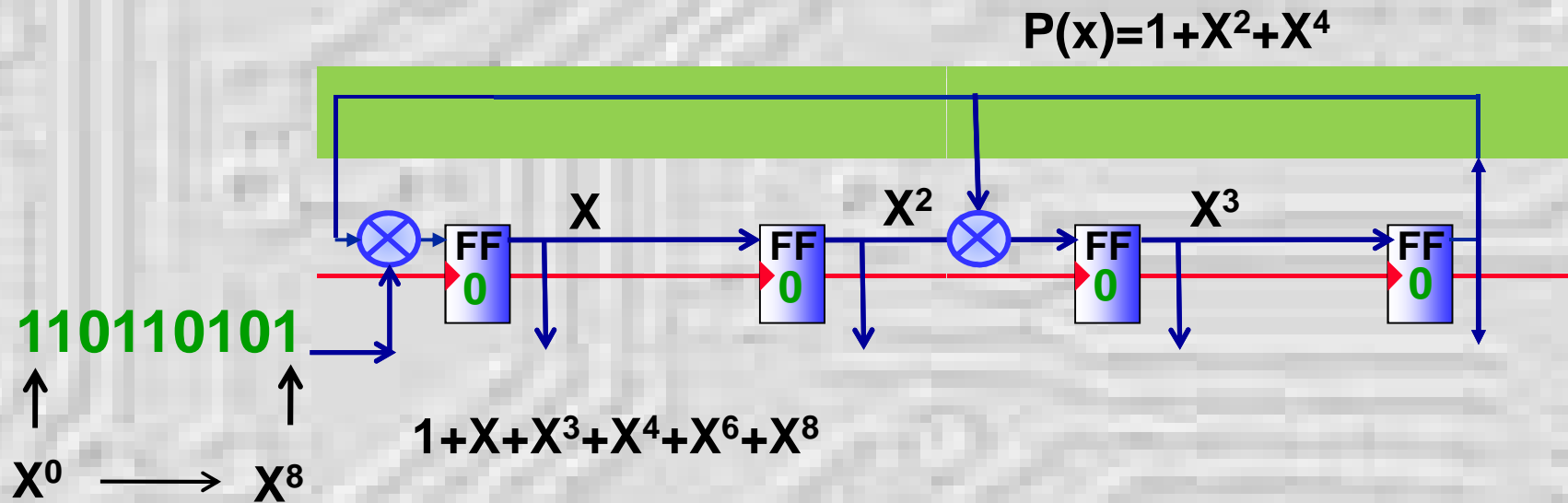


$$\begin{array}{r|l}
 X^8 + X^6 + X^4 + X^3 + X + 1 & X^4 + X^2 + 1 \\
 X^8 + X^6 + X^4 & \hline
 \hline
 0X^8 + 0X^6 + 0X^4 + X^3 & X^4 \\
 \quad \quad \quad 0 & \\
 \quad \quad \quad \hline
 \quad \quad \quad X^3 + X & \\
 \quad \quad \quad \quad \quad 0 & \\
 \quad \quad \quad \quad \quad \hline
 \quad \quad \quad X^3 + X + 1 &
 \end{array}$$

$$\begin{array}{r|l}
 101011011 & 10101 \\
 10101 & \hline
 \hline
 000001 & 10000 \\
 \quad \quad 0 & \\
 \quad \quad \hline
 \quad \quad 10 & \\
 \quad \quad \quad \quad 00 & \\
 \quad \quad \quad \quad \hline
 \quad \quad \quad 101 & \\
 \quad \quad \quad \quad 000 & \\
 \quad \quad \quad \quad \hline
 \quad \quad \quad 1011 &
 \end{array}$$


# BIST

IN2P3

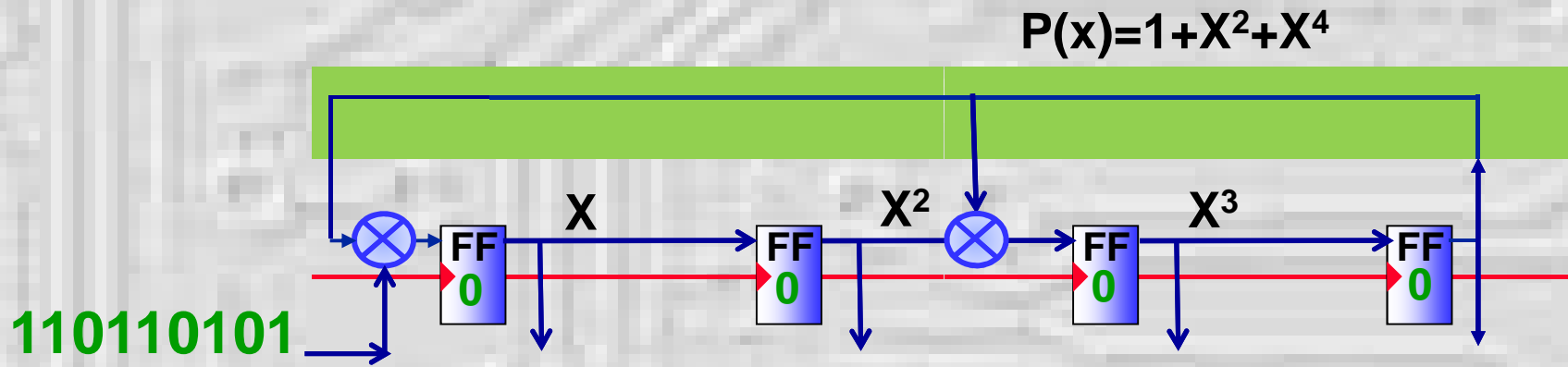

# BIST

IN2P3

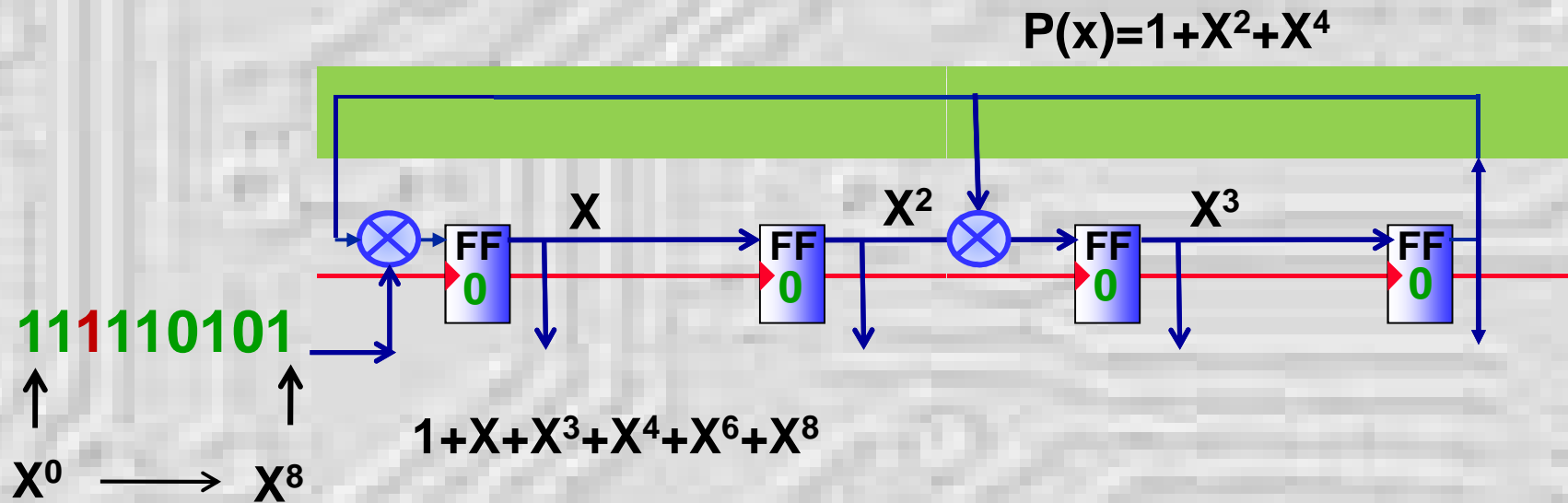

$$\begin{array}{r}
 X^8 + X^6 + X^4 + X^3 + X^2 + X + 1 \\
 \underline{X^8 + X^6 + X^4} \\
 0X^8 + 0X^6 + 0X^4 + X^3 \\
 \quad \underline{0} \\
 \quad X^3 + X^2 \\
 \quad \quad \underline{0} \\
 \quad \quad X^3 + X^2 + X \\
 \quad \quad \quad \underline{0} \\
 \quad \quad X^3 + X^2 + X + 1
 \end{array}$$

$$\begin{array}{r}
 X^4 + X^2 + 1 \\
 \hline
 X^4
 \end{array}$$

$$\begin{array}{r}
 101011111 \\
 \underline{10101} \\
 000001 \\
 \quad \underline{0} \\
 \quad 11 \\
 \quad \quad \underline{00} \\
 \quad \quad 111 \\
 \quad \quad \underline{000} \\
 \quad \quad 1111
 \end{array}$$


$$\begin{array}{r}
 10101 \\
 \hline
 10000
 \end{array}$$




# BIST

IN2P3

$$P(x) = 1 + X^2 + X^4$$

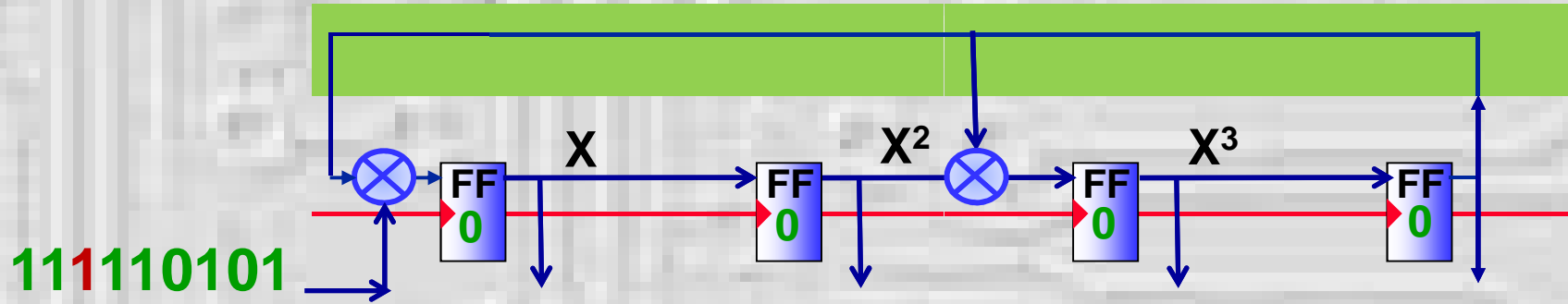

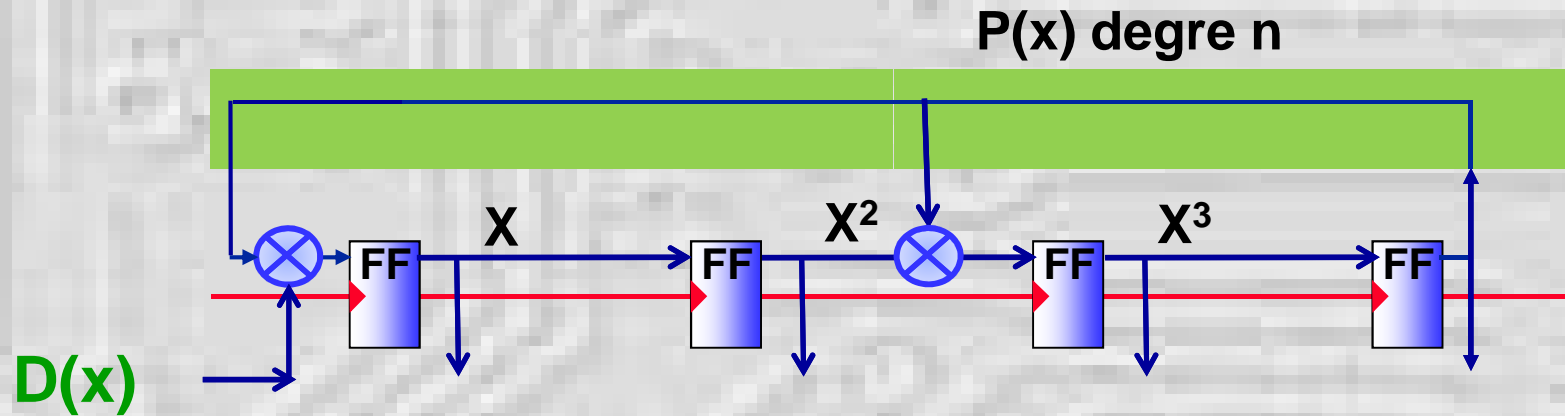

$$D(x) = P(x) \cdot Q(x) + R(x)$$



$$D'(x) = P(x) \cdot Q'(x) + R'(x)$$

Probability  $R(x) = R'(x)$

Aliasing

Prob= $1/2^n$

# BIST

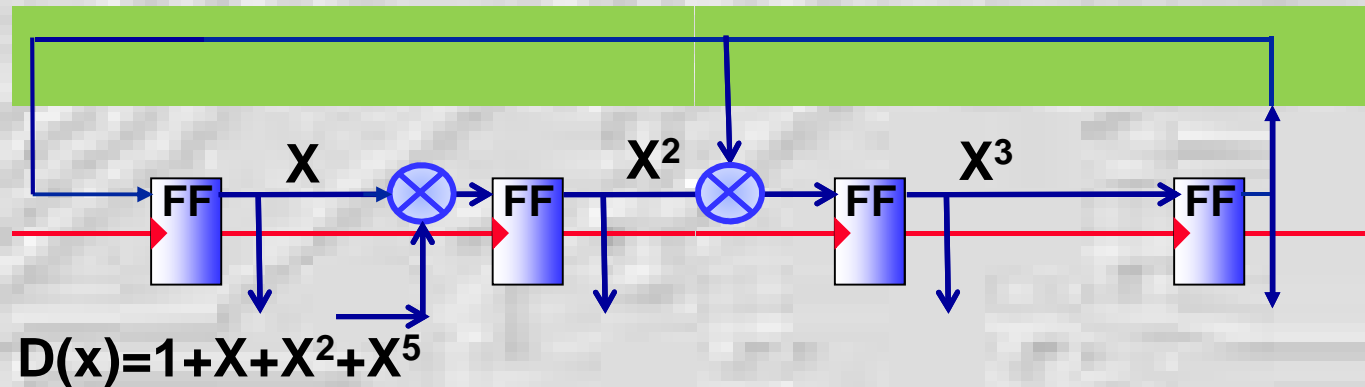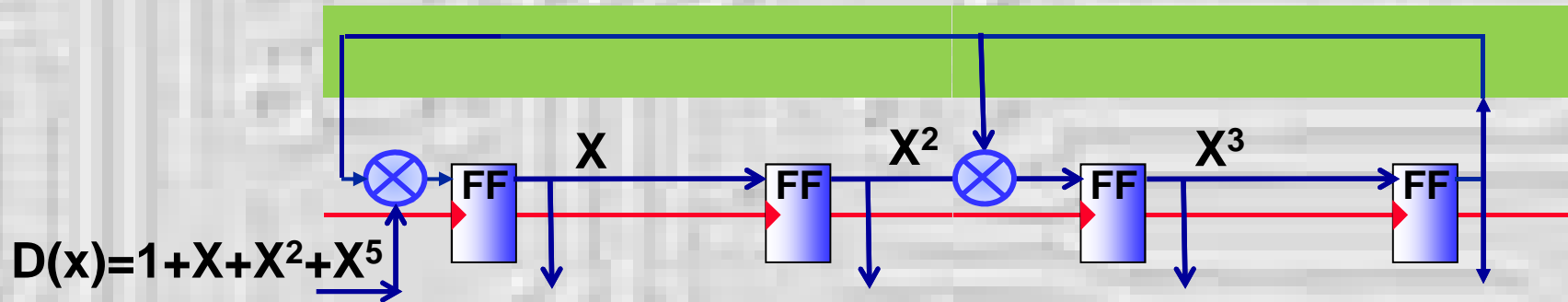


Aliasing

$P = 1/2^n$

$$\begin{array}{r}
 X^5 + X^2 + X + 1 \\
 \underline{X^5 + X^3 + X} \\
 1X^3 + 1X^2 + 0X + 1
 \end{array}
 \quad \left| \begin{array}{r}
 X^4 + X^2 + 1 \\
 \hline
 X
 \end{array}
 \right.$$

↻

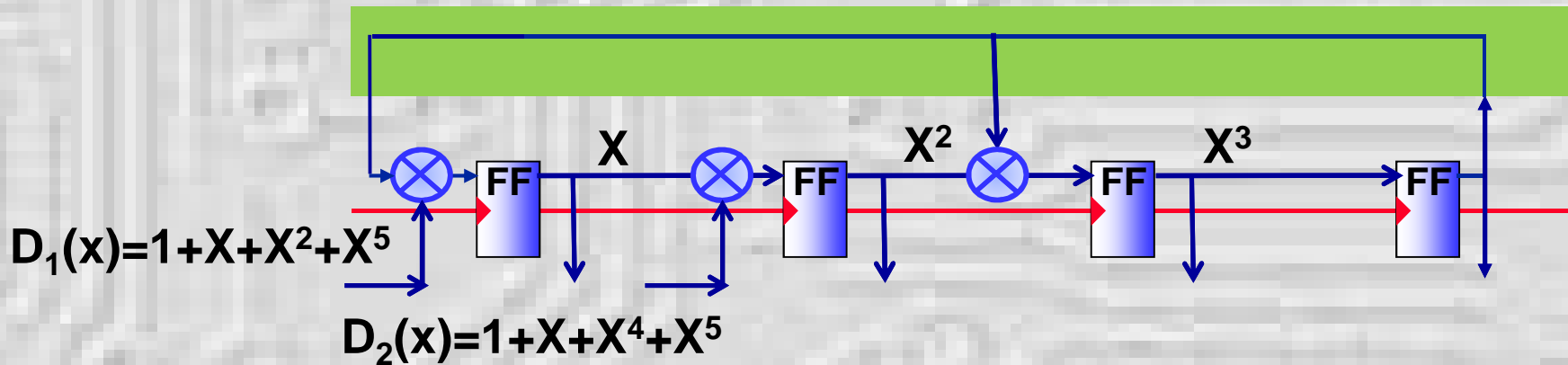

$$D_1(x) = P(x) \cdot Q_1(x) + R_1(x)$$

$$D_2(x) = P(x) \cdot Q_2(x) + R_2(x)$$


$$\left\{ \begin{array}{l} \Rightarrow R(x) = R_1(x) \otimes R_2(x) \\ \Rightarrow R'(x) = R'_1(x) \otimes R_2(x) \\ \Rightarrow R'(x) = R_1(x) \otimes R'_2(x) \end{array} \right.$$

**Aliasing**

$$P = 1/2^n$$


# BIST

IN2P3

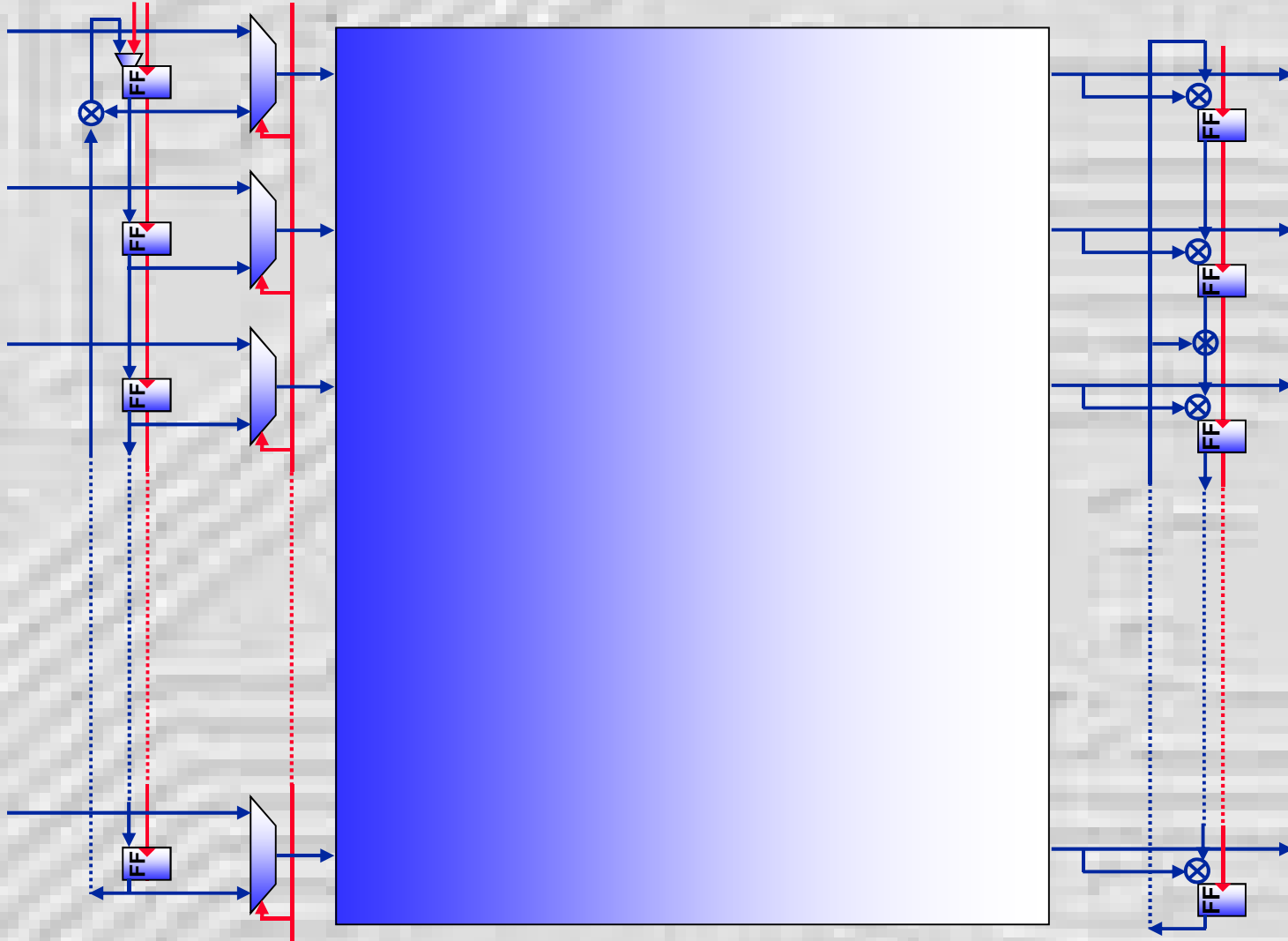

# BIST

IN2P3

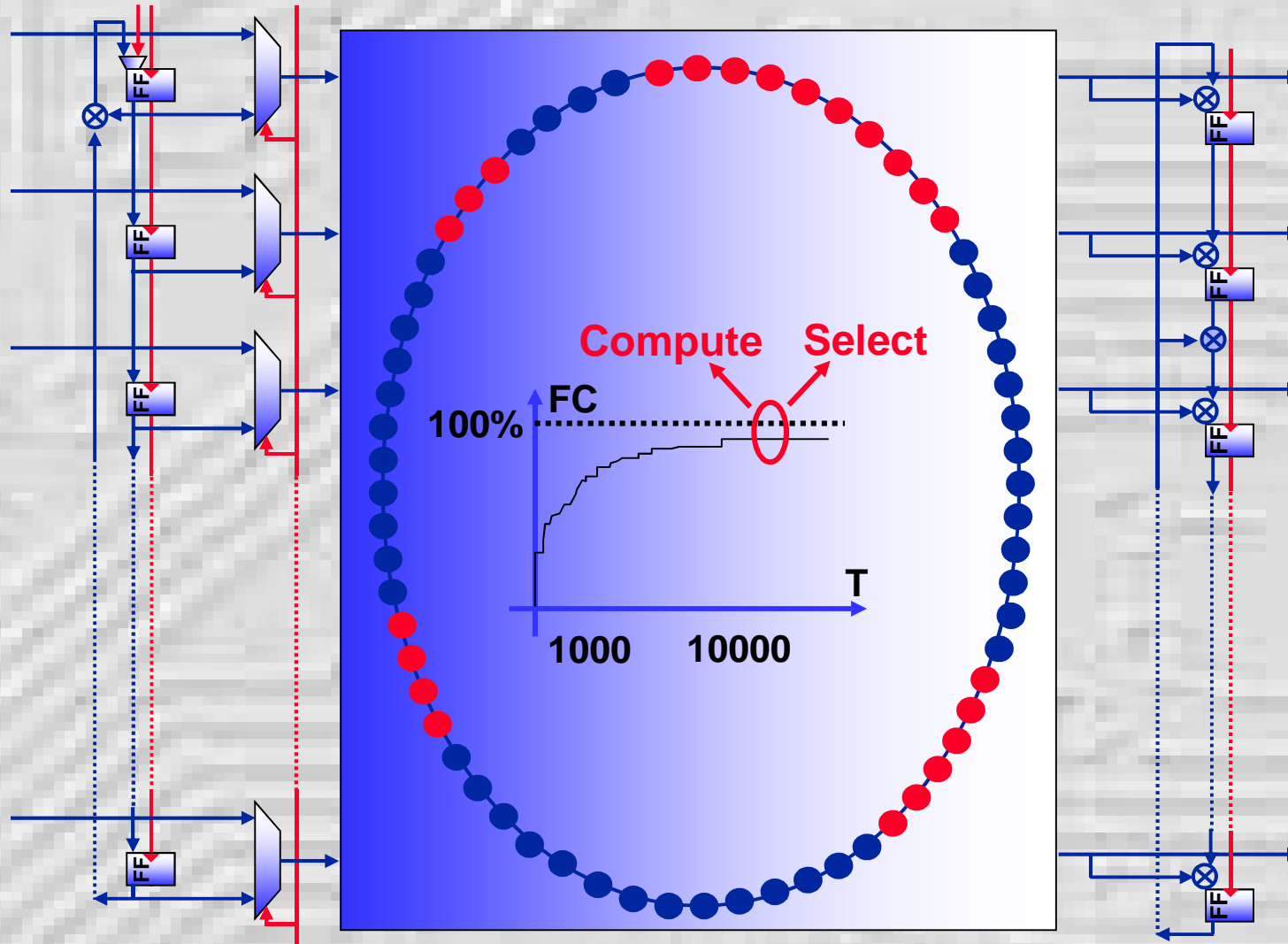

■ Test Length<sup>2</sup>

■ Seed/Clock

■ Reconf Polyn

# BIST

IN2P3

## IBM STUMPS

