

12 bit – 25 MHz – Pipeline Analog to Digital Converter


Ecole de Microélectronique IN2P3
Fatah-Ellah RARBI
LPSC Grenoble

Outline

- Architecture project
 - ADC: 1.5 bits
 - ADC: 2,5 bits
- ADC test
 - ADC parameters
 - Static parameters
 - Dynamic parameters
 - Test method
- Conclusions

Slow vs High speed ADC configuration

ILC – ECAL configuration

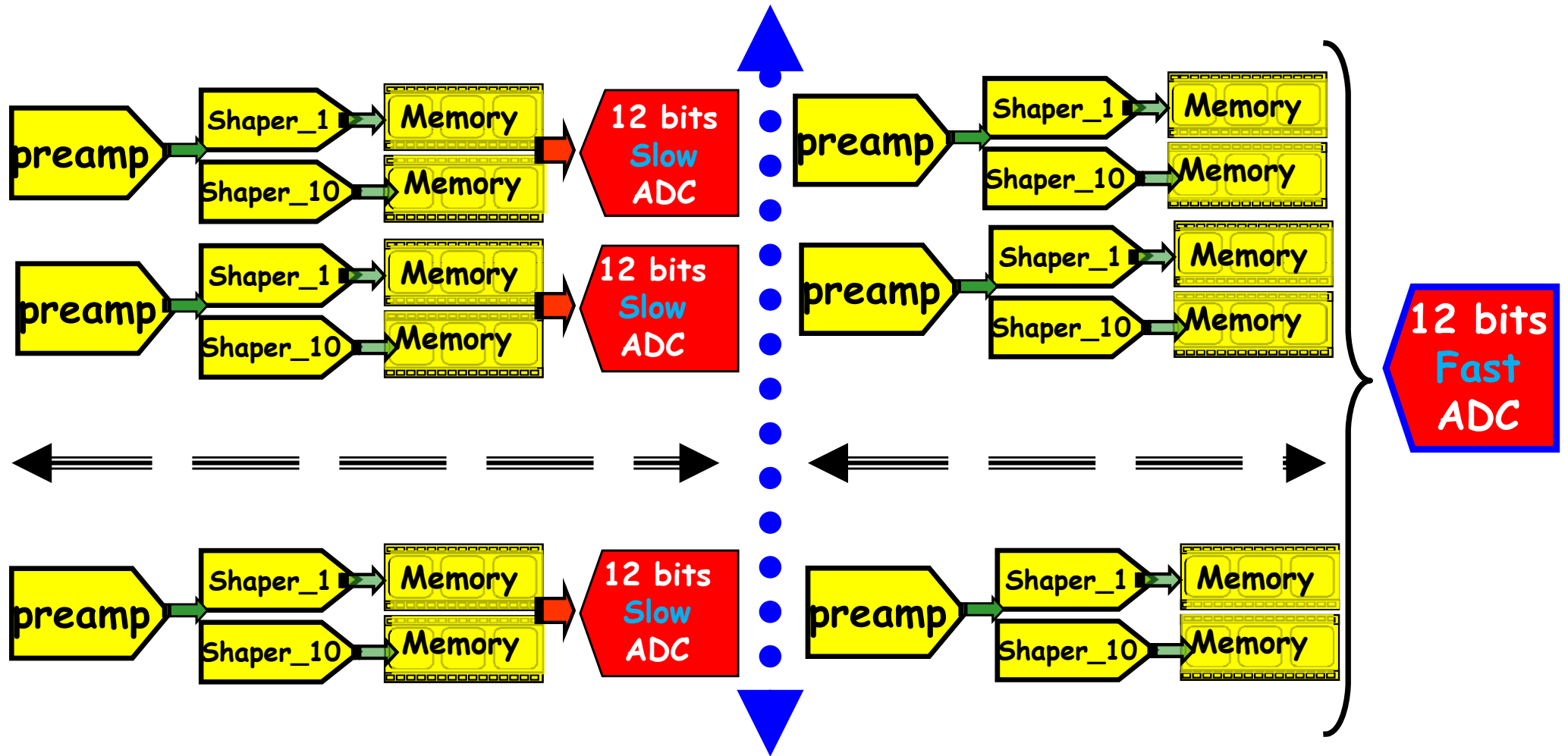

High speed ADC industrial purpose


- **MEMS**

- Gyroscope
- Accelerometer

- **Imaging applications**



- Infrared Bolometer
- Cryogenic Bolometer
- Nanowire sensor (LOAG Lab)

Pipeline ADC architecture (1)

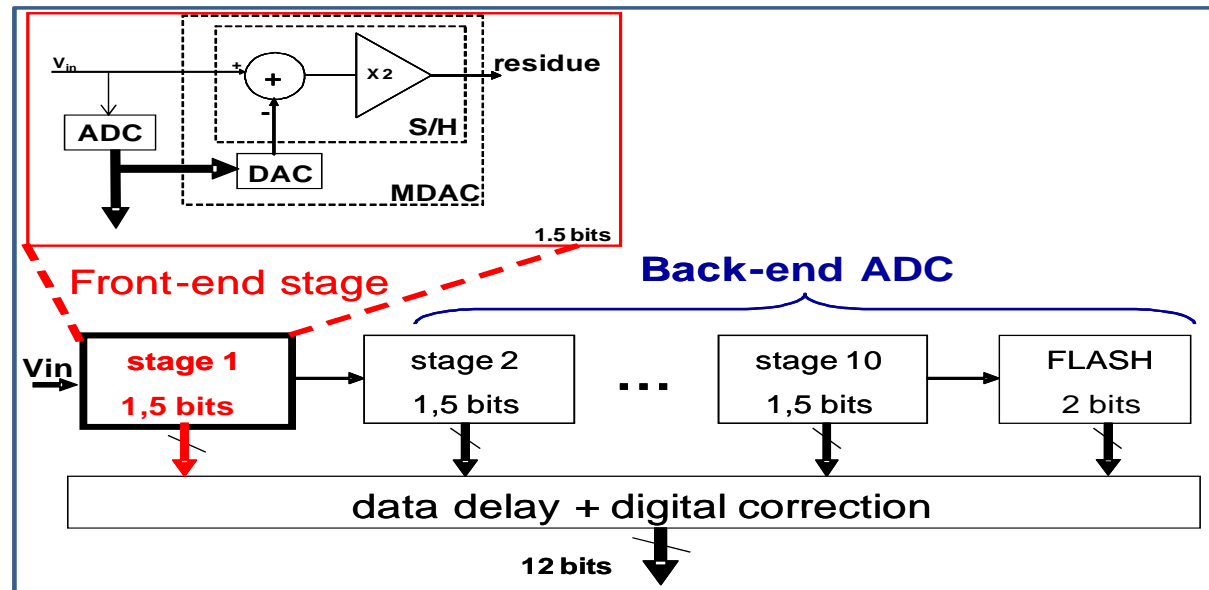

Dynamic
Comparator




1.5 bit MDAC

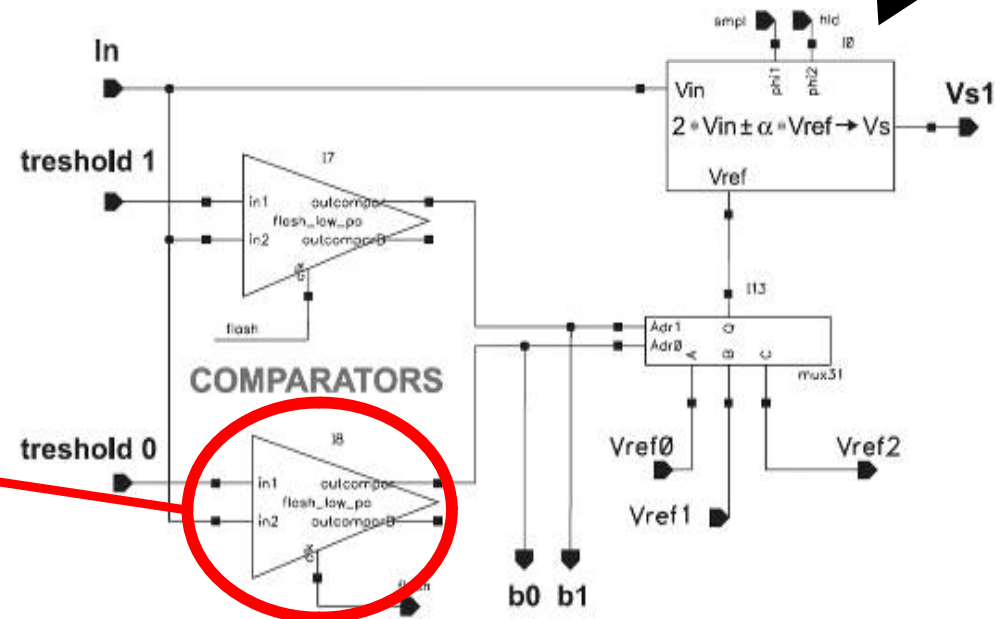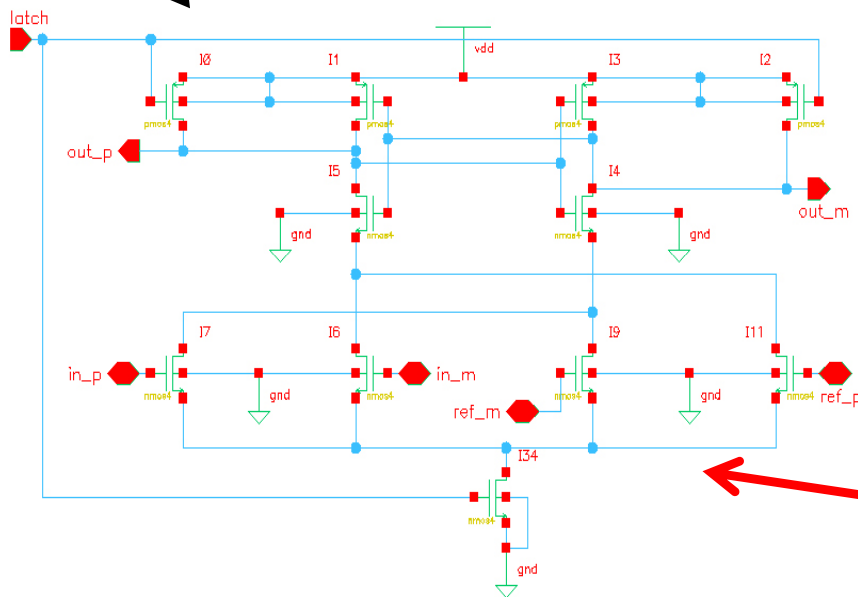

Pipeline ADC architecture (2)

Sampling phase

Hold phase

 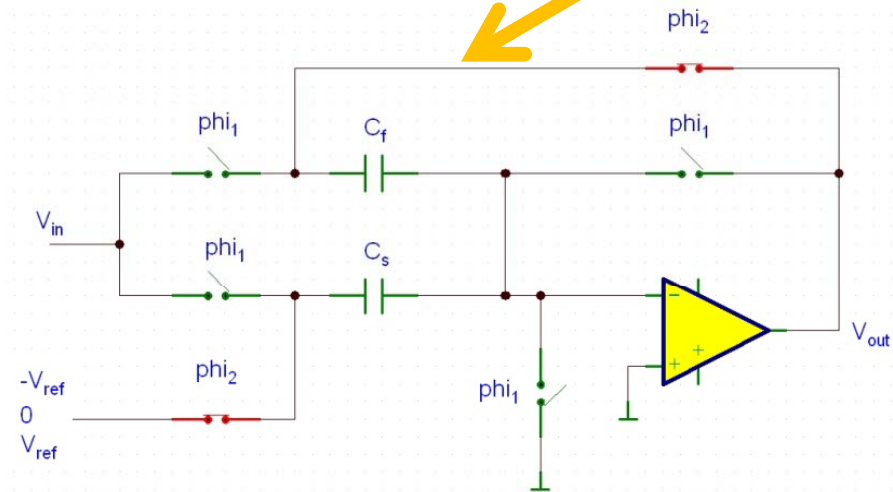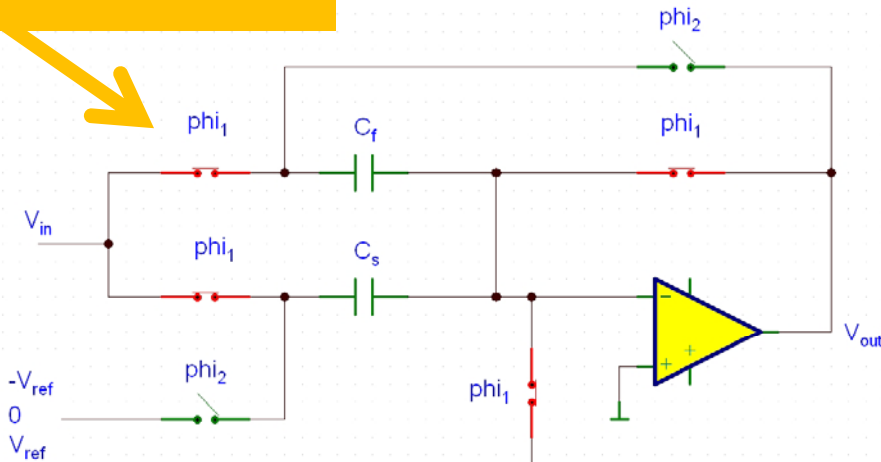


$$V_{out} = 2 \cdot V_{in} - d_i \cdot V_{ref}$$

$$d_i = \{-1, 0, +1\}$$



Pipeline ADC architecture (3)

Comparator Offset


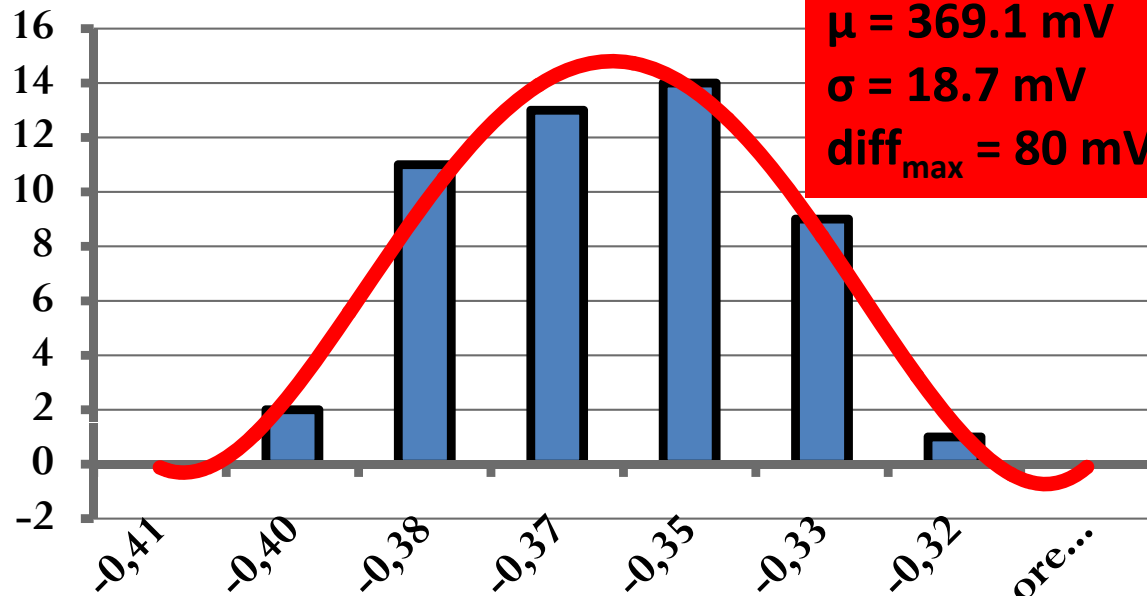


• ADC block:


- 2 dynamic comparators
- Offset allowed: $V_{\text{ref}}/4$

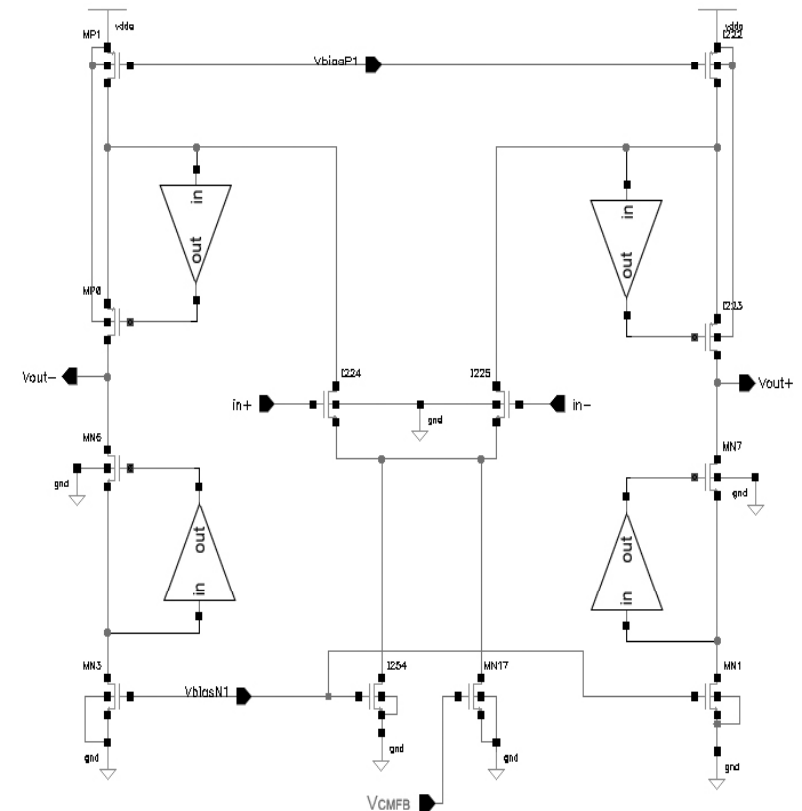 


Full 1.5 bit Pipeline ADC

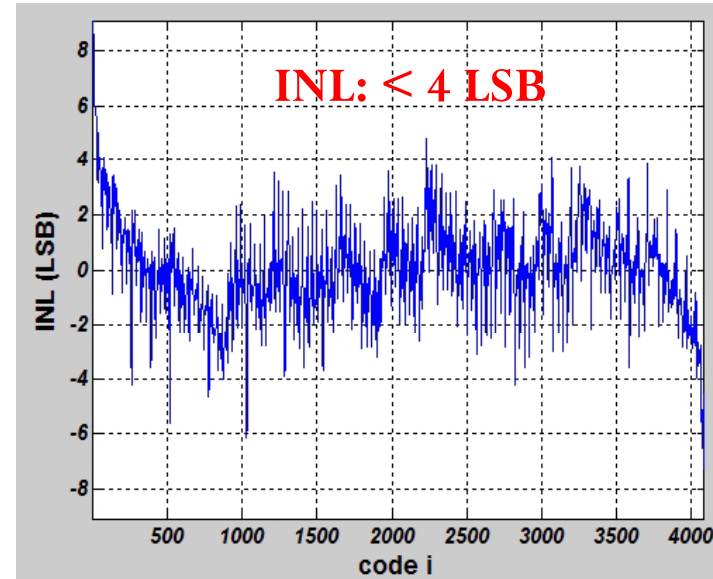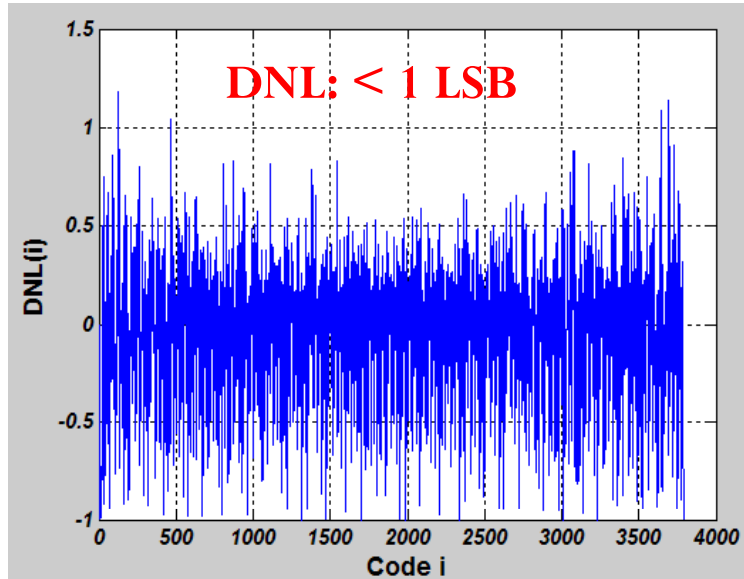

 - Process matching is limiting to 10 bits
 - Increase resolution in 1st stage
 - Difficult to design OTA block
 - Comparator offset
 - **Capacitor Matching**
 - Digital gain correction
 - Dynamic Element Matching
 - Still under study



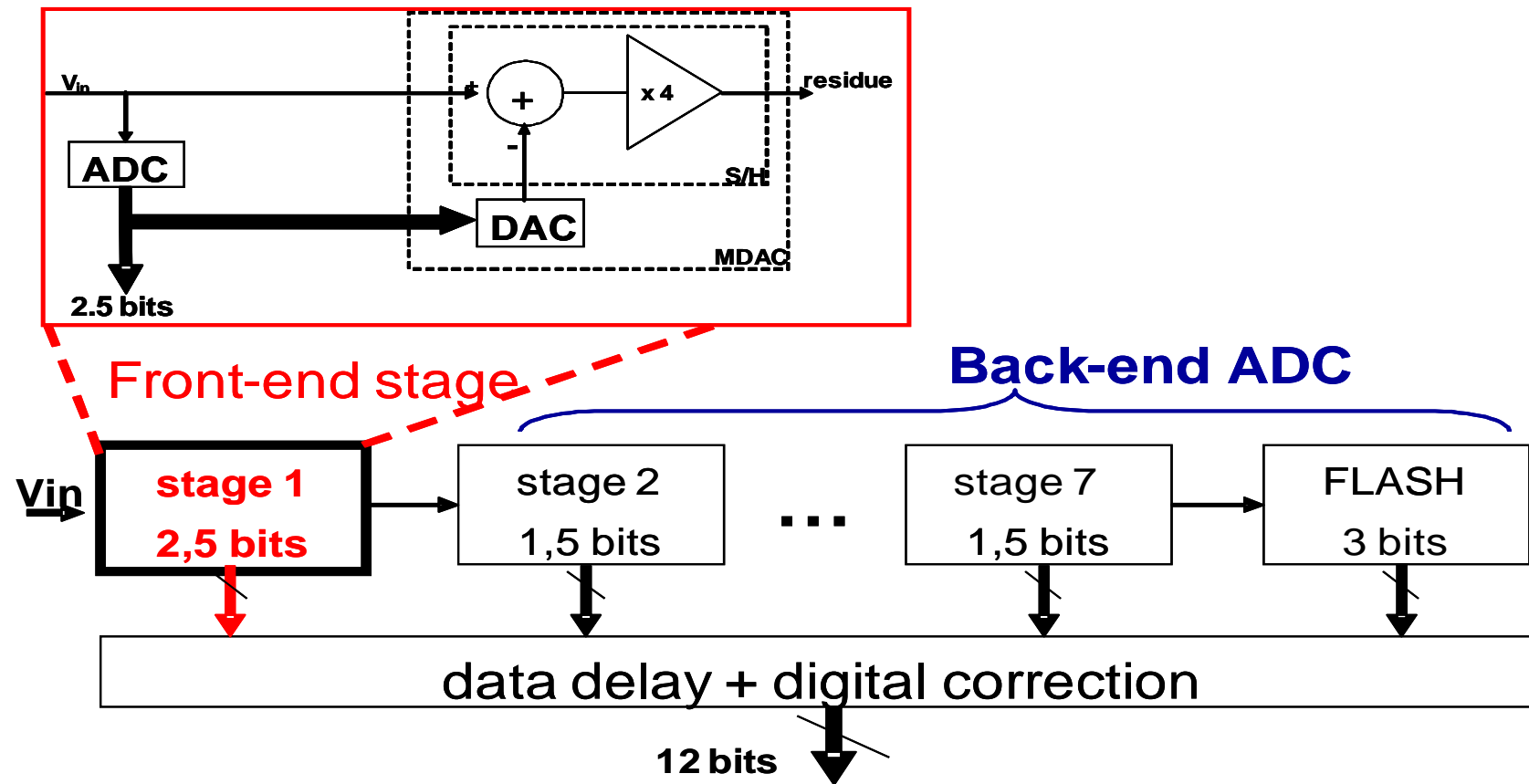Pipeline ADC with Multi-bit first stage (1)




- Multi-bit 1st stage: 2.5 bit
 - MDAC with a gain of 4
- Back-end composed by 6*1.5 bit stage and a 3 bit flash ADC



Pipeline ADC with Multi-bit first stage (2)

- Multi-bit 1st stage: 2.5 bit => 1st prototype

 
Capacitor
Matching more
critical on 2.5
bit stage



Linearity
about ± 8 LSB

 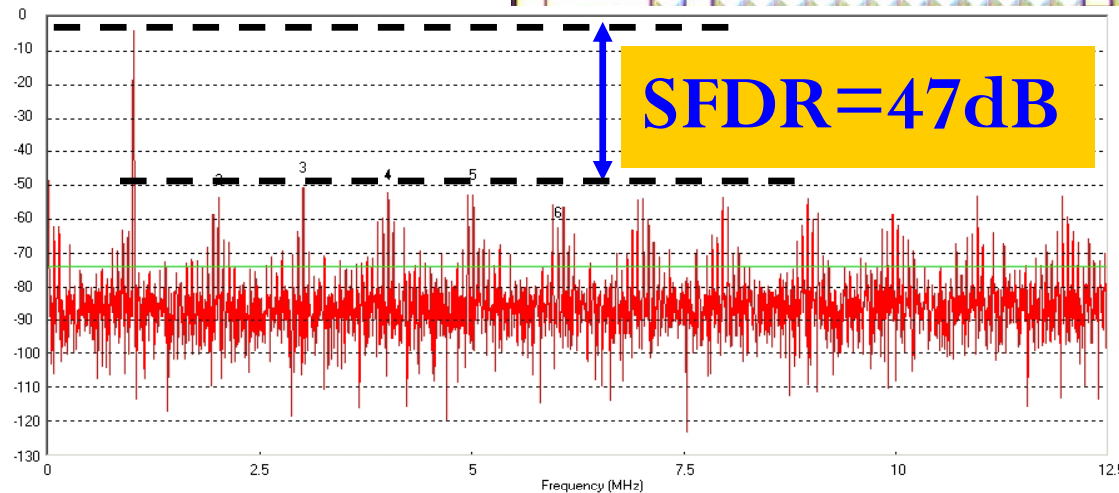

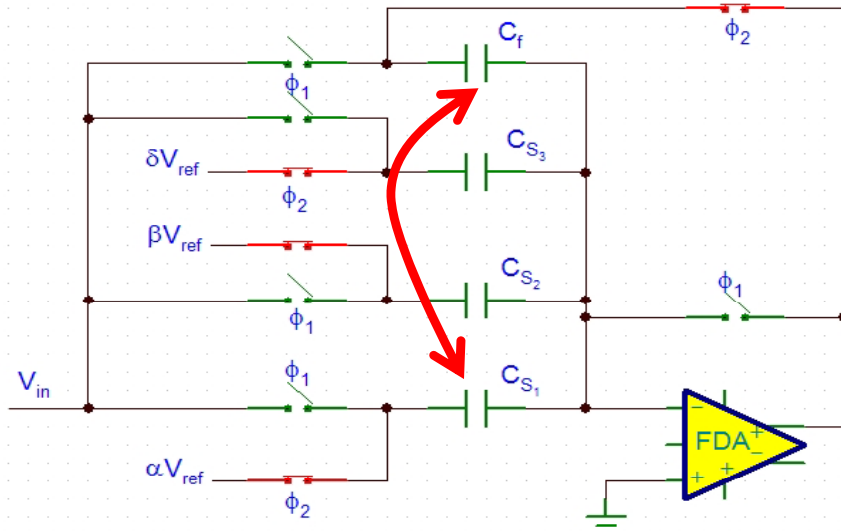
Pipeline ADC with Multi-bit first stage (3)





$$V_{out} = \left(\frac{\sum_{i=1}^3 C_{s_i} + C_f}{C_i} \right) \times V_{in} \pm \alpha \times \left(\frac{\sum C_j}{C_i} \right) \times V_{ref}$$

$$i = \{1, 2, 3, f\}, i \oplus j = 0$$

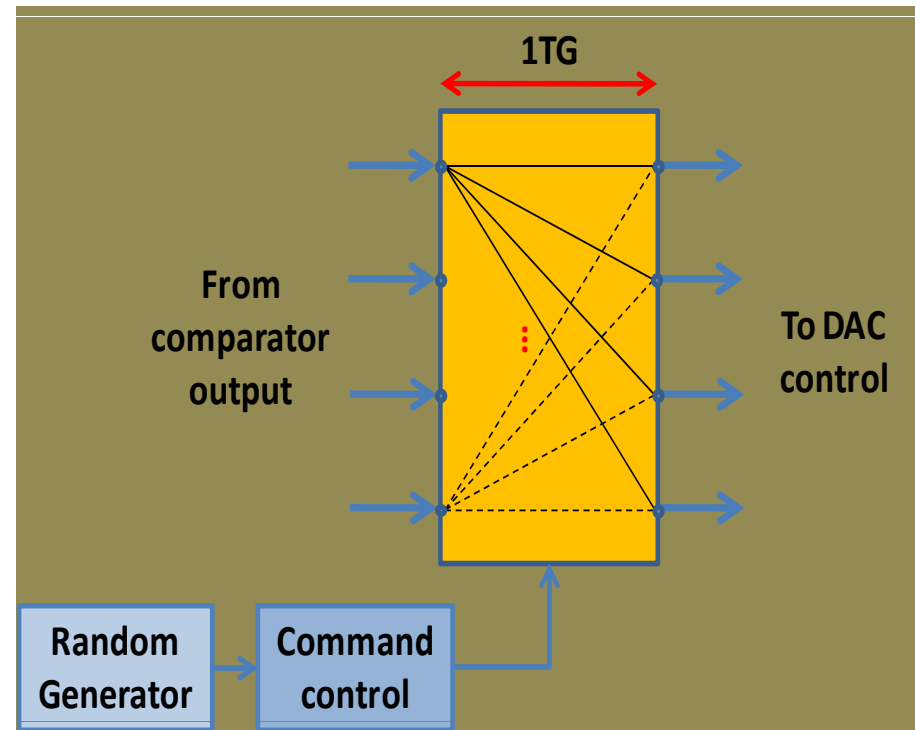
- Dynamic element
 - Random selection of the feedback capacitor
 - Closed loop Gain modulation
 - 1 Transmission gate from comparator output to DAC control
 - Distortion => Noise



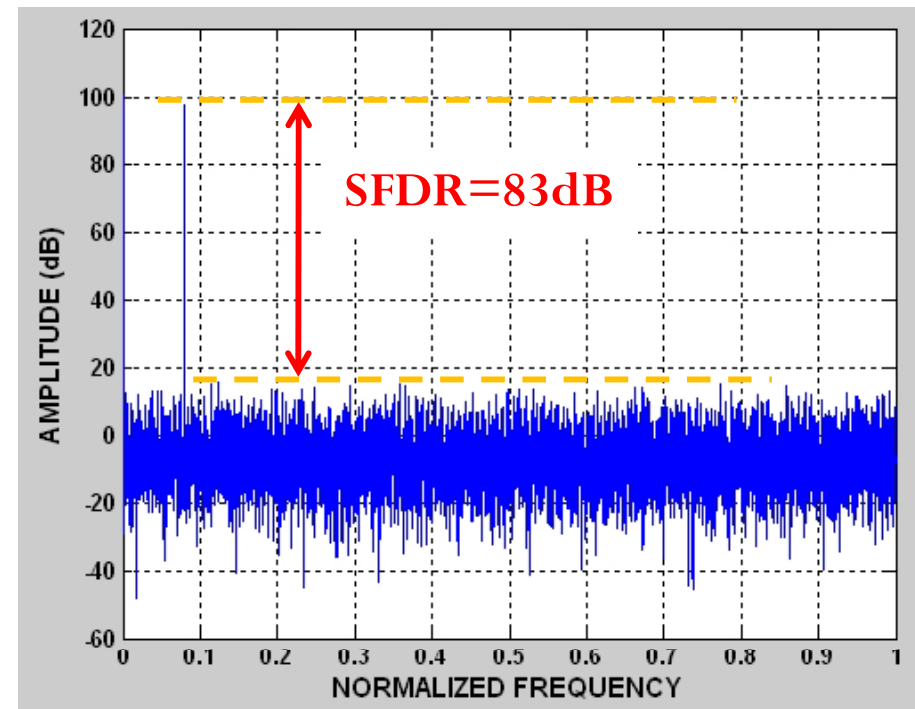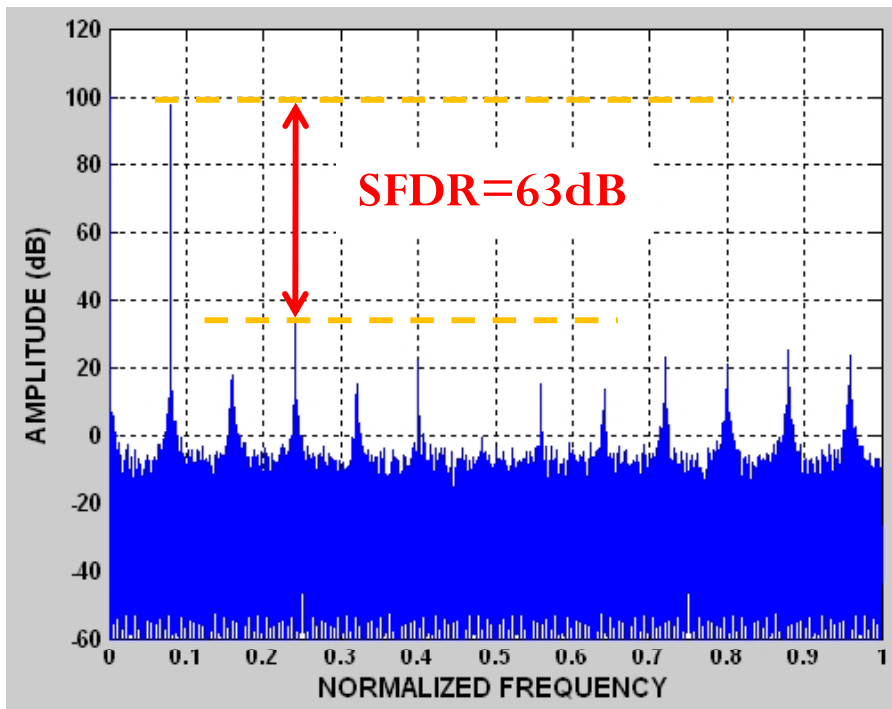Pipeline ADC with Multi-bit first stage (4)



 
- Dynamic Element Matching: MATLAB simulation
 - Distortion \Rightarrow Noise
 - SFDR is increased
 - Improve linearity



Submitted on
September 09



ADC test: Configuration

- Test configuration

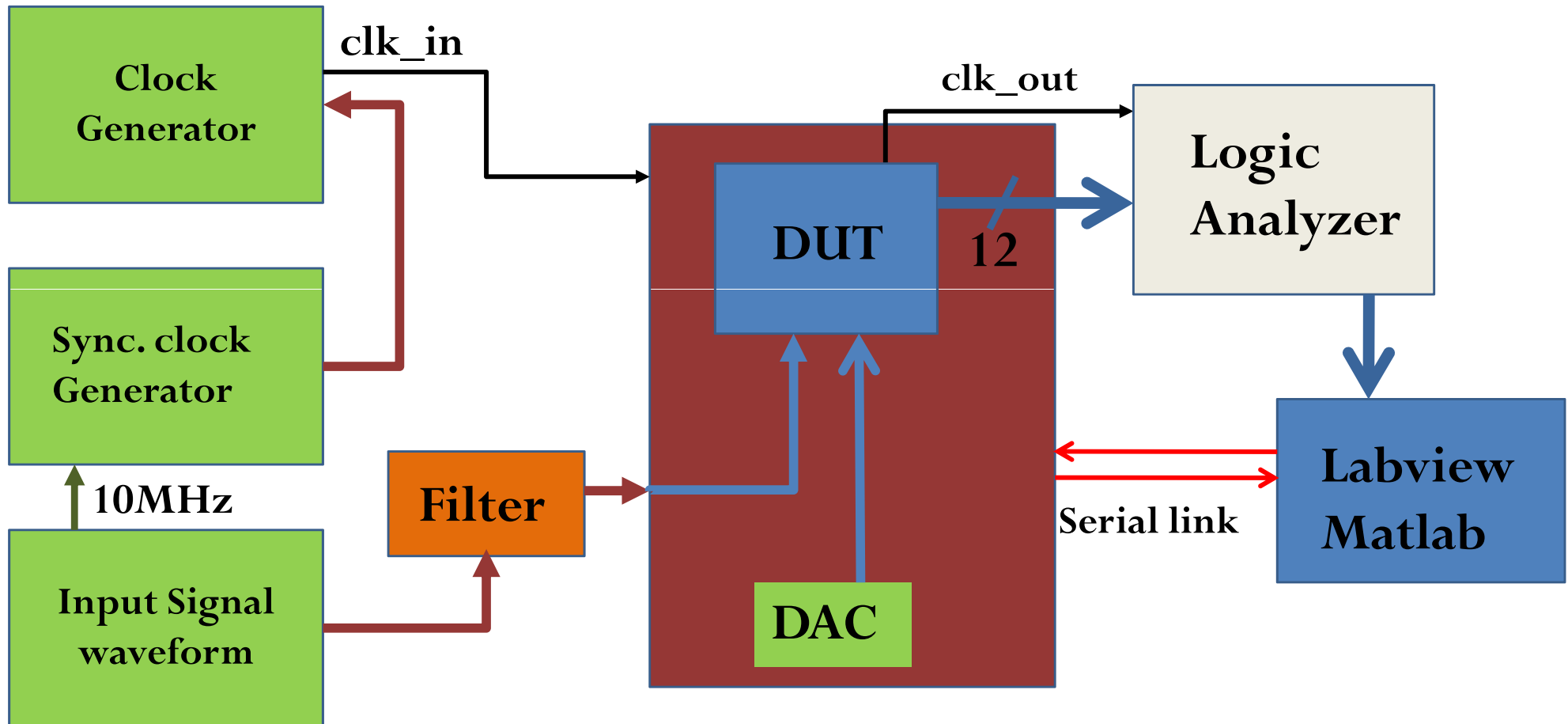

ADC test: parameters (1)

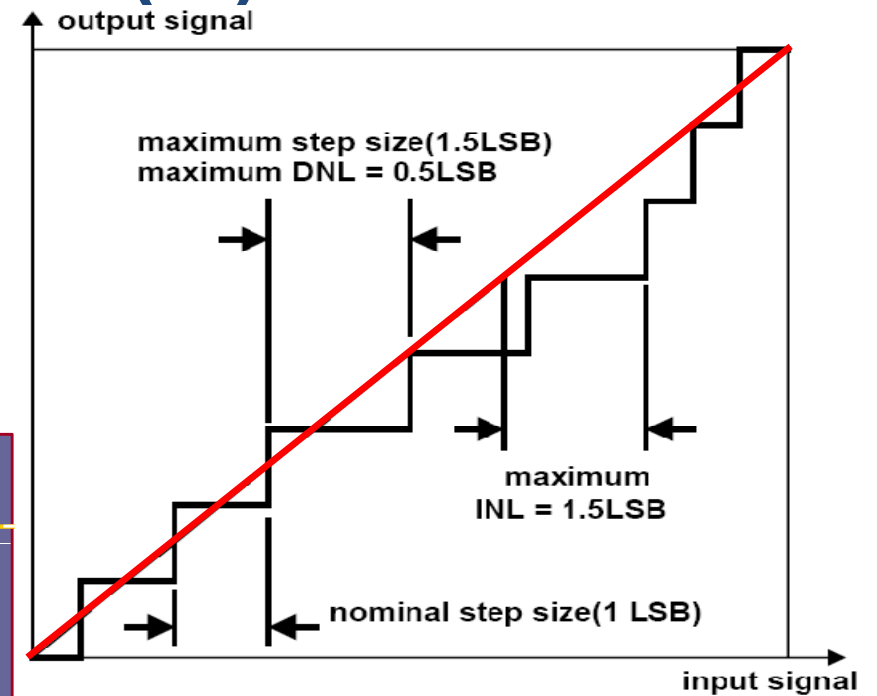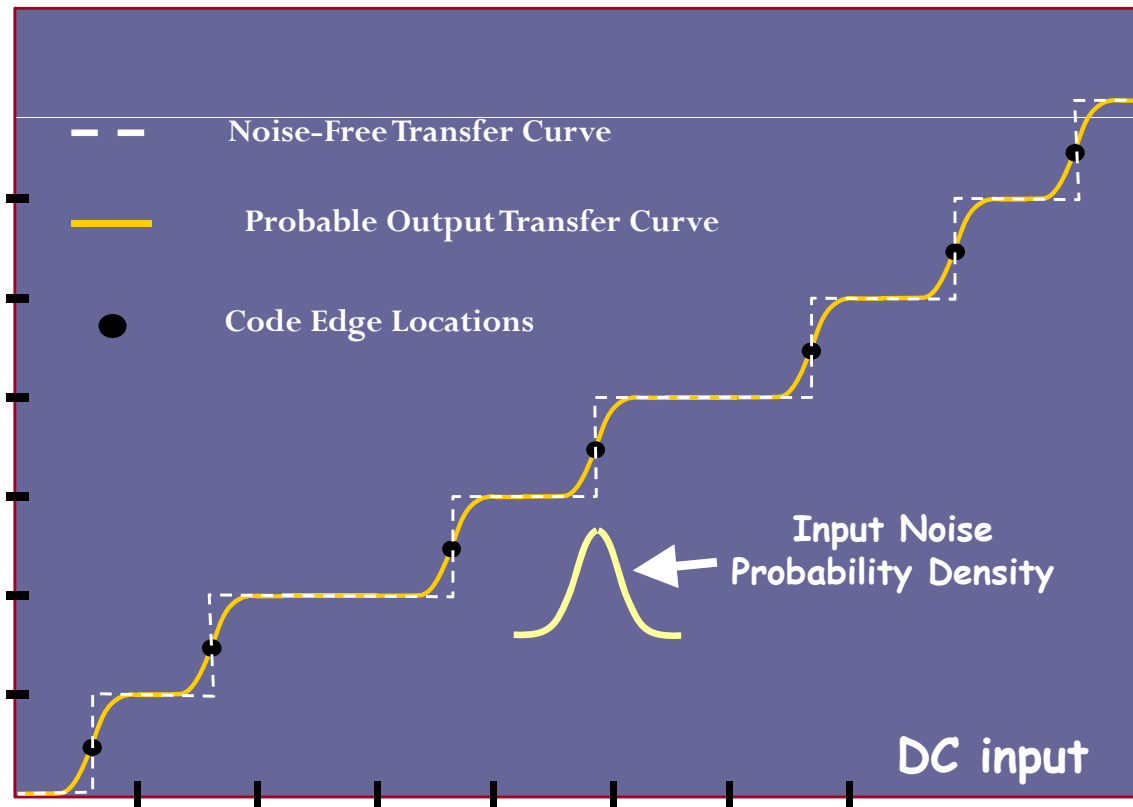- Static parameters
 - Differential Non Linearity (DNL)
 - Integral Non Linearity (INL)
 - Noise



ADC test: parameters (2)

- Dynamic parameters

- Noise floor => SNR


- SINAD => ENOB

- SFDR => Linearity

- ...

$$\frac{\text{SINAD} - 1.76}{6.02}$$
 
$$\text{SNR} + 10 * \log_{10} \left(\frac{M}{2} \right)$$






Test Method (1): Full 1.5 bit stage ADC

- Tools: Labview + MATLAB
- **Ramp input signal**
 - DC parameter extraction (Labview)
 - Step size = LSB
 - > 100 points by step
 - INL: fit of the output transfer function
- **Sine wave input signal**
 - Static parameters => Histogram (statistical results) (MATLAB script)
 - Coherent sampling (excel script: MAXIM IC)
 - Dynamic parameters => FFT

Test Method (2) : Full 1.5 bit stage ADC

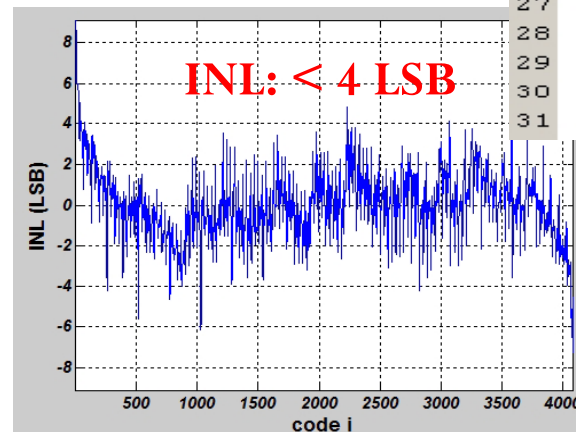  - Tools: MATLAB
- Sine wave input signal
 - Static parameters => Histogram (statistical results) (MATLAB script)



```
1 % DNL and INL extraction from histogram plot
2 my_minbin=min(my_data);
3 my_maxbin=max(my_data);
4 % Histogram plot
5 figure(1);
6 hist(dat,my_minbin:my_maxbin);
7 xlabel('Code i'); title('histogramme'); grid
8 my_h=hist(dat,my_minbin:my_maxbin);
9 % Cumulative histogram
10 my_ch=cumsum(my_h);
11 % Edge level
12 my_T=-cos(pi*my_ch/sum(my_h));
13 %linearise
14 my_hlin=my_T(2:end) - my_T(1:end-1);
15 % Cut min and max
16 trunc=2;
17 hlin_trunc = my_hlin(1+trunc:end-trunc);
18 % calculate DNL
19 my_dnl= [0 hlin_trunc/my_lsb-1];
20 misscodes = length(find(my_dnl<-0.9));
21 % DNL Plot
22 hold off; figure (2);
23 plot(my_dnl);
24 xlabel('Code i'); ylabel('DNL(i)');grid
25
26 % Calculate INL
27 my_inl= cumsum(my_dnl);
28 % INL Plot
29 hold off; figure (3);
30 plot(my_inl);
31 xlabel('Code i');ylabel('INL(i)');grid
```

Test Method (3) : Full 1.5 bit stage ADC

- Tools: MATLAB
- Sine wave input signal
 - Coherent sampling (excel script: MAXIM IC)

$$\frac{f_s}{f_{in}} = \frac{N_{tot}}{N_{wind}}$$

→ prime number


Example:

$$f_s = 25 \text{ MHz} \quad f_{in} = 1 \text{ MHz}$$

$$N_{tot} = 2^{14}$$

$$N_{wind} = 657$$

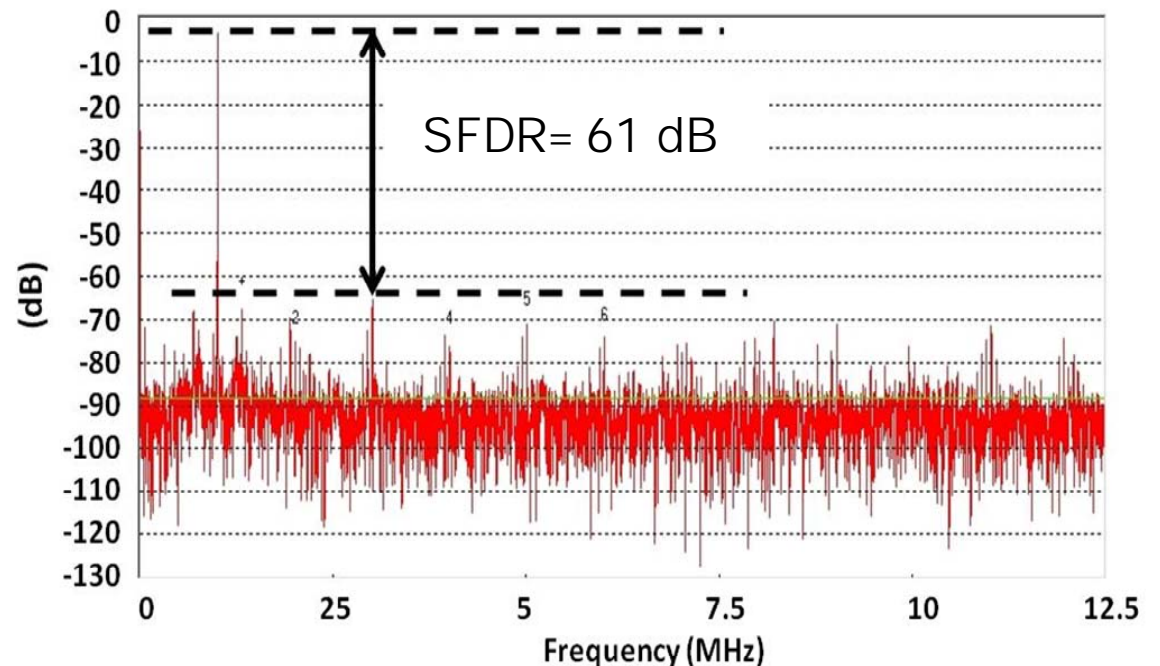
$$f_{in} = 1.0025024414 \text{ 06250 MHz}$$



Conclusions (1)

- Pipeline ADC 25MHz - < 40mW
 - 2 versions: 1.5 bit stages, multi-bit first stage
- Figure of Merit (FoM) → ADC with full 1.5 bit stage
 
$$FoM = \frac{Power}{2^{ENOB} \cdot f_s} \bullet V_{dd}$$



Conclusions (2)

- ADC Test
 - Parameters
 - Methods

**Testing results reliability
Depend very often
on SETUP & METHOD used**

12 bit – 25 MHz – Pipeline Analog to Digital Converter

Ecole de Microélectronique IN2P3

Fatah-Ellah RARBI – Daniel Dzahini – Laurent Gallin-Martel

LPSC Grenoble

**Thanks for your
attention**